

Chapter 5

Synchronous Sequential Logic

1


Outline

- Sequential Circuits
- Storage Elements: Latches
- Storage Elements: Flip-Flops
- Analysis of Clocked Sequential Circuits
- Synthesizable HDL Model of Sequential Circuits
- State Reduction and Assignment
- Design Procedure

2

Sequential Circuits

 - Combinational circuits contain no memory elements and the outputs depends on the current inputs.
- Sequential circuits:



- a feedback path
- Memory to store the state of the sequential circuit
- Combinational circuit computes (inputs, current state) \Rightarrow (outputs, next state)
- synchronous: the transition happens at discrete instants of time
- asynchronous: depends on the input signals at any instant of time and the order in which the inputs change. (instable)


3

Synchronous Sequential Circuits

- A master-clock generator generates a periodic train of clock pulses and distributes it throughout the system.
- The clocked sequential circuit has no instability problems
- the memory elements: Flip-Flops
 - Binary cells capable of storing one bit of information
 - Two outputs: one for the normal value and one for the complement value
 - Maintain a stable binary state indefinitely until directed by an input signal to switch states

4

Synchronous Clocked Sequential Circuit

 


1. The stored value in a flip-flop is updated when a pulse of the clock signal occurs.
2. The output of the combinational circuit (CC) must reach a stable state before the next clock pulse. \Rightarrow speed limited by CC.
3. If clock pulse is not active \Rightarrow feedback loop is broken \Rightarrow value of flip-flop is not updating.

5

SR Latch with NOR Gates

- Latch can be formed by two cross-coupled NOR gates
 - $(S, R) = (0, 0)$: no operation (Q and Q' state unchanged)
 - $(S, R) = (0, 1)$: reset state ($Q = 0$ and $Q' = 1$)
 - $(S, R) = (1, 0)$: set state ($Q = 1$ and $Q' = 0$)
 - $(S, R) = (1, 1)$: undefined state ($Q = Q' = 0$)
 - Latch is an asynchronous sequential circuit. (state changes whenever inputs change).
 - The (S, R) must go back to $(0, 0)$ before any other change to avoid the occurrence of the undefined state.

 

(a) Logic diagram


S	R	Q	Q'
1	0	1	0
0	0	1	0 (after $S = 1, R = 0$)
0	1	0	1
0	0	0	1 (after $S = 0, R = 1$)
1	1	0	0 (forbidden)

(b) Function table

6

SR Latch with NAND Gates

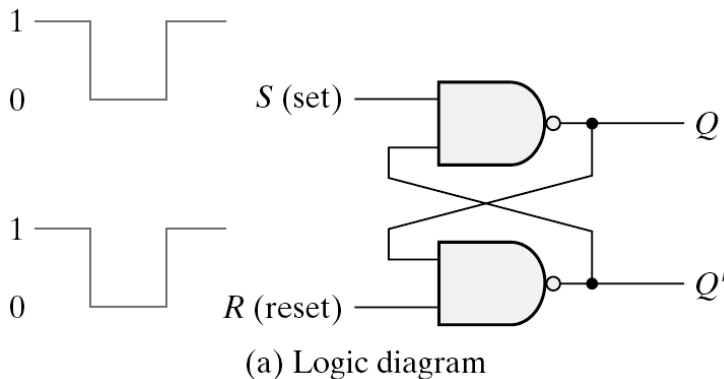- Latch can be formed by two cross-coupled NAND gates
 - $(S, R) = (1, 1)$: no operation (Q and Q' state unchanged)
 - $(S, R) = (1, 0)$: reset state ($Q = 0$ and $Q' = 1$)
 - $(S, R) = (0, 1)$: set state ($Q = 1$ and $Q' = 0$)
 - $(S, R) = (0, 0)$: undefined state ($Q = Q' = 1$)
 - The (S, R) must go back to $(1, 1)$ before any other change to avoid the occurrence of the undefined state.




S	R	Q	Q'
1	0	0	1
1	1	0	1 (after $S = 1, R = 0$)
0	1	1	0
1	1	1	0 (after $S = 0, R = 1$)
0	0	1	1 (forbidden)

(b) Function table

7

SR Latch with Control

 - SR latch with control input
 - $En = 0$, no change
 - $En = 1$, operate as normal SR latch



En	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; reset state
1	1	0	$Q = 1$; set state
1	1	1	Indeterminate


(b) Function table

8

D Latch


■ D Latch

 - D latch can eliminate the undesirable conditions of the indeterminate state in the SR latch
- D: data
- $D \Rightarrow Q$ when $En = 1$; no change when $En = 0$
- A *transparent* latch when $En = 1$




9


Graphic Symbols for Latches

 

NOR

 

NAND

 


Trigger

- A trigger
 - The state of a latch or flip-flop is switched by a change of the control input. This momentary change is called trigger.
- Level triggered – latches
 - The state transition starts as soon as clock is during logic 1 or logic 0 level.
 - The change of input makes the combination logic keep changing with the input latch at logic 1 or logic 0.
- Edge triggered – Flip-Flops
 - The state transition starts only at positive or negative edge of the clock signal.
 - The edge trigger flip-flops will isolate the input changes (current state) and output driving logic (previous state).

11

Edged-Triggered Flip-Flops

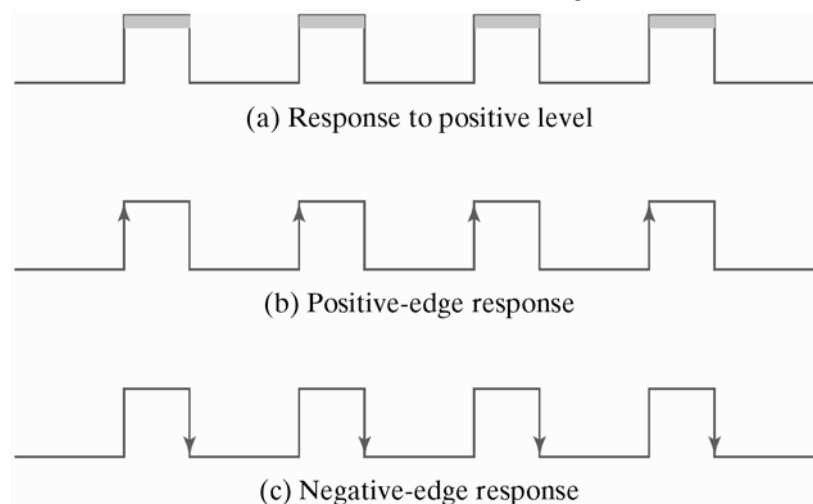
- If level-triggered latches are used,
 - The output result will affect the inputs through the feedback path and cause instability problem.
- If edge-triggered latches are used,
 - the output of flip-flop is isolated from being affected by the input signals, and
 - the state transition happens only at the clock edge.



12

Edge-Triggered D Flip-Flop


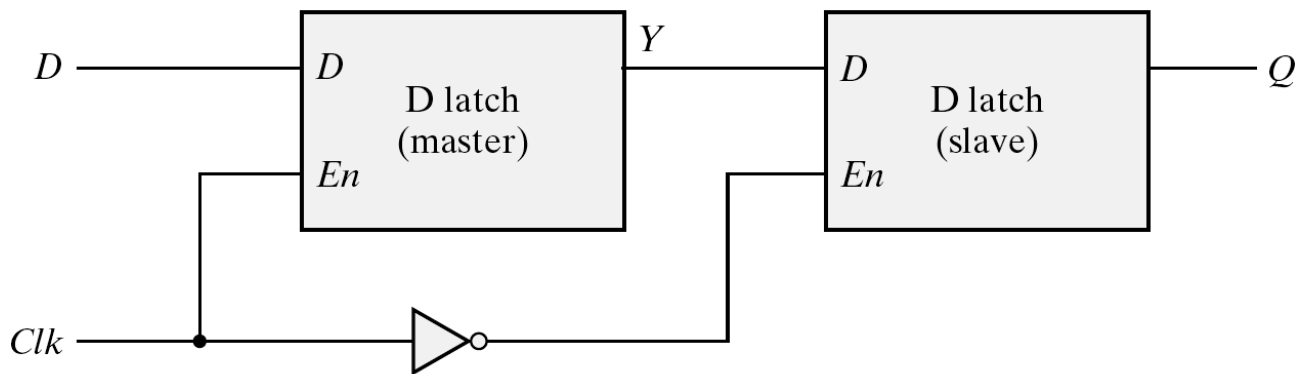
- Master-slave D flip-flop is formed by two separate latches and one inverter.
 - A master D latch (positive-level triggered)
 - A slave D latch (negative-level triggered)



13

Edge-Triggered D Flip-Flop

  
- Two stage operations
 - $CP = 1$:
 - Master D latch active: $(S, R) \Rightarrow (Y, Y')$;
 - Slave D latch inactive: (Q, Q') holds
 - $CP = 0$:
 - Master D latch inactive: (Y, Y') holds;
 - Slave D latch active: $(Y, Y') \Rightarrow (Q, Q')$
- (S, R) could not affect (Q, Q') directly.
- The state changes at the negative edge transition of CP.



14

Edge-Triggered Flip-Flops

 
- Edge-triggered flip-flops
 - the state changes during a clock-pulse transition
- A D-type positive-edge-triggered flip-flop with three SR latches.





15

Edge-Triggered Flip-Flops with Three Latches

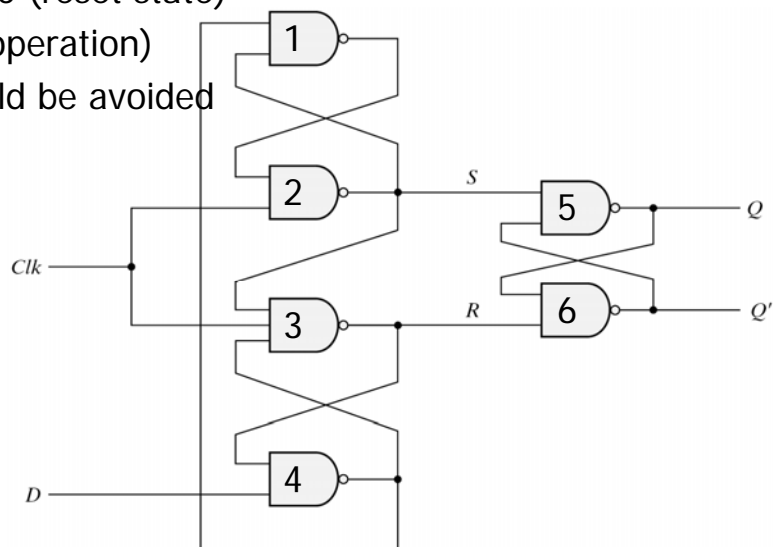- Output Latches (5)(6)
 - $Clk = 0$: $(S, R) = (1, 1)$, no operation
 - $Clk = 1$: operates as a normal latch
 - $(S, R) = (0, 1)$: $Q = 1$ (set state)
 - $(S, R) = (1, 0)$: $Q = 0$ (reset state)
 - $(S, R) = (1, 1)$: (no operation)
 - $(S, R) = (0, 0)$: should be avoided



  

17

Edge-Triggered Flip-Flops with Three Latches

■ Input latches (1)(2)(3)(4)

– $Clk = 0$: $(S, R) = (1, 1)$

■ $D = 0$ output of (1) = 0, output of (4) = 1

■ $D = 1$ output of (1) = 1, output of (4) = 0

– $Clk = 1$:

■ $D = 0$ output of (1) = 0, output of (4) = 1

$\Rightarrow (S, R) = (1, 0)$

$\Rightarrow Q = 0$

■ $D = 1$ output of (1) = 1, output of (4) = 0

$\Rightarrow (S, R) = (0, 1)$

$\Rightarrow Q = 1$


■ Positive transition of clock (Clk) transfers the input data D to output Q .

■ A negative transition of clock (Clk) does not affect the output

18

Setup Time/Hold Time

 - The setup time
 - D input must be maintained at a constant value prior to the application of the positive *Clk* pulse.
 - Equals the propagation delay through gates 4 and 1
 - data to the internal latches
- The hold time
 - D input must not change after the application of the positive *Clk* pulse
 - Equals the propagation delay of gate 3
 - clock to the internal latch




Edge-Triggered Flip-Flops with Three Latches


- Summary
 - $Clk = 0$: $(S, R) = (1, 1)$, no state change
 - $Clk = \uparrow$: state change once
 - $Clk = 1$: state holds
 - To eliminate the feedback problems in sequential circuits
- All flip-flops must make their transition at the same time.

Other Flip-Flops

 - The edge-triggered D flip-flops is the most economical and efficient because it requires the smallest number of gates.
- Other two flip-flops widely used in the design of digital systems are – *JK-flip-flops* and *T flip-flops*.



(a) Positive-edge

 


(a) Negative-edge


21

JK Flip-Flop

■ JK Flip-Flop

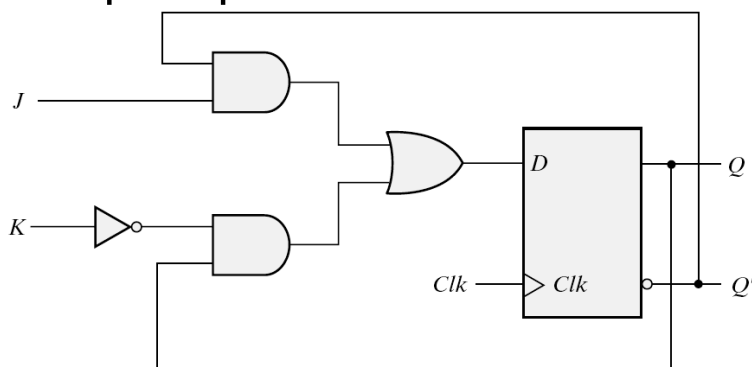

(a) Circuit diagram

 

(b) Graphic symbol


- $D = JQ' + K'Q$
 - $J = 0, K = 0: D = Q$, no change (no operation)
 - $J = 0, K = 1: D = 0 \Rightarrow Q = 0$ (reset state)
 - $J = 1, K = 0: D = 1 \Rightarrow Q = 1$ (set state)
 - $J = 1, K = 1: D = Q' \Rightarrow Q = Q'$ (complement state)

22


T Flip-Flop

■ T flip-flop

 - T flip-flop is a complementing flip-flop controlled by input T.




(a) From JK flip-flop

 

 (b) From D flip-flop

$$D = T \oplus Q = TQ' + T'Q$$

- $T = 0$: $D = Q$, no change (no operation)
- $T = 1$: $D = Q' \Rightarrow Q = Q'$ (complement state)



(c) Graphic symbol

23

Characteristic Tables

JK Flip-Flop			
J	K	$Q(t + 1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

– D Flip-Flop

- $Q(t + 1) = D$

– JK Flip-Flop

- $Q(t + 1) = JQ' + K'Q$

– T Flip-Flop

- $Q(t + 1) = T \oplus Q$

D Flip-Flop

D	$Q(t + 1)$	
0	0	Reset
1	1	Set

T Flip-Flop

T	$Q(t + 1)$	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

24



Direct Inputs

- When power is on, the state of flip-flop is unknown. The direct input will force the flip-flops in the system to a known starting state before the system starts.
- *Preset* or (*Direct Set*) sets the flip-flop to 1
- *Clear* or (*Direct Reset*) sets the flip-flop to 0

25

Asynchronous Set/Reset

- D Flip-Flop with asynchronous reset

  


R	Clk	D	Q	Q'
0	X	X	0	1
1	\uparrow	0	0	1
1	\uparrow	1	1	0

(b) Function table

26

Analysis of Clocked Sequential Circuit

 - A sequential circuit
 - (inputs, current state) \Rightarrow (output, next state)
 - a state transition table or state transition diagram
- An example :



27

State Equations

- A *state equation (transition equation)* specifies the next state as a function of the present state and input.
- State equation of an example in the previous slide.
 - $A(t+1) = A(t)x(t) + B(t)x(t)$
 - $B(t+1) = A'(t)x(t)$
- A compact form
 - $A(t+1) = Ax + Bx$
 - $B(t+1) = A'x$
- The output equation
 - $y(t) = (A(t) + B(t))x'(t)$
 - $y = (A + B)x'$

28

State Table

- A *state table (transition table)* enumerates the time sequence of inputs, outputs, and flip-flop state.
- State table consists of four sections labeled
 - *present state*
 - *input*
 - *next state*
 - *output*

Table 5.2

State Table for the Circuit of Fig. 5.15


Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

29

State Diagram

- State transition diagram
 - a circle: a state
 - a directed lines connecting the circles: the transition between the states
- Each directed line is labeled 'inputs/outputs'
 - a logic diagram \Leftrightarrow a state table \Leftrightarrow a state diagram
- Derive the state diagram from state table

Present State		Next State				Output	
		x = 0		x = 1		x = 0	x = 1
A	B	A	B	A	B	y	y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

 

30

Flip-Flop Input Equations

- Flip-flop *input equations (excitation equations)* describes the part of circuit that generates the inputs to flip-flops

- $D_A = Ax + Bx$ (1)


- $D_B = A'x$ (2)

- The *output equations*

- $y = (A + B)x'$ (3)

- Input equations* and *output equations* provide the necessary information for drawing the logic diagram of the sequential circuit.

 - The *input equations* are identical to the corresponding *state equations* only for D Flip-flop.



31



Analysis with D flip-flops

- The input equation

- $D_A = A \oplus x \oplus y$

- The state equation

- $A(t + 1) = A \oplus x \oplus y$

  

Present state	Inputs		Next state
A	x	y	A
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

2


Analysis with JK/T flip-flops

- For JK flip-flop and T flip-flop, the input equations and state equations are not the same.
 - 1. Determine the flip-flop input function in terms of the present states and input variables.
 - 2. List the binary values of each input equations.
 - 3. Use the corresponding flip-flop characteristic table to determine the next state.
 - 4. Compute output signals.
 - 5. Draw State Diagram.

- An example: JK Flip-Flop circuit

Note:

$$Q(t + 1) = JQ' + K'Q$$

 

33

Analysis with JK flip-flops

- Input equations of the circuit

$$J_A = B, K_A = Bx' \quad (1)$$

$$J_B = x', K_B = A'x + Ax' \quad (2)$$

- State table

- Or, derive the state equations using characteristic equations of the flip-flop.

JK Flip-Flop			
J	K	Q(t + 1)	
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement

Table 5.4

State Table for Sequential Circuit with JK Flip-Flops

Present State			Input		Next State		Flip-Flop Inputs			
A	B		x		A	B	J _A	K _A	J _B	K _B
0	0		0		0	1	0	0	1	0
0	0		1		0	0	0	0	0	1
0	1		0		1	1	1	1	1	0
0	1		1		1	0	1	0	0	1
1	0		0		1	1	0	0	1	1
1	0		1		1	0	0	0	0	0
1	1		0		0	0	1	1	1	1
1	1		1		1	1	1	0	0	0

34


Analysis with JK flip-flops

- Characteristic equation of JK flip-flops
 - $Q(t + 1) = JQ' + K'Q$ (3)
- Evaluation of the state equations from the characteristic equations
 - JK flip-flop A : $A(t + 1) = J_A A' + K_A' A$ (4)
 - JK flip-flop B : $B(t + 1) = J_B B' + K_B' B$ (5)
- Substituting the values of J_A , K_A , J_B , and K_B from the input equations (1)(2) to get the state equations of the circuit
 - $A(t + 1) = BA' + (Bx')'A = A'B + AB' + Ax$ (6)
 - $B(t + 1) = x'B' + (A \oplus x)'B = B'x' + ABx + A'Bx'$ (7)

35

Analysis with JK flip-flops


 
- Using the state equation or state table (preferred) of the circuit to draw the state transition diagram.



36

Analysis with T flip-flops

  - The characteristic equation of the T flip-flops
 - $Q(t + 1) = T \oplus Q = TQ' + T'Q$



37

Analysis with T flip-flops

- The input and output functions
 - $T_A = Bx$
 - $T_B = x$
 - $y = AB$
- The state equations
 - $A(t + 1) = (Bx)'A + (Bx)A'$
 $= AB' + Ax' + A'Bx$
 - $B(t + 1) = x \oplus B$


State Table for Sequential Circuit with T Flip-Flops

Present State		Input			Next State		Output
A	B	x	T _A	T _B	A	B	y
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	0	0	0	1	0
0	1	1	1	1	1	0	0
1	0	0	0	0	1	0	0
1	0	1	0	1	1	1	0
1	1	0	0	0	1	1	1
1	1	1	1	1	0	0	1

38

Mealy Model


 
- *Mealy model*: the outputs are functions of both the present states and inputs
 - the outputs may change if the inputs change during the clock pulse period
 - the outputs may have momentary false values unless the inputs are synchronized with the clocks
- An example:



39

Moore Model

  
- *Moore model*: the outputs are functions of the present states only. The outputs are synchronous with the clock.
- An example:




40

Moore Model v.s Mealy Model

■ Mealy machine

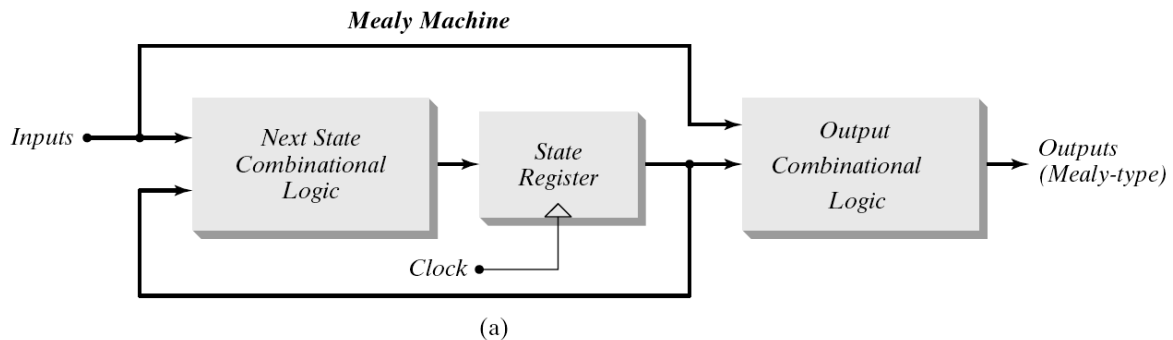

■ Moore machine

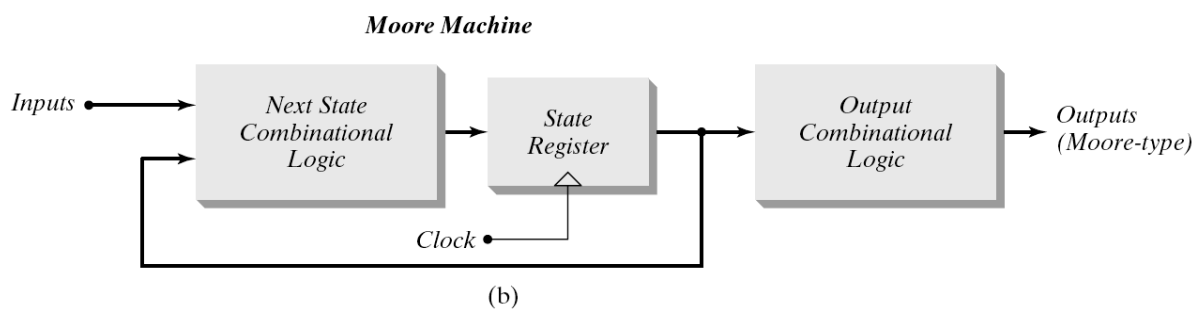

41

Synthesizable HDL Models of Sequential Circuits

■ Behavioral Modeling

■ Example: Two ways to provide free-running clock

<pre>initial begin clock = 1'b0; repeat (30) #10 clock = ~clock; end</pre>	<pre>initial begin clock = 1'b0; end initial 300 \$finish; always #10 clock = ~clock;</pre>
--	--

■ Example: Another way to describe free-running clock

```
initial begin clock = 0; forever #10 clock = ~clock; end
```

42

Behavioral Modeling

■ **always** statement

```
always @ (event control expression) begin  
    // Procedural assignment statements that execute when the condition is met  
end
```

■ Examples:

```
always @ (A or B or C)
```

```
always @(posedge clock or negedge reset) // Verilog 1995
```

```
always @(posedge clock, negedge reset) // Verilog 2001, 2005
```

Two procedural blocking assignments:

```
B = A  
C = B + 1
```

Two nonblocking assignments:

```
B <= A  
C <= B + 1
```

43

Procedural Assignment

- Procedural assignments update the values of registers under the control of two kinds of procedure assignment .
- Blocking procedure assignments are executed sequentially in the order they are listed.
- Non-Blocking procedure assignments evaluate the expressions on the right-hand side, but do not make the assignment to the left-hand side until all expressions are evaluated.

<pre>initial begin A=1; B=2; C=0; end always c = #5 ~c;</pre>	<pre>always @(posedge c) begin B=A; // B=1 C=B+1; // C=2 end</pre> <p>Blocking</p>	<pre>always @(posedge c) begin B<=A; // B=1 C<=B+1; // C=3 end</pre> <p>Non-Blocking</p>
--	---	---

44

Flip-Flops and Latches

■ HDL Example 5.1


// Description of D latch (transparent latch)
// See Fig. 5-6

```
module D_latch (Q, D, enable);
  output      Q;
  input       D, enable;
  reg         Q;
```

```
  always @ (enable or D)
    if (enable) Q <= D;    // Alternative: if (enable == 1) Q <= D;
endmodule
```

// Alternative syntax (Verilog 2001, 2005)
 
```
module D_latch (output reg Q, input enable, D);
  always @ (enable, D)
    if (enable) Q <= D;    // No action if enable is not asserted
endmodule
```



45

Flip-Flops and Latches

■ HDL Example 5.2

// Description of D flip-flop without reset (See Fig. 5-11)

```
module D_FF (Q, D, Clk);
  output      Q;
  input       D, Clk;
  reg         Q;
  always @ (posedge Clk)
    Q <= D;
endmodule
```

// Description of D flip-flop with asynchronous reset, Verilog 2001, 2005

```
module DFF (output reg Q, input D, Clk, rst);
  always @ (posedge Clk, negedge rst)
    if (~rst) Q <= 1'b0;    // same as: if (rst == 0) Q <= 1'b0;
    else Q <= D;
endmodule
```

46

Characteristic Equation

$Q(t + 1) = Q \oplus T \quad \Rightarrow$ For a T flip-flop

$Q(t + 1) = JQ' + K'Q \quad \Rightarrow$ For a JK flip-flop

■ HDL Example 5.3

```
// T flip-flop from D flip-flop and gates
module TFF (output Q, input T, Clk,
rst);
```

```
  wire DT;
```

```
  assign DT = Q ^ T;
```

```
// Instantiate the D flip-flop
```

```
  DFF TF1 (Q, DT, Clk, rst);
```

```
endmodule
```

```
// JK flip-flop from D flip-flop and gates
```

```
module JKFF (output reg Q, input J,
K, Clk, rst);
```

```
  wire JK;
```

```
  assign JK = (J & ~Q) | (~K & Q);
```

```
// Instantiate D flip-flop
```

```
  DFF JK1 (Q, JK, Clk, rst);
```

```
endmodule
```

```
// D flip-flop (V2001, V2005)
```

```
module DFF (output reg Q, input D, Clk,
rst);
```

```
  always @ (posedge Clk, negedge rst)
```

```
    if (~rst) Q <= 1'b0;
```

```
    else Q <= D;
```

```
endmodule
```

47

HDL Example 5-4

```
// Function description of JK flip-flop (V2001, V2005)
```

```
module JK_FF (input J, K, Clk, output reg Q, output Q_b);
```

```
  assign Q_b = ~Q;
```

```
  always @ (posedge Clk)
```

```
    case ({J, K})
```

```
      2'b00: Q <= Q;           // No change
```

```
      2'b01: Q <= 1'b0;       // Set
```

```
      2'b10: Q <= 1'b1;       // Reset
```

```
      2'b11: Q <= ~Q;         // Complement
```

```
    endcase
```

```
endmodule
```


HDL Example 5.5: Mealy HDL model

```
// Mealy FSM zero detector
module Mealy_Zero_Detector (
  output reg    y_out,
  input         x_in, clock, reset
);
  reg [1: 0]     state, next_state;
  parameter     S0 = 2'b00, S1 =
2'b01, S2 = 2'b10, S3 = 2'b11;

  always @ (posedge clock, negedge
reset) // state transition
    if (reset == 0) state <= S0;
    else state <= next_state;

  always @ (state, x_in) // Form the
next state
    case (state)
      S0: if (x_in) next_state = S1;
         else next_state = S0;
```

```
      S1: if (x_in) next_state = S3;
         else next_state = S0;
      S2: if (~x_in) next_state = S0;
         else next_state = S2;
      S3: if (x_in) next_state = S2;
         else next_state = S0;
    endcase

    always @ (state, x_in) // Form the
output
    case (state)
      S0: y_out = 0;
      S1, S2, S3: y_out = ~x_in;
    endcase
endmodule
```

49

HDL Example 5.5 (Cont'd)

```
module t_Mealy_Zero_Detector;
  wire    t_y_out;
  reg     t_x_in, t_clock, t_reset;

  Mealy_Zero_Detector M0 (t_y_out,
t_x_in, t_clock, t_reset);


  initial #200 $finish;
  initial begin t_clock = 0; forever #5
t_clock = ~t_clock; end

  initial fork
    t_reset = 0;
    #2 t_reset = 1;
    #87 t_reset = 0;
    #89 t_reset = 1;
    #10 t_x_in = 1;
    #30 t_x_in = 0;
    #40 t_x_in = 1;
```

```
    #50 t_x_in = 0;
    #52 t_x_in = 1;
    #54 t_x_in = 0;
    #80 t_x_in = 1;
    #100 t_x_in = 0;
    #120 t_x_in = 1;
    #160 t_x_in = 0;
    #170 t_x_in = 1;
  join
endmodule
```

50

Mealy_Zero_Detector

 

51

HDL Example 5-6: Moore Model FSM

// Moore FSM (See state diagram in Fig. 5-19)

module Moore_Model_Fig_5_19 (

output [1: 0] y_out,

input x_in, clock, reset

);

reg [1: 0] state;

parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;

always @ (posedge clock, negedge reset)

if (reset == 0) state <= S0; // Initialize to state S0

else case (state)

 S0: **if** (~x_in) state <= S1; **else** state <= S0;

 S1: **if** (x_in) state <= S2; **else** state <= S3;



 S2: **if** (~x_in) state <= S3; **else** state <= S2;

 S3: **if** (~x_in) state <= S0; **else** state <= S3;

endcase


assign y_out = state; // Output of flip-flops

endmodule

  

52

Simulation Output of HDL Example 5-6

 

53


Structural Description of Clocked Sequential Circuits

```

module Moore_Model_Fig_5_20 (
  output      y_out,
  input       x_in, clock, reset
);
  reg [1: 0]   state;
  parameter   S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;

  always @ (posedge clock, negedge reset)
    if (reset == 0) state <= S0;    // Initialize to state S0
    else case (state)
      S0: if (x_in) state <= S1; else state <= S0;
      S1: if (x_in) state <= S2; else state <= S1;
      S2: if (x_in) state <= S3; else state <= S2;
      S3: if (x_in) state <= S0; else state <= S3;
    endcase

     assign y_out = (state == S3);    // Output of flip-flops
endmodule
  
```



54

HDL Example 5-7 (Cont'd)

```


module Moore_Model_STR_Fig_5_20 (
  output      y_out, A, B,
  input       x_in, clock, reset
);
  wire        TA, TB;

  // Flip-flop input equations
  assign TA = x_in & B;
  assign TB = x_in;
  //output equation
  assign y_out = A & B;
  // Instantiate Toggle flip-flops
  Toggle_flip_flop_3 M_A (A, TA, clock, reset);
  Toggle_flip_flop_3 M_B (B, TB, clock, reset);

endmodule

module t_Moore_Fig_5_20;
  wire  t_y_out_2, t_y_out_1;
  reg   t_x_in, t_clock, t_reset;

```

 

55

HDL Example 5-7 (Cont'd)

```

Moore_Model_Fig_5_20      M1(t_y_out_1, t_x_in, t_clock, t_reset);
Moore_Model_STR_Fig_5_20  M2 (t_y_out_2, A, B, t_x_in, t_clock, t_reset);

```

```

initial #200 $finish;
initial begin
  t_reset = 0;
  t_clock = 0;
  #5 t_reset = 1;
  repeat (16)
    #5 t_clock = ~t_clock;
end

```

```


initial begin
  t_x_in = 0;
  #15 t_x_in = 1;
  repeat (8)
    #10 t_x_in = ~t_x_in;
  end
endmodule

```

56

State Reduction and Assignment

 
- m flip-flops produce 2^m states.
- State Reduction
 - may result in a reduction in the number of flip-flops and the number of gates
- An example of state diagram:
- Note: different input sequence results in different output sequence.



57

State Reduction

- Input/Output sequences are the most important!
 - Each input of 0 or 1 produces an output of 0 or 1 and causes the circuit goes to the next state.
 - state a a b c d e f f g f g a
 - input 0 1 0 1 0 1 1 0 1 0 0
 - output 0 0 0 0 0 1 1 0 1 0 0
 - Only the input-output sequences are important.
 - So, two circuits are equivalent if they have identical outputs for all input sequences.
 - Note: the number of states is not important.

 

58

Equivalent States

- Two states are said to be equivalent:
 - For each member of the set of inputs, they give exactly the same output and send the circuit to the same state or to an equivalent state.
 - When two states are equivalent, one of them can be removed.

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>g</i>	<i>f</i>	0	1
<i>g</i>	<i>a</i>	<i>f</i>	0	1

59

The Reduced Finite State Machine

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>d</i>	0	1
<i>e</i>	<i>a</i>	<i>d</i>	0	1


state	a a b c d e f f g f g a
input	0 1 0 1 0 1 1 0 1 0 0
output	0 0 0 0 0 1 1 0 1 0 0

state	a a b c d e d d e d e a
input	0 1 0 1 0 1 1 0 1 0 0
output	0 0 0 0 0 1 1 0 1 0 0

60

The Reduced Finite State Machine

 - The checking of each pair of states for possible equivalence can be done systematically (in Chap. 9-5)
- The unused states are treated as don't-care conditions .
- The more unused states \Rightarrow the more don't care conditions \Rightarrow the fewer combinational gates are required.



61

State Assignment

- For a circuit with m states, we need at least n -bit, where $2^n \geq m$, to encode the states.
- Three possible binary state assignments for the previous example:

Three Possible Binary State Assignments

State	Assignment 1, Binary	Assignment 2, Gray Code	Assignment 3, One-Hot
<i>a</i>	000	000	00001
<i>b</i>	001	001	00010
<i>c</i>	010	011	00100
<i>d</i>	011	010	01000
<i>e</i>	100	110	10000

62

State Assignment

- Any binary number assignment is satisfactory as long as each state is assigned a unique number
- The state table uses binary assignment 1:

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>d</i>	0	1
<i>e</i>	<i>a</i>	<i>d</i>	0	1

63

Design Procedure

- The design of synchronous sequential circuit consists of
 - Choosing flip-flops
 - Depending on the number of states
 - Finding the combinational logic
 - Evaluation of input equations and output equations
- Recommended steps of the design procedures for synchronous sequential circuits
 - the word description of the circuit behavior (a state diagram)
 - state reduction if necessary
 - assign binary values to the states
 - obtain the binary-coded state table
 - choose the type of flip-flops
 - derive the simplified flip-flop input equations and output equations
 - draw the logic diagram

64

Synthesis Using D Flip-Flops

- An example: state diagram and state table

 


Table 5.11
State Table for Sequence Detector

Present State		Input <i>x</i>	Next State		Output <i>y</i>
<i>A</i>	<i>B</i>		<i>A</i>	<i>B</i>	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

65


Synthesis Using D Flip-Flops

- The flip-flop's input equations
 - $A(t + 1) = D_A(A, B, x) = \Sigma(3, 5, 7)$
 - $B(t + 1) = D_B(A, B, x) = \Sigma(1, 5, 7)$
- The output equation
 - $y(A, B, x) = \Sigma(6, 7)$
- Logic minimization using the K map
 - $D_A = Ax + Bx$
 - $D_B = Ax + B'x$
 - $y = AB$

66

Sequence Detector

- The logic diagram:

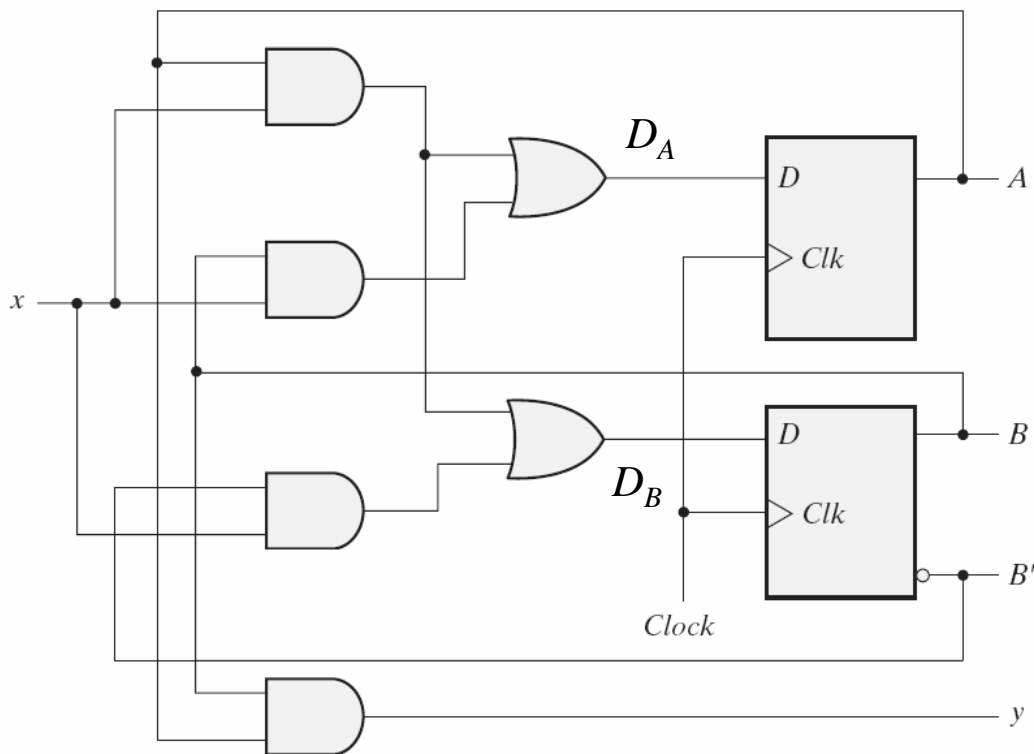

67

Excitation Tables

- A state diagram \Rightarrow flip-flop input functions
 - straightforward for D flip-flops
 - we need excitation tables for JK and T flip-flops

Table 5.12

Flip-Flop Excitation Tables

$Q(t)$	$Q(t+1)$	J	K	$Q(t)$	$Q(t+1)$	T
0	0	0	X	0	0	0
0	1	1	X	0	1	1
1	0	X	1	1	0	1
1	1	X	0	1	1	0

(a) JK

(b) T

68

Synthesis Using JK Flip-Flops

- The synthesis procedure is the same as DFF.
- The state table and JK flip-flop inputs

Table 5.13


State Table and JK Flip-Flop Inputs

Present State		Input	Next State		Flip-Flop Inputs			
A	B		A	B	J_A	K_A	J_B	K_B
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

69


Maps for JK Input Equations

 – $J_A = Bx'$; $K_A = Bx$ – $J_B = x$; $K_B = (A \oplus x)'$



70

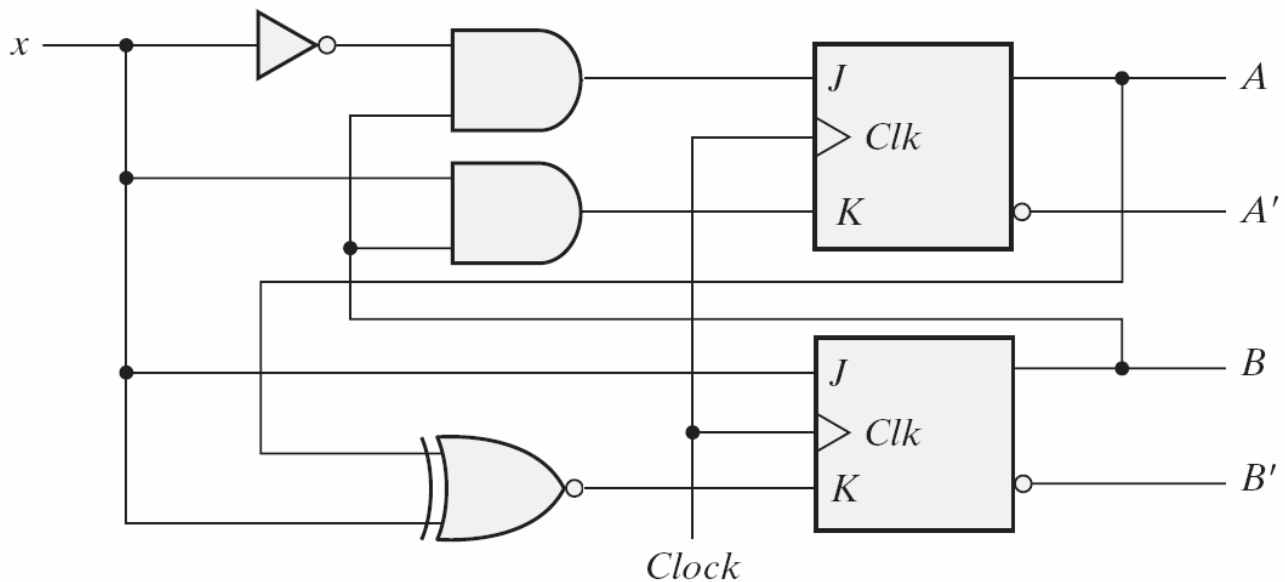Logic Diagram for Sequential Circuit with JK Flip-Flops




71

Synthesis Using T flip-flops

- An n -bit binary counter
 - the state diagram
 - no inputs (except for the clock input)

 State diagram of three-bit binary counter



72

The State Table and The Flip-Flop Inputs


Table 5.14

State Table for Three-Bit Counter

Present State			Next State			Flip-Flop Inputs		
A_2	A_1	A_0	A_2	A_1	A_0	T_{A2}	T_{A1}	T_{A0}
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	1	1
1	1	1	0	0	0	1	1	1

73

Maps of Three-Bit Binary Counter

 

74

Logic Simplification Using The K Map

- $T_{A2} = A_1A_2$
- $T_{A1} = A_0$
- $T_{A0} = 1$

■ The logic diagram

