

HW7

1. The memory units that follow are specified by the number of words times the number of bits per word. (1) How many address lines and input-output lines are needed in each case? (2) Give the number of bits stored in the memories in each case. (a) $2M \times 16$ (b) $2G \times 8$.
2. Design a 8×5 RAM.
3. A 12-bit Hamming code word containing 8 bits of data and 4 parity bits is read from the memory. What is the original 8-bit data word that was written into memory if the 12-bit word read out is as: (a) 011001000110 (b) 101110110100
4. Tabulate the truth table for an 8×4 ROM that implements the Boolean functions.
 - (a) $A(X, Y, Z) = \sum m(1, 2, 4)$
 - (b) $B(X, Y, Z) = \sum m(3, 5, 7)$
 - (c) $C(X, Y, Z) = \sum m(1, 2, 6, 7)$
 - (d) $D(X, Y, Z) = \sum m(2, 3, 5, 6, 7)$
5. FPGA: The logic cell has four inputs (A, B, C, D) and one output (Z).
 - (a) Draw the logic diagram of a simple logic cell with 4-bit inputs and 1-bit outputs.
 - (b) Explain how the logic cell can finish the sum function in a full adder. ($Z = A + B + C$)

