

HW6

1. The content of a 4-bit shift register is initially 1011. The register is shifted five times to the left with the serial input 101110 (left bit is first input). What is the content of the register after *each* shift?

initially :1011 input:101110

shift 1 :0111

shift 2 :1110


shift 3 :1101

shift 4 :1011

shift 5 :0111

2. Draw the logic diagram of a four-bit register with four D flip-flops and four 4x1 multiplexers with mode selection S_1 and S_0 . The register operates according to the following function table.

S_1	S_0	Register Operation
0	0	Load parallel data
0	1	Clear register to 0 (synchronous with the clock)
1	0	Complement the four outputs
1	1	No change

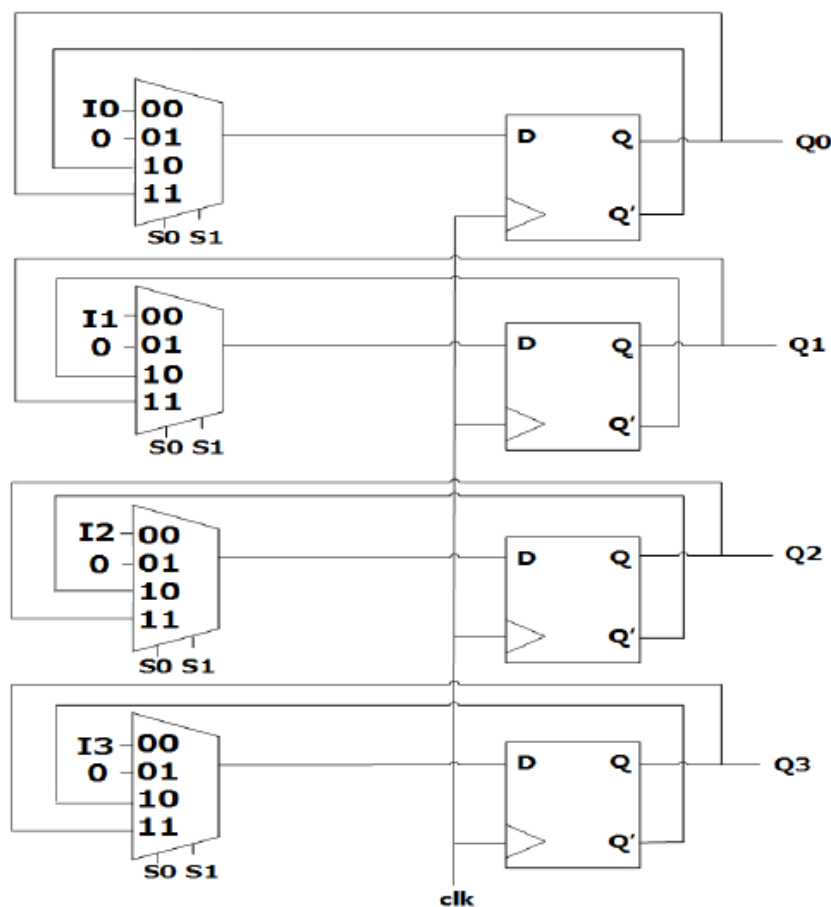

3. Show that a Johnson counter with n flip-flops produces a sequence of $2n$ states. List the 10 states produced with five flip-flops and the Boolean terms of each of the 10 AND gate outputs.

State 1

CD \ AB	00	01	11	10
00	1	x	x	x
01	x	x	x	x
11	0	x	0	0
10	0	x	x	x

F=0

State 2

CD \ AB	00	01	11	10
00	0	x	x	x
01	x	x	x	x
11	0	x	0	0
10	1	x	x	x

F=0

State 3

CD \ AB	00	01	11	10
00	0	x	x	x
01	x	x	x	x
11	1	x	0	0
10	0	x	x	x

F=0

State 4

CD \ AB	00	01	11	10
00	0	x	x	x
01	x	x	x	x
11	0	x	0	1
10	0	x	x	x

F=0

CD \ AB	00	01	11	10
00	0	0	0	x
01	x	x	0	x
11	x	x	0	x
10	x	x	x	x

F=1

CD \ AB	00	01	11	10
00	0	0	0	x
01	x	x	0	x
11	x	x	0	x
10	x	x	x	x

F=1

CD \ AB	00	01	11	10
00	0	0	0	x
01	x	x	0	x
11	x	x	0	x
10	x	x	x	x

F=1

CD \ AB	00	01	11	10
00	0	0	0	x
01	x	x	0	x
11	x	x	0	x
10	x	x	x	x

F=1

State 5

CD \ AB	00	01	11	10
00	0	x	x	x
01	x	x	x	x
11	0	x	1	0
10	0	x	x	x

F=0

State 6

CD \ AB	00	01	11	10
00	0	x	x	x
01	x	x	x	x
11	0	x	0	0
10	0	x	x	x

F=0

State 7

CD \ AB	00	01	11	10
00	0	x	x	x
01	x	x	x	x
11	0	x	0	0
10	0	x	x	x

F=0

State 8

CD \ AB	00	01	11	10
00	0	x	x	x
01	x	x	x	x
11	0	x	0	0
10	0	x	x	x

F=0

CD \ AB	00	01	11	10
00	0	0	0	x
01	x	x	0	x
11	x	x	0	x
10	x	x	x	x

F=1

CD \ AB	00	01	11	10
00	0	0	0	x
01	x	x	0	x
11	x	x	1	x
10	x	x	x	x

F=1

CD \ AB	00	01	11	10
00	0	0	0	x
01	x	x	1	x
11	x	x	0	x
10	x	x	x	x

F=1

CD \ AB	00	01	11	10
00	0	0	1	x
01	x	x	0	x
11	x	x	0	x
10	x	x	x	x

F=1

State 9

CD \ AB	00	01	11	10
00	0	x	x	x
01	x	x	x	x
11	0	x	0	0
10	0	x	x	x

F=0

CD \ AB	00	01	11	10
00	0	1	0	x
01	x	x	0	x
11	x	x	0	x
10	x	x	x	x

F=1


State 10

CD \ AB	00	01	11	10
00	0	x	x	x
01	x	x	x	x
11	0	x	0	0
10	0	x	x	x

F=0

CD \ AB	00	01	11	10
00	1	0	0	x
01	x	x	0	x
11	x	x	0	x
10	x	x	x	x

F=1

 

Sequence Number	A	B	C	E	F	AND gate for output
1	0	0	0	0	0	$A'F'$
2	1	0	0	0	0	AB'
3	1	1	0	0	0	BC'
4	1	1	1	0	0	CD'
5	1	1	1	1	0	DF'
6	1	1	1	1	1	AF
7	0	1	1	1	1	$A'B$
8	0	0	1	1	1	$B'C$
9	0	0	0	1	1	$C'D$
10	0	0	0	0	1	$D'F$

4. Use D flip-flops and gates to design a binary counter with each of the following repeated binary sequences:

(a) 1, 5, 7

4. (a)

Present State			Next State			Flip-Flop Inputs		
A	B	C	A	B	C	D_A	D_B	D_C
0	0	1	1	0	1	1	0	1
1	0	1	1	1	1	1	1	1
1	1	1	0	0	1	0	0	1

D_A :

A \ BC	00	01	11	10
0	X	1	X	X
1	X	1	0	X

$D_A = B'$

D_B :

A \ BC	00	01	11	10
0	X	0	X	X
1	X	1	0	X

$D_B = AB'$

D_C :

A \ BC	00	01	11	10
0	X	1	X	X
1	X	1	1	X

$D_C = 1$

(b) 0, 2, 4, 6

Present state			Next State			Flip-Flop inputs		
A	B	C	A	B	C	D_A	D_B	D_C
0	0	0	0	1	0	0	1	0
0	1	0	1	0	0	1	0	0
1	0	0	1	1	0	1	1	0
1	1	0	0	0	0	0	0	0

For D_A :

A \ BC	00	01	11	10
0	0	X	X	1
1	1	X	X	0

$$D_A = AB' + A'B$$

For D_B :

A \ BC	00	01	11	10
0	1	X	X	0
1	1	X	X	0

$$D_B = B'$$

For D_C :


A \ BC	00	01	11	10
0	0	X	X	0
1	0	X	X	0

$$D_C = 0$$

5. Frequency divider:

(a) Design a frequency divider to provide the output signal with frequency as 1/8 of the that of the original signal.

(a) use DFF

 

- (b) Design a frequency divider to provide the output signal with frequency as $1/6$ of the that of the original signal.

