

Verilog 2

Hsi-Pin Ma 馬席彬

<http://lms.nthu.edu.tw/course/40757>

Department of Electrical Engineering
National Tsing Hua University


Verilog Description

```

module HalfAdder(a, b, c, s);
  input a, b;
  output c, s; // carry and sum

  assign s = a ^ b;
  assign c = a & b;

endmodule
  
```

 


```

module FullAdder(a, b, cin, cout, s);
  input a, b, cin;
  output cout, s; // carry and sum
  wire g, p; // generate and propagate
  wire cp;

  HalfAdder ha1(.a(a), .b(b), .c(g), .s(p));
  HalfAdder ha2(.a(cin), .b(p), .c(cp), .s(s));
  assign cout = g | cp;

endmodule
  
```

Ripple-Carry Adder (4 / 4)

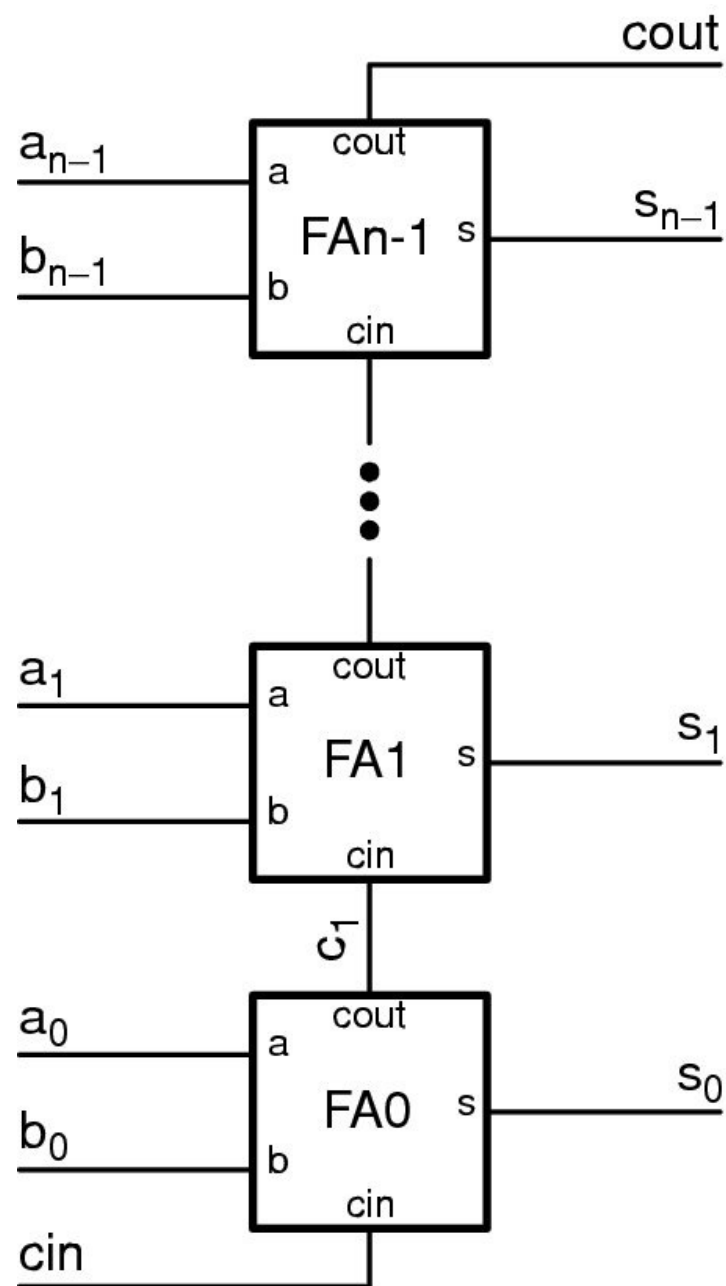

```
module adder(a, b, cin, cout, s);
```

```
parameter n=4;
```

```
input [n-1:0] a, b;
```

```
input cin;
```

```
output reg [n-1:0] s;
```

```
output cout;
```

```
reg [n-1:0] c;
```

```
integer i;
```

```
assign cout = c[4];
```

```
always @*
```

```
    c[0] = cin;
```

```
always @*
```

```
    for (i=0;i<4;i=i+1)
```

```
        {c[i+1],s[i]} = a[i] + b[i] + c[i];
```


```
endmodule
```

```
assign {c[1],s[0]} = a[0] + b[0] + c[0];
assign {c[2],s[1]} = a[1] + b[1] + c[1];
assign {c[3],s[2]} = a[2] + b[2] + c[2];
assign {c[4],s[3]} = a[3] + b[3] + c[3];
```



Multi-bit Binary Adder

behavioral model

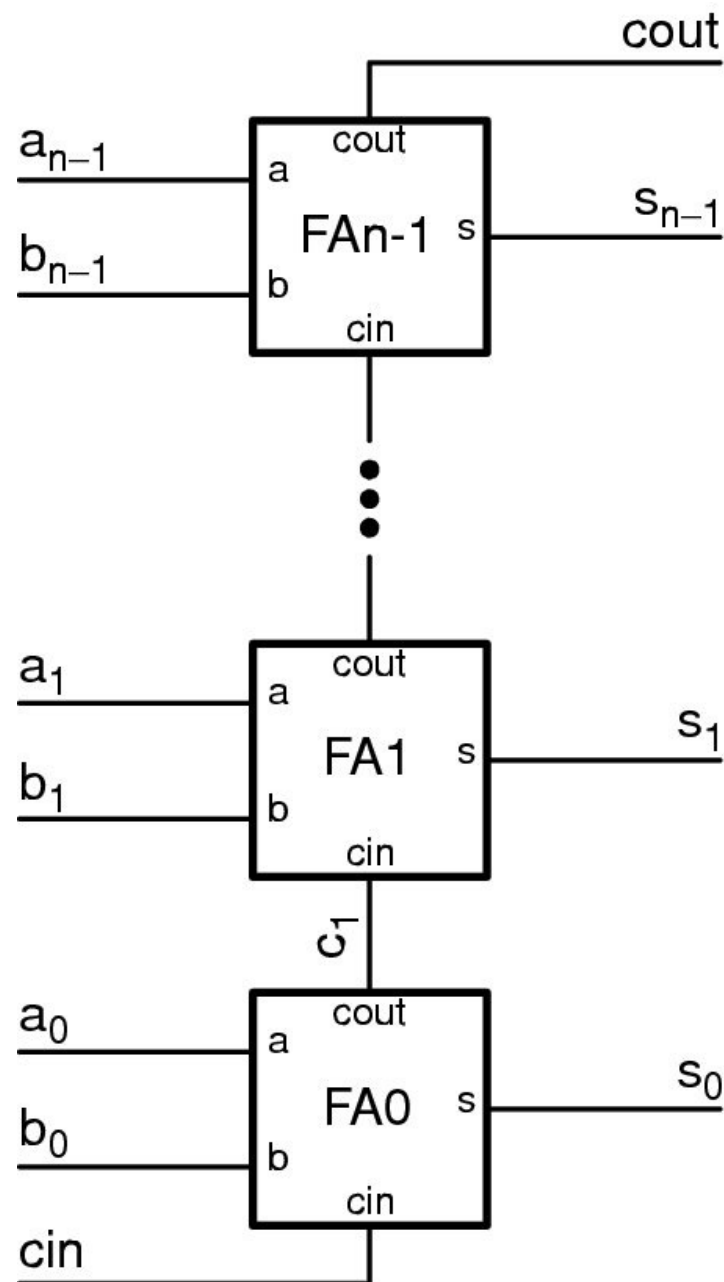

```


module Adder1(a, b, cin, cout, s);
  parameter n=8;
  input [n-1:0] a, b;
  input cin;
  output [n-1:0] s;
  output cout;

  assign {cout, s} = a + b + cin;

endmodule
  
```

Maximun Unit

$$y = \max\{a, b\}$$

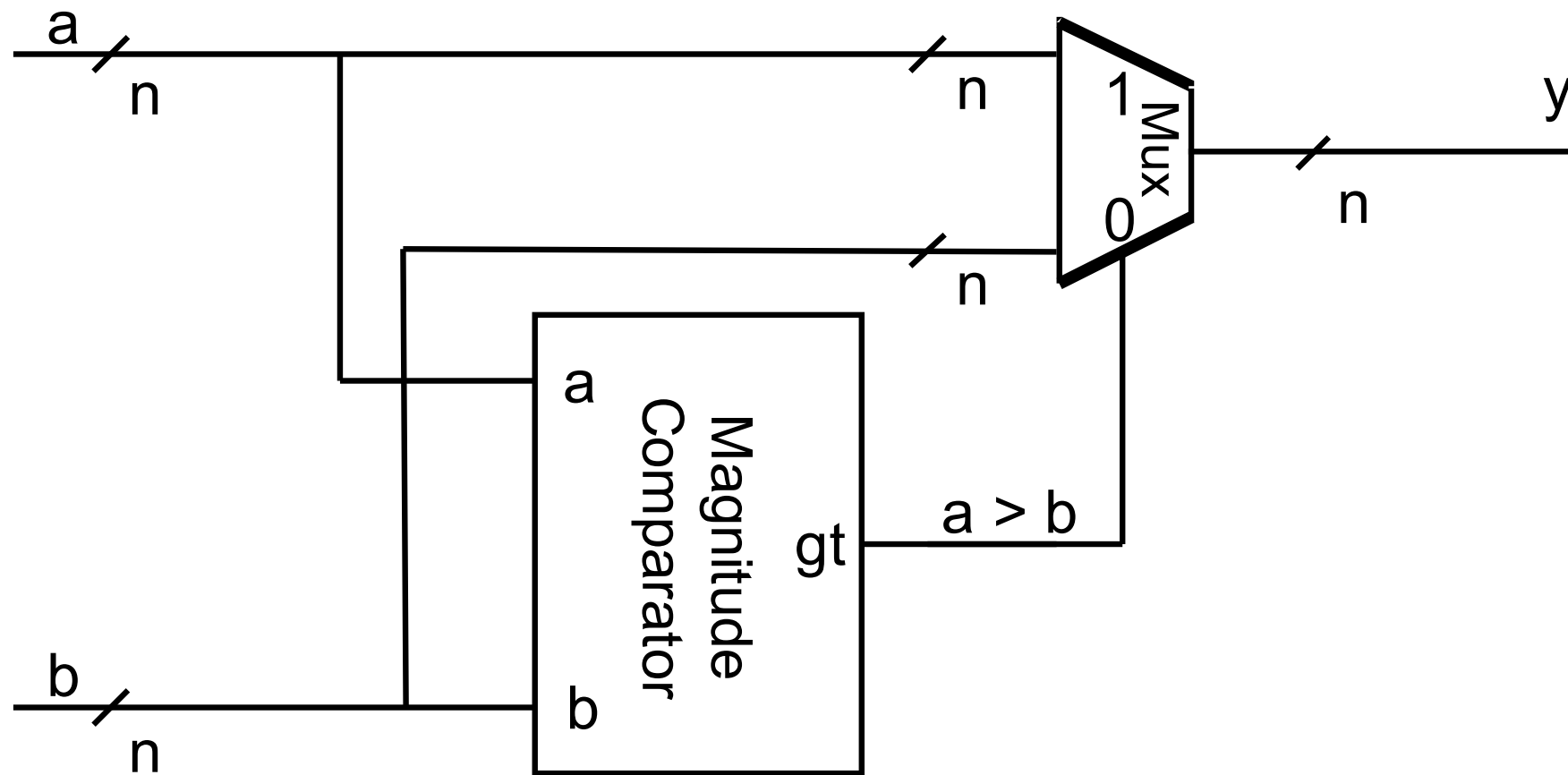

Verilog Module Construction


- Separate flip-flops with other logics (two types)
 - flip-flops (edge-triggered with clock, reset)
 - combinational logics (level sensitive)
- Combinational logics
 - simple logics (AND, OR, NOT)
 - coder / decoder (mapping, addressing)
 - comparison (conditional / equality test)
 - selection (select correct results, MUX)
 - arithmetic functions and superposition (+, -, *, binary shift)
- Finite state machine (FSM)

Magnitude Comparator

```
module MagComp_b(a, b, gt);  
parameter k=8;  
input [k-1:0] a, b;  
output gt;  
  
assign gt = (a > b) ? 1 : 0;  
  
endmodule
```


D-type Flip Flop
 
```
module dff(  
    q, // output  
    d, // input  
    clk, // global clock  
    rst_n // active low reset  
);  
  
output q; // output  
input d; // input  
input clk; // global clock  
input rst_n; // active low reset  
  
reg q; // output (in always block)  
  
always @(posedge clk or negedge rst_n)  
    if (~rst_n)  
        q<=0;  
    else  
        q<=d;  
  
endmodule
```



Style Guide: FSMs in Verilog

- All feedback through explicitly instantiated DFF module
- Next state and output functions are combinational - case (if / else) or assign
 - No “inferred latches”
- Make sure you can reset your FSM
- Use defines for state encoding (and width)

Verilog Design of FSM Ex1

```
// Gray code state assignment
`define SWIDTH 2
`define S0 2'b00
`define S1 2'b01
`define S2 2'b11
`define S3 2'b10

// define output codes
`define DETECTED 1'b1
`define NOT_DETECTED 1'b0


module Ex2(clk, rst, in, out);
input clk;
input rst;
input in;
output reg out;

reg [`SWIDTH-1:0] state;
reg [`SWIDTH-1:0] next_state;
```

```
// low active asynchronous reset
always @(posedge clk or negedge rst_n)
if (~rst_n)
state <= `S0;
else
state <= next_state;
```

```
// state and output eqs - combinational logic
always @*
case (state)
`S0: {next_state,out} = {(in?`S1:`S0), `NOT_DETECTED};
`S1: {next_state,out} = {(in?`S2:`S0), `NOT_DETECTED};
`S2: {next_state,out} = {(in?`S3:`S0), `NOT_DETECTED};
`S3: {next_state,out} = {(in?`S3:`S0), `DETECTED};
default: {next_state,out} = {`SWIDTH+1{1'bx}};
endcase

endmodule
```

 

```
module test_ex2;
reg clk;
reg rst_n;
reg in;
wire out;

Ex2 U0(.clk(clk), .rst(rst_n), .in(in), .out(out));

always
    #5 clk = ~clk;    // generate periodic clock

initial
begin
    clk=0;rst_n=0;in=0; // set initial input, let FF reset
    #10 rst_n=1; // disable reset
    #10 in=1;
    #10 in=0;
    #10 in=1;
    #10 in=1;
    ...
end

endmodule
```


Verilog Design of FSM Ex2

```
// Gray code state assignment
`define SWIDTH 2
`define A 2'b00
`define B 2'b01
`define C 2'b11
`define D 2'b10

// define output codes
`define DETECTED 1'b1
`define NOT_DETECTED 1'b0

module Ex3(clk, rst_n, in, out);
input clk;
input rst_n;
input in;
output reg out;

 reg [`SWIDTH-1:0] state;
reg [`SWIDTH-1:0] next_state;
```



Verilog Design of FSM Ex2

```
// low active asynchronous reset
always @(posedge clk or negedge rst_n)
  if (~rst_n)
    state <= `S0;
  else
    state <= next_state;
```

```
// state and output eqs - combinational logic
always @*
```

```
case (state)
  `S0: {next_state,out} = {(in?`B:`A), (in?`NOT_DETECTED:`NOT_DETECTED)};
  `S1: {next_state,out} = {(in?`C:`A), (in?`NOT_DETECTED:`NOT_DETECTED)};
  `S2: {next_state,out} = {(in?`C:`D), (in?`NOT_DETECTED:`NOT_DETECTED)};
  `S3: {next_state,out} = {(in?`B:`A), (in?`DETECTED:`NOT_DETECTED)};
  default: {next_state,out} = {`SWIDTH+1{1'bx}};
endcase
```

```
endmodule
```

