

# **Chapter 6**

## **Registers and Counters**

1

### **Outline**

- Registers
- Shift Registers
- Ripple Counters
- Synchronous Counters
- Other Counters
- HDL for Registers and Counters


# Registers

- Clocked sequential circuits
  - A group of flip-flops and combinational gates
  - Two typical clocked sequential circuits are *registers* and *counters*.
    - Flip-flops + Combinational gates  
(essential) (optional)
- Register:
  - a group of flip-flops holding the binary information
  - gates that determine how the information is transferred into the register
- Counter:
  - a register that goes through a predetermined sequence of states

3
 
# Registers


- An  $n$ -bit register
  - $n$  flip-flops are capable of storing  $n$  bits of binary information
  - Four-bit register



4
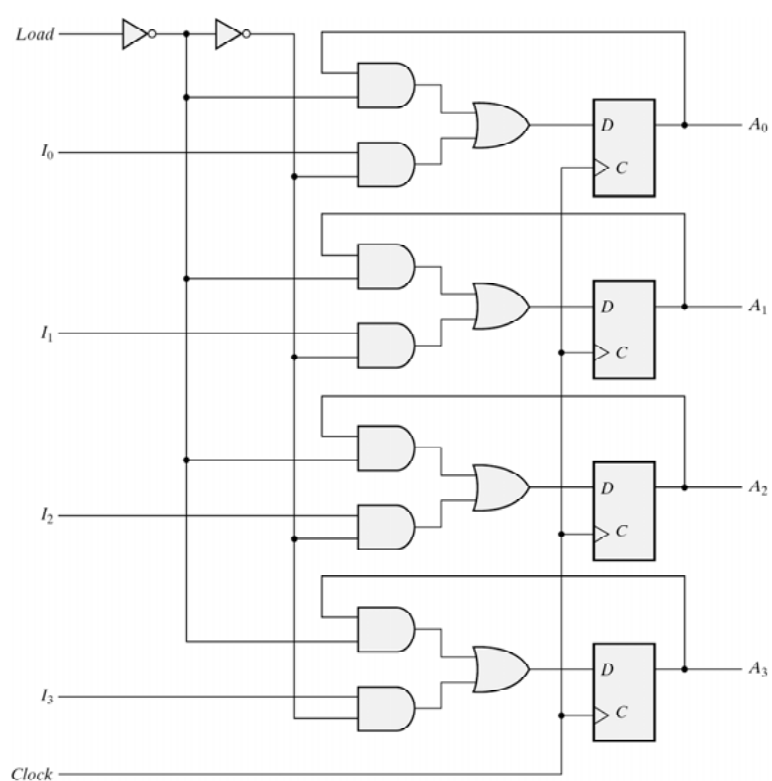
# 4-bit Register with Parallel Load


- Transfer (loading) of new information into the registers.
- All the bits are loaded to the flip-flops synchronously within one clock period.
- When load is disabled, the information in the flip-flops must be left unchanged.



5
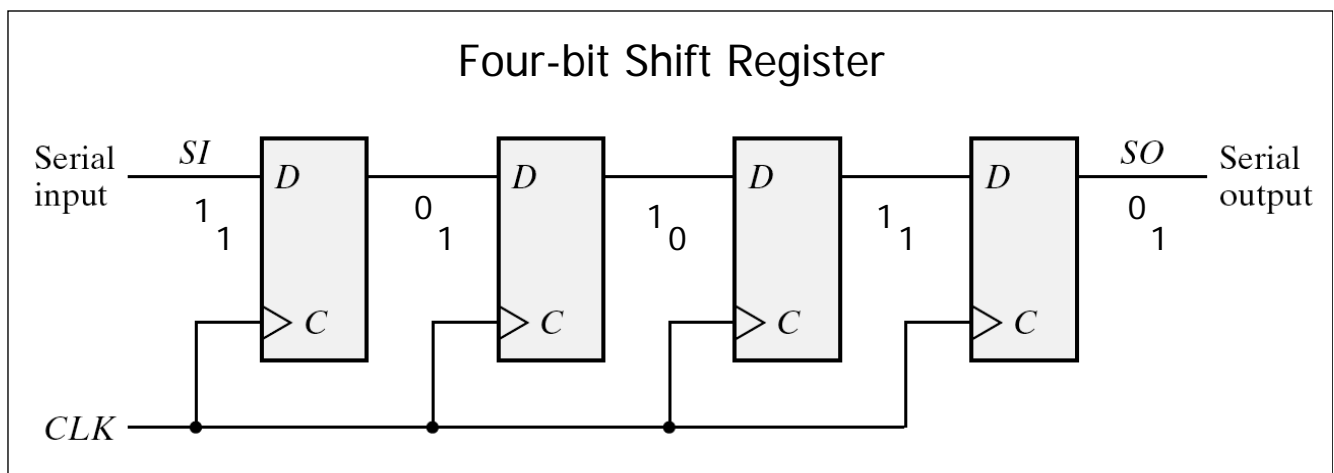
## Shift Registers

- Shift register
  - a register capable of shifting its binary information in one or both directions
- Simplest shift register using flip-flops



6


# Serial Transfer

- Serial transfer vs. Parallel transfer
- Serial transfer:
  - Information is transferred and manipulated one bit at a time
  - shifts the bits out of the source register into the destination register
- Parallel transfer:
  - All the bits of the register are transferred and manipulated at the same time

7

# Serial Transfer

- Example: Serial transfer from reg A to reg B
- Feedback of SO to SI in shift register A in order to prevent the loss of information.
- Information are shifted from register A to register B within  $n$  clock period.
- Information of shift register B will be lost unless it is connected to 3<sup>rd</sup> shift register.
- Shift control (negative edge triggered ) determines when and how many times the registers are shifted.

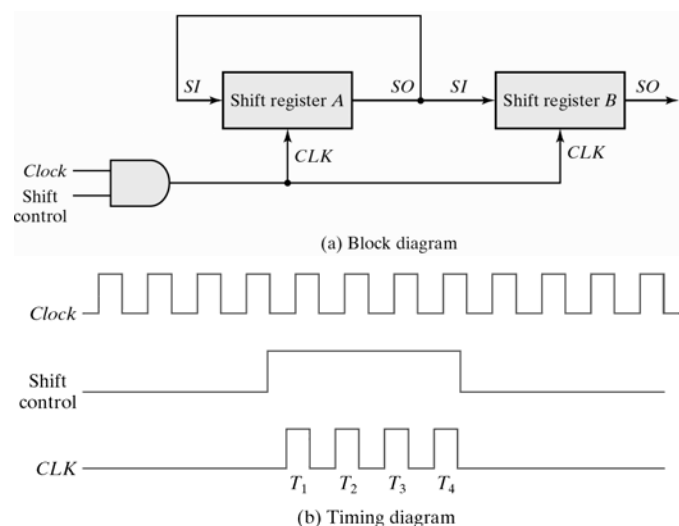

**Table 6.1**  
Serial-Transfer Example

Timing Pulse	Shift Register A				Shift Register B			
Initial value	1	0	1	1	0	0	1	0
After $T_1$	1	1	0	1	1	0	0	1
After $T_2$	1	1	1	0	1	1	0	0
After $T_3$	0	1	1	1	0	1	1	0
After $T_4$	1	0	1	1	1	0	1	1

8


# Serial Addition vs. Parallel Addition

- Parallel mode vs. serial mode
  - Operation in parallel mode is faster, but requires more hardware.
  - Operation in serial mode is slower, but requires less hardware.
- Serial adder vs. Parallel adder
  - Serial adder transfer data using shift register while parallel adder transfer data using parallel load.
  - Serial adder uses only one full adder while parallel adder uses  $n$  full adders.
  - Serial adder is a sequential circuit while parallel adder is a combinational circuit.

9
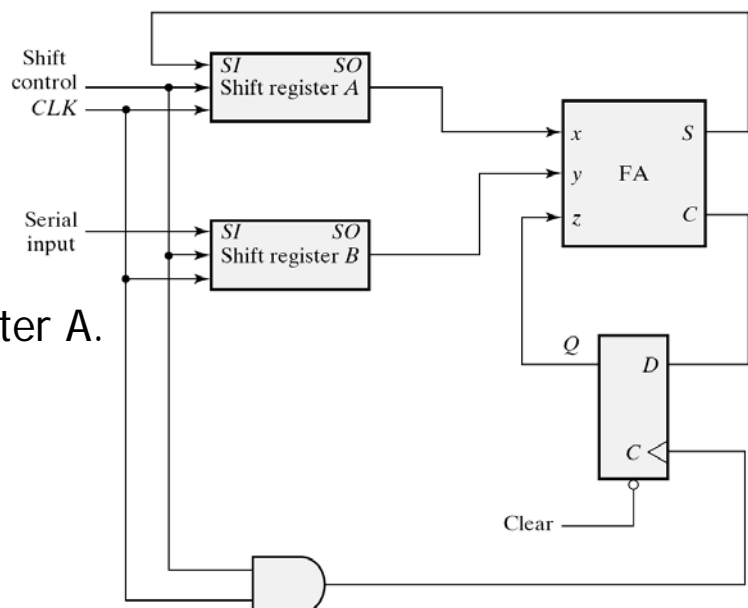
## Serial Addition using D Flip-Flops

- Initially, augend is in register A and addend is in register B.
- Shift control enables the triggering of clock and 1-bit addition of two operands from LSB to MSB.
- A new sum (S) bit is transferred to shift register A.
- A carry-out (C) of full adder is transferred to Q flip-flop as the z input of next addition.
- Finally, when the shift control is disabled, summation result is stored in shift register A.



10

# Serial Adder using JK Flip-Flops

- Serial adder can be redesign using sequential circuit design method.

**Table 6.2**  
*State Table for Serial Adder*

Present State	Inputs		Next State	Output	Flip-Flop Inputs	
	$x$	$y$			$J_Q$	$K_Q$
0	0	0	0	0	0	X
0	0	1	0	1	0	X
0	1	0	0	1	0	X
0	1	1	1	0	1	X
1	0	0	0	1	X	1
1	0	1	1	0	X	0
1	1	0	1	0	X	0
1	1	1	1	1	X	0

- By K Map:

$$J_O = x y$$

$$K_Q = x' y' = (x + y)'$$


$$S = x \oplus y \oplus Q$$

### Flip-Flop Excitation Tables

$Q(t)$	$Q(t+1)$	$J$	$K$
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

11

## Circuit Diagram

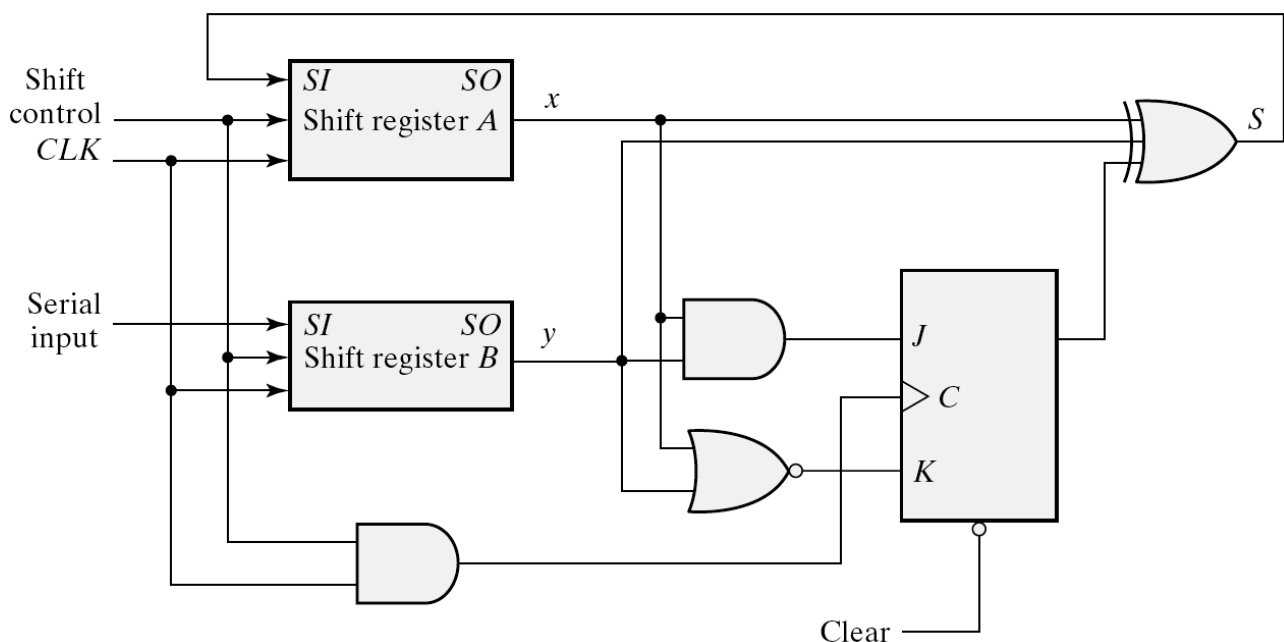

# Universal Shift Register

- Some Shift Register Types:
  - Unidirectional shift register
    - Shifting in one direction
  - Bidirectional shift register
    - Shifting in both direction
  - Universal shift register:
    - Having capabilities of both-direction shifting & parallel load/out.

13


## Capability of a Universal Shift Register

- 1. A *clear* control to clear the register to 0.
- 2. A *clock* input to synchronize the operations.
- 3. A *shift-right* control to enable the shift right operation and the *serial input* and *output* lines associated with the shift right.
- 4. A *shift-left* control to enable the shift left operation and the *serial input* and *output* lines associated with the shift left.
- 5. A *parallel-load* control to enable a parallel transfer and the *n parallel input* lines associated with the parallel transfer.
- 6. *n parallel output* lines.
- 7. A control state that leaves the information in the register unchanged in the presence of the clock.

14

# Universal Shift Register

- Four-bit universal shift register:

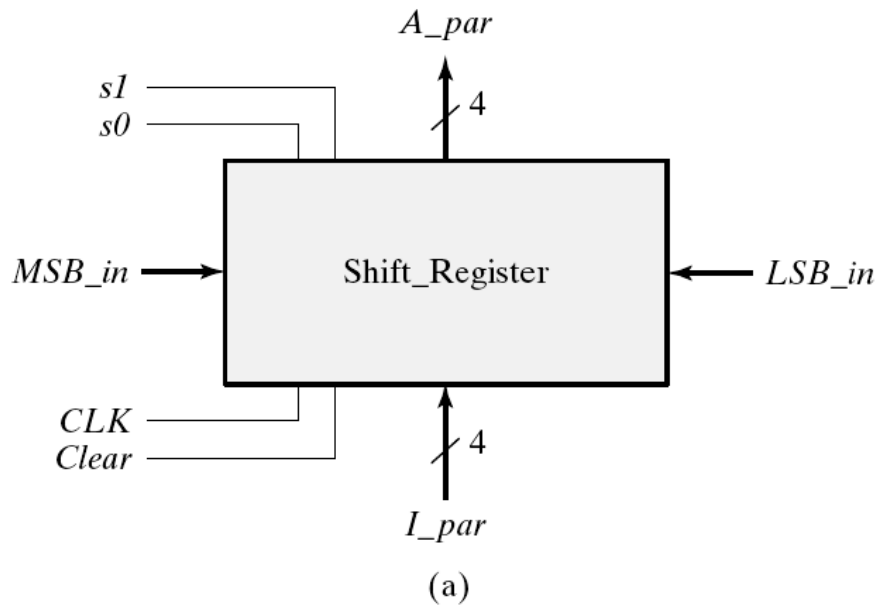

15

## Function Table


- Function Table:

Clear	$s_1$	$s_0$	$A_3^+$	$A_2^+$	$A_1^+$	$A_0^+$	(operation)
0	x	x	0	0	0	0	Clear
1	0	0	$A_3$	$A_2$	$A_1$	$A_0$	No change
1	0	1	sri	$A_3$	$A_2$	$A_1$	Shift right
1	1	0	$A_2$	$A_1$	$A_0$	sli	Shift left
1	1	1	$I_3$	$I_2$	$I_1$	$I_0$	Parallel load

16



# 4-Bit Universal Shift Register

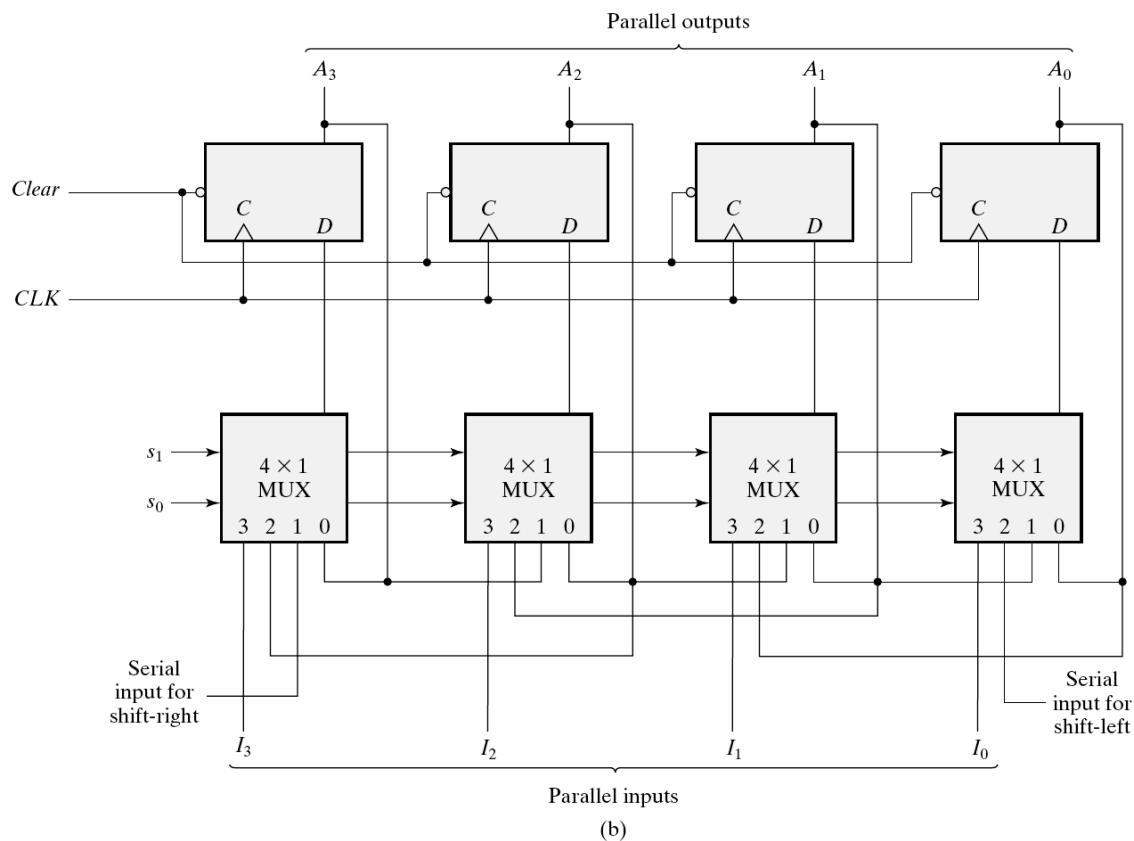

17

# Ripple Counters

- Counter:

- A register that goes through a prescribed sequence of states upon the application of input pulses
  - Input pulses: may be clock pulses or originate from some external source
  - The sequence of states: may follow the binary number sequence ( $\Rightarrow$  Binary counter) or any other sequence of states

# Categories of Counters

## ■ 1. Ripple counters:

- The flip-flop output transition serves as a source for triggering other flip-flops  
⇒ no common clock pulse (not synchronous)

## ■ 2. Synchronous counters:

- The CLK inputs of all flip-flops receive a common clock

## ■ Example: 4-bit binary ripple counter


- A complementing flip-flop is used in the least significant bit as the trigger source.
- JK flip-flop, T-flip-flop, and D-flip-flop

## Binary Counter Sequence

$A_3$	$A_2$	$A_1$	$A_0$
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0

19


## 4-bit Binary Ripple Counter

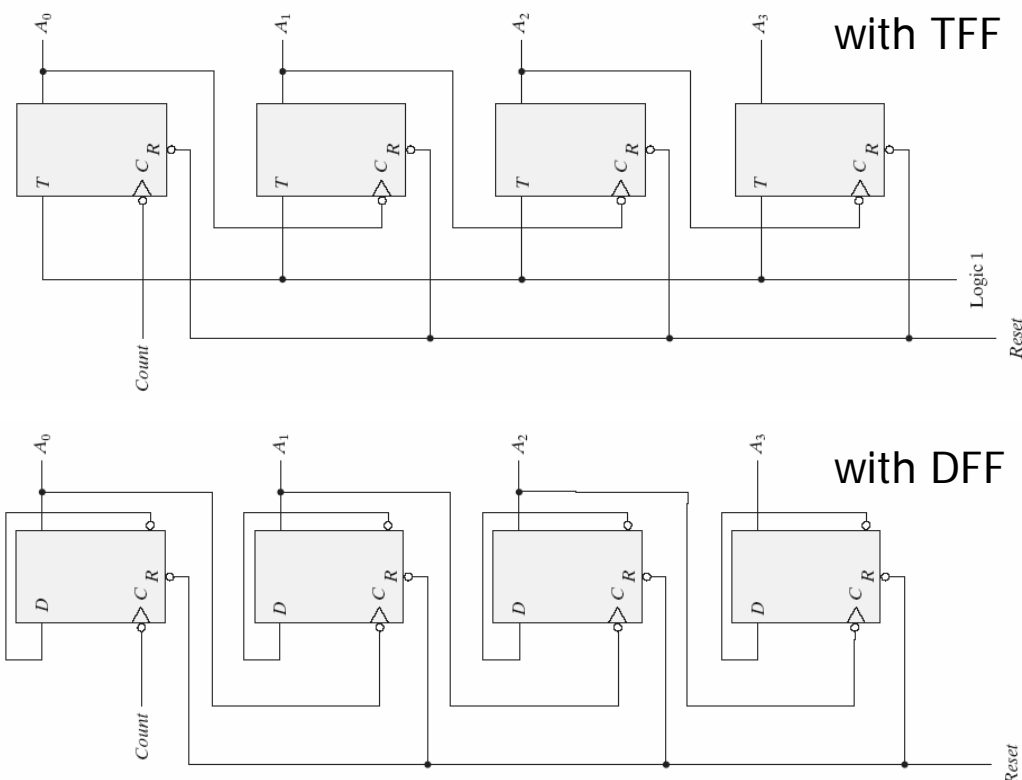

20

# BCD Ripple Counter

- State Diagram of a BCD counter

 


- State table for BCD ripple counter
- Excitation Table of JK flip-flop
- K-Map method

Present State				Next State			
$Q_8$	$Q_4$	$Q_2$	$Q_1$	$Q_8$	$Q_4$	$Q_2$	$Q_1$
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0

21
 
# Logic Diagram of a BCD Ripple Counter

- The circuit for one-decade BCD counter
  - When  $J = 1$   $K = 1$ , JK is complementing flip-flop.
- Observation from the state table
  - $Q_1$ : Complementing  $Q_1$  for every negative count
  - $Q_2$ : Complementing  $Q_2$  at negative  $Q_1$  when  $Q_8$  is 0
  - $Q_4$ : Complementing  $Q_4$  at negative  $Q_2$
  - $Q_8$ : Complementing  $Q_8$  at negative  $Q_4$  when  $Q_2 = 1$  and  $Q_4 = 1$ .




22

# Three-decade BCD Counter
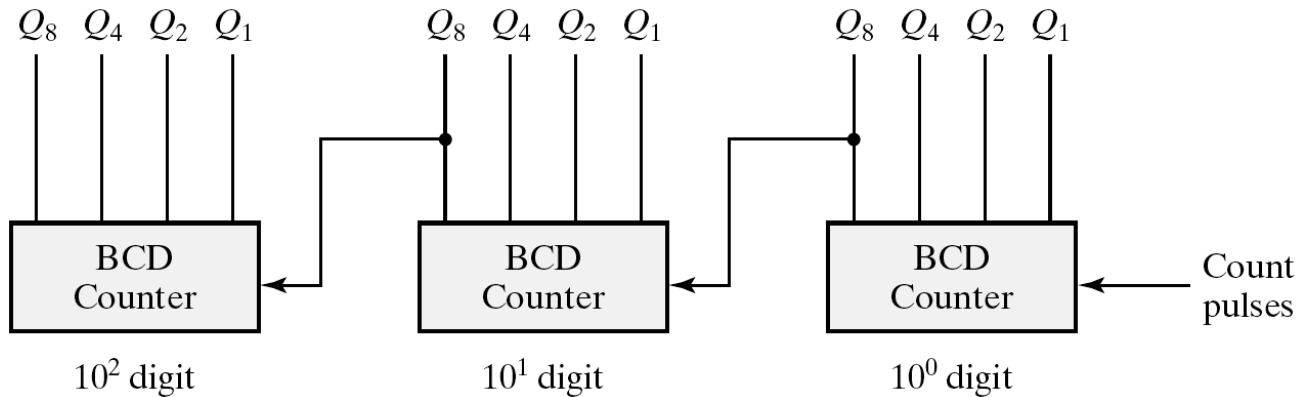
## ■ Block diagram

- When  $Q_8$  in one decade goes from 1 to 0, it triggers the count for the next higher-order decade while its own decade goes from 9 to 0.



23

# Synchronous Counters

## ■ Synchronous counter

- A common clock triggers all flip-flops simultaneously


## ■ Design procedure

- Apply the same procedure of synchronous sequential circuits.
- Synchronous counter is simpler than general synchronous sequential circuit because of its regularity.

24
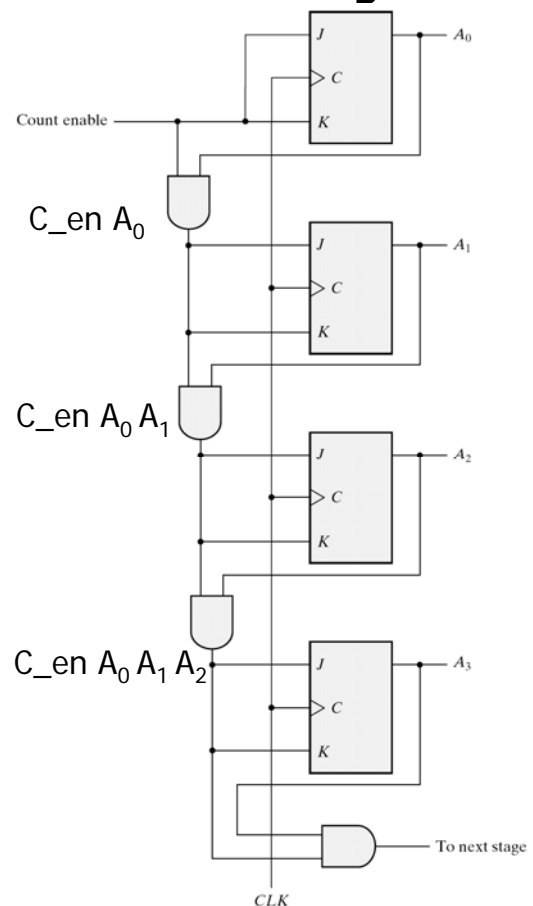
# Four-bit Synchronous Binary Counter


- 4-bit synchronous binary counter
  - $A_1$  counts when  $C\_en = 1$  and  $A_0 = 1$
  - $A_2$  counts when  $C\_en = 1$ ,  $A_0 = 1$ , and  $A_1 = 1$ .
  - $A_3$  counts when  $C\_en = 1$ ,  $A_0 = 1$ ,  $A_1 = 1$ , and  $A_2 = 1$ .
- The synchronous counter can be triggered with either the positive or the negative clock edge



25
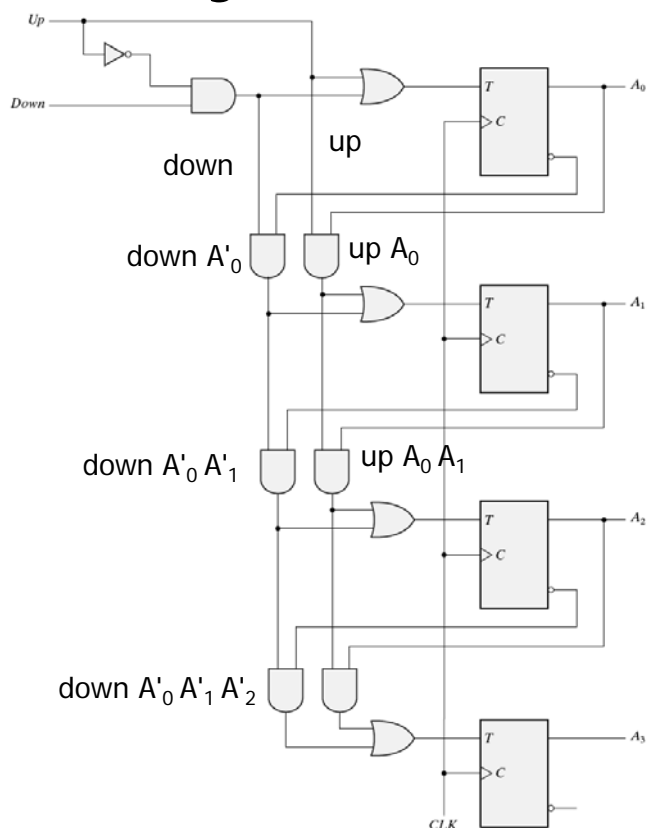
# 4-bit Up/Down Binary Counter

- 4-bit up/down binary counter
  - The bit in the least significant position is complemented with each pulse.
  - *Up counter*: A bit is complemented if all lower significant bits are equal to 1.
  - *Down counter*: A bit is complemented if all lower significant bits are equal to 0.



26

# BCD Counters

- A BCD counter does not have a regular pattern as in a straight binary count, thus need to go through a sequential circuit procedure.

**Table 6.5**  
*State Table for BCD Counter*

Present State				Next State				Output	Flip-Flop Inputs			
$Q_8$	$Q_4$	$Q_2$	$Q_1$	$Q_8$	$Q_4$	$Q_2$	$Q_1$	$y$	$TQ_8$	$TQ_4$	$TQ_2$	$TQ_1$
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1

27

## Excitation Function and Mapping

### ■ K-map

- $T_{Q1} = 1$
- $T_{Q2} = Q_8'Q_1$
- $T_{Q4} = Q_2Q_1$
- $T_{Q8} = Q_8Q_1 + Q_4Q_2Q_1$
- $y = Q_8Q_1$

$Q(t)$	$Q(t + 1)$	$T$
0	0	0
0	1	1
1	0	1
1	1	0

### ■ • Circuit Diagram



**Table 6.6**  
*Function Table for the Counter of Fig. 6.14*

Clear	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change

28

  
# 4-bit Binary Counter with Parallel Load

- 4-bit binary counter with parallel load
- For each JK flip-flop, complementing is executed when the least significant bits are all 1's.



 
## BCD Counter Using a Binary Counter

- Generate any count sequence:
  - The AND gate in (a) detects the occurrence of state 1001, then the counter loads input 0000.
  - The NAND gate in (b) detects the occurrence of state 1001, then clears the counter and reset the counter to 0000.



(a) Using the load input

 

(b) Using the clear input

# Other Counters

- Counters can be designed to generate any desired sequence of states
- Divide-by- $N$  counter (modulo- $N$  counter)
  - A counter that goes through a repeated sequence of  $N$  states
  - The sequence may follow the binary count or may be any other arbitrary sequence

31

## Counters with Unused States

- $n$  flip-flops  $\Rightarrow 2^n$  binary states
- Unused states
  - states that are not used in specifying the FSM and may be treated as don't-care conditions or may be assigned specific next states
- Self-correcting counter
  - Ensure that when a circuit enter one of its unused states, it eventually goes into one of the valid states after one or more clock pulses so it can resume normal operation.  
 $\Rightarrow$  Analyze the circuit to determine the next state from an unused state after it is designed

32



# Counters with Unused States

- An example:

**Table 6.7**

*State Table for Counter*

Present State			Next State			Flip-Flop Inputs					
A	B	C	A	B	C	$J_A$	$K_A$	$J_B$	$K_B$	$J_C$	$K_C$
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

Two unused states: 011 & 111

The simplified flip-flop input equations:

$$J_A = B, K_A = B$$



$$J_B = C, K_B = 1$$

$$J_C = B', K_C = 1$$

33
 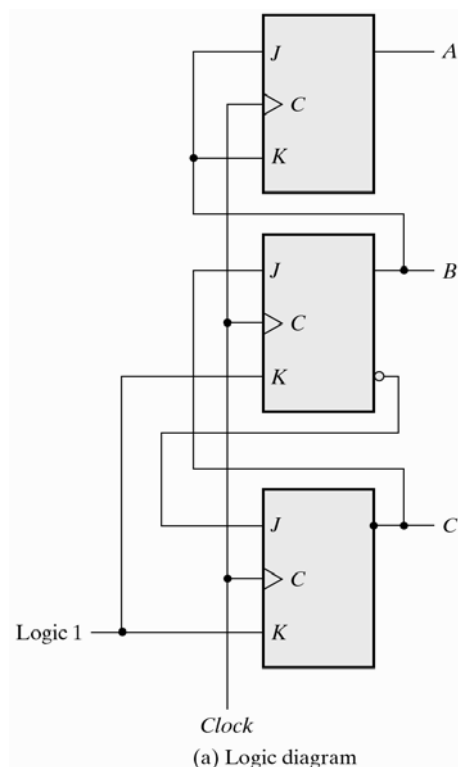
## Counter with Unused States

- The logic diagram and state diagram of the circuit




34

# Ring Counter

- A circular shift register w/ only one flip-flop being set at any particular time, all others are cleared  
(initial value = 1 0 0 ... 0 )
- The single bit is shifted from one flip-flop to the next to produce the sequence of timing signals.
- An example: 4-bit counter


$A_3$	$A_2$	$A_1$	$A_0$
1	0	0	0
0	1	0	0
0	0	1	0
0	0	0	1
1	0	0	0

 

35
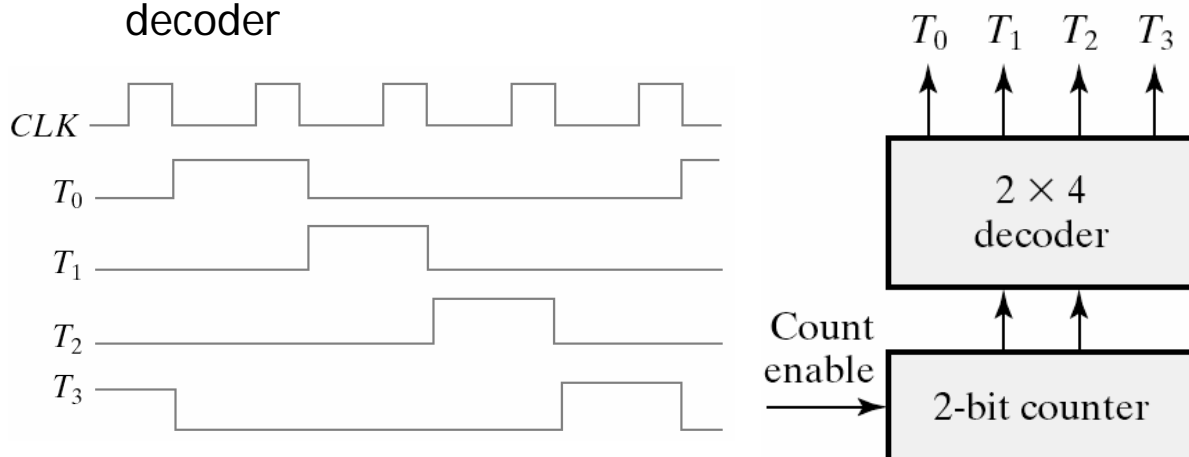
# Ring Counter

- Application of counters
  - Counters may be used to generate timing signals to control the sequence of operations in a digital system.
- Approaches for generation of  $2^n$  timing signals
  1. a shift register w/  $2^n$  flip-flops
  2. an  $n$ -bit binary counter together w/ an  $n$ -to- $2^n$ -line decoder




36

# Johnson Counter

- Ring counter vs. Switch-tail ring counter
  - Ring counter
    - a  $k$ -bit ring counter circulates a single bit among the flip-flops to provide  $k$  distinguishable states.
  - Switch-tail ring counter
    - is a circular shift register w/ the complement output of the last flip-flop connected to the input of the first flip-flop
    - a  $k$ -bit switch-tail ring counter will go through a sequence of  $2k$  distinguishable states. (initial value = 0 0 ... 0)

37

## Switch-Tail Ring Counter

 

(a) Four-stage switch-tail ring counter

Sequence number	Flip-flop outputs				AND gate required for output
	A	B	C	E	
1	0	0	0	0	$A'E'$
2	1	0	0	0	$AB'$
3	1	1	0	0	$BC'$
4	1	1	1	0	$CE'$
5	1	1	1	1	$AE$
6	0	1	1	1	$A'B$
7	0	0	1	1	$B'C$
8	0	0	0	1	$C'E$

(b) Count sequence and required decoding

38

# Johnson Counter

- Johnson counter
  - a  $k$ -bit switch-tail ring counter +  $2k$  decoding gates
  - provide outputs for  $2k$  timing signals
    - E.g.: 4-bit Johnson counter
  - The decoding follows a regular pattern:
    - 2 inputs per decoding gate

39

## Summary

- Disadvantage of the switch-tail ring counter
  - If it finds itself in an unused state, it will persist to circulate in the invalid states and never find its way to a valid state.
  - One correcting procedure:  $D_C = (A + C) B$
- Summary:
  - Johnson counters can be constructed for any # of timing sequences:
    - # of flip-flops = 1/2 (the # of timing signals)
    - # of decoding gates = # of timing signals
    - 2-input per gate

40

# HDL for Registers and Counters

- Shift Register
- Statement: `A_par <+ {MSB_in, A_par [3: 1]}`
  - specifies a concatenation of serial data input for a right shift operation (MSB\_in) with bits `A_par[3 : 1]` of the output data bus.

41

## Behavioral Description of a 4-bit Universal Shift Register

```
// Fig. 6.7 and Table 6.3
module Shift_Register_4_beh (                                // V2001, 2005
    output reg      [3: 0]  A_par,                          // Register output
    input           [3: 0]  I_par,                          // Parallel input
    input           s1, s0,                                  // Select inputs
                    MSB_in, LSB_in,                         // Serial inputs
                    CLK, Clear                             // Clock and Clear
);

always @ (posedge CLK, negedge Clear) // V2001, 2005
    if (~Clear) A_par <= 4'b0000;
    else
        case ({s1, s0})
            2'b00: A_par <= A_par;                          // No change
            2'b01: A_par <= {MSB_in, A_par[3: 1]};          // Shift right
            2'b10: A_par <= {A_par[2: 0], LSB_in};           // Shift left
            2'b11: A_par <= I_par;                          // Parallel load of input
        endcase
endmodule
```

42

# HDL for Universal Shift Register

```
// Structural description of a 4-bit universal shift register (see Fig. 6.7)
module Shift_Register_4_str (                                // V2001, 2005
    output [3: 0]  A_par,                                     // Parallel output
    input  [3: 0]  I_par,                                     // Parallel input
    input          s1, s0,                                   // Mode select
    input          MSB_in, LSB_in, CLK, Clear                // Serial inputs, clock, clear
);

// bus for mode control
wire  [1:0]  select = {s1, s0};

// Instantiate the four stages
stage ST0 (A_par[0], A_par[1], LSB_in, I_par[0], A_par[0], select, CLK, Clear);
stage ST1 (A_par[1], A_par[2], A_par[0], I_par[1], A_par[1], select, CLK, Clear);
stage ST2 (A_par[2], A_par[3], A_par[1], I_par[2], A_par[2], select, CLK, Clear);
stage ST3 (A_par[3], MSB_in, A_par[2], I_par[3], A_par[3], select, CLK, Clear);
endmodule
```

43

# HDL for Universal Shift Register

```
// One stage of shift register
module stage (i0, i1, i2, i3, Q, select,
    CLK, Clr);
    input  i0,          // circulation bit
    selection
            i1,          // data from left
neighbor or serial input for shift-right
            i2,          // data from right
neighbor or serial input for shift-left
            i3;          // data from parallel
input
    output Q;
    input [1: 0]  select;  // stage
mode control bus
    input  CLK, Clr;      // Clock,
Clear for flip-flops
    wire  mux_out;

// instantiate mux and flip-flop
    Mux_4_x_1 M0 (mux_out, i0, i1, i2, i3,
select);
```

```
D_flip_flop M1 (Q, mux_out, CLK, Clr);
endmodule

// 4x1 multiplexer
// behavioral model
module Mux_4_x_1 (mux_out, i0, i1, i2,
i3, select);
    output          mux_out;
    input           i0, i1, i2, i3;
    input [1: 0]    select;
    reg             mux_out;
    always @ (select, i0, i1, i2, i3)
        case (select)
            2'b00:    mux_out = i0;
            2'b01:    mux_out = i1;
            2'b10:    mux_out = i2;
            2'b11:    mux_out = i3;
        endcase
endmodule
```

44

# HDL for Binary Counter with Parallel Load

```
module Binary_Counter_4_Par_Load (  
  
    output reg      [3:0]    A_count, // Data output  
    output          C_out,   // Output carry  
    input           [3:0]    Data_in, // Data input  
    input           Count,   // Active high to count  
    Load,         // Active high to load  
    CLK,           // Positive edge sensitive  
    Clear          // Active low  
);  
  
assign C_out = Count & (~Load) & (A_count == 4'b1111);  
always @ (posedge CLK, negedge Clear)  
    if (~Clear)          A_count <= 4'b0000;  
    else if (Load)        A_count <= 4'b0000;  
    else if (Count)       A_count <= A_count + 1'b1;  
    else                  A_count <= A_count;    // redundant statement  
endmodule
```

45

# HDL for Ripple Counter

```
//Ripple Counter  
`timescale 1ns / 100 ps  
module Ripple_Counter_4bit (A3, A2, A1, A0, Count, Reset);  
    output      A3, A2, A1, A0;  
    input       Count, Reset;  
    //Instantiate complementing flip-flop  
    Comp_D_flip_flop F0 (A0, Count, Reset);  
    Comp_D_flip_flop F1 (A1, A0, Reset);  
    Comp_D_flip_flop F2 (A2, A1, Reset);  
    Comp_D_flip_flop F3 (A3, A2, Reset);  
endmodule  
    //Complementing flip-flop with delay  
    //Input to D flip-flop = Q'  
    module Comp_D_flip_flop (Q, CLK, Reset);  
        output      Q;  
        input       CLK, Reset;  
        reg          Q;  
        always @ (negedge CLK, posedge Reset)  
            if (Reset) Q <= 1'b0; else Q <= #2 ~Q;  
    endmodule
```

46

# HDL for Ripple Counter



```
//Stimulus for testing ripple counter
module t_Ripple_Counter_4bit;
  reg    Count;
  reg    Reset;
  wire   A0, A1, A2, A3;
  //Instantiate ripple counter
  Ripple_Counter_4bit M0 (A3, A2, A1, A0, Count, Reset);
  always
    #5 Count = ~Count;
  initial
    begin
      Count = 1'b0;
      Reset = 1'b1;
      #4 Reset = 1'b0;
    end

  initial #170 $finish;

endmodule
```

47

## Simulation Output

  

48