

Chapter 2

Boolean Algebra and Logic Gates

1

Outline

- Basic Definitions of Boolean Algebra
- Axiomatic Definitions
- Basic Theorems and Properties of Boolean Algebra
- Boolean Functions
- Canonical and Standard Forms
- Other Logic Operations
- Digital Logic Gates
- Integrated Circuits

2

History of Boolean Algebra

- In 1854, George Boole introduced a systematic treatment algebra for logic now called Boolean algebra.
- In 1904, Edward V. Huntington proposed a formal definition of Boolean Algebra.
- In 1938, Claude E. Shannon introduced two-value Boolean Algebra called switching algebra for bistable electrical switching circuits.

3

The postulates of a mathematical system

1. **Closure:** A set S is closed with respect to (w.r.t.) a binary operator $*$ if, for every pair of elements of S , the binary operator specifies a rule for obtaining a unique element of S .
 - For any $a, b \in S$, a unique $c \in S$ such that $a * b = c$.
2. **Associative law:** A binary operator $*$ on a set S is said to be associative whenever $(x * y) * z = x * (y * z)$ for all $x, y, z \in S$.
3. **Commutative law:** A binary operator $*$ on a set is said to be commutative whenever $x * y = y * x$ for all $x, y \in S$.

4

The postulates of a mathematical system (Cont'd)

4. **Identity element:** A set S is said to have an identity element w.r.t. a binary operator $*$ on S there exist an element $e \in S$ with the property:

$$e * x = x * e = x \text{ for every } x \in S$$

5. **Inverse:** A set S having the identity element e w.r.t. to a binary operator $*$ is said to have an inverse whenever, for every $x \in S$, there exists an element $y \in S$ such that $x * y = e$.

6. **Distributive Law:** If $*$ and \cdot are binary operators on S , $*$ is said to be distributive over \cdot whenever

$$x * (y \cdot z) = (x * y) \cdot (x * z)$$

5

Example

- For real number:
 - The operator “+” defines as addition.
 - The additive identity is 0.
 - Additive inverse is “subtraction.”
 - The operator “•” defines multiplication.
 - The multiplicative identity is 1.
 - For $a \neq 0$, the multiplicative inverse of a is $1/a$ defines division.
 - The distributive law is “•” over “+”:

$$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$$

6

Boolean Algebra (Huntington Postulates)

- A set of elements B and two binary operators “+” and “•” are defined by the following postulates.
 - 1. Closure with respect to “+” and “•”.
 - 2. An identity element with respect to “+” and “•”.
$$x + 0 = 0 + x = x \text{ and } x \cdot 1 = 1 \cdot x = x$$
 - 3. Commutative with respect to “+” and “•” .
$$x + y = y + x \text{ and } x \cdot y = y \cdot x$$
 - 4. Distributive over “+” and “•”.
$$x \cdot (y + z) = (x \cdot y) + (x \cdot z) \text{ and } x + (y \cdot z) = (x + y) \cdot (x + z)$$
 - 5. For $x \in B$, there exists $x' \in B$ (complement of x) such that $x + x' = 1$ and $x \cdot x' = 0$.
 - 6. There exist at least two elements $x, y \in B$, such that $x \neq y$.

7

Differences b/w Boolean and Ordinary Algebra

1. Huntington's postulates do not include associative law, but it holds for Boolean algebra.
2. The distributive law of “+” over “•” ($x + (y \cdot z) = (x + y) \cdot (x + z)$) is valid only for Boolean algebra, but not for ordinary algebra.
3. Boolean algebra has no *additive* and *multiplicative* inverses. Therefore, there are no *subtraction* and *division* operations.
4. The complement element is not available in ordinary algebra.
5. The two-value algebra (special case of Boolean algebra) is defined as a set of limited two elements, 0 and 1.

Two-Valued Boolean Algebra

- $B = \{0, 1\}$ is the set of two-valued Boolean Algebra
- The binary operators “+” and “•” have the following characteristics:

x	y	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

AND Logic

x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

OR Logic

x	x'
0	1
1	0

NOT Logic

9

Two-Valued Boolean Algebra (Cont'd)

- Verifying Huntington postulates:
 - 1. Closure: The result of each operator belongs to B .
 - 2. Identity elements:
 - (a) $0 + 0 = 0$ $0 + 1 = 1 + 0 = 1$ (0: identity element for +)
 - (b) $1 \cdot 1 = 1$ $1 \cdot 0 = 0 \cdot 1 = 0$ (1: identity element for •)
 - 3. Commutative: The commutative is obvious from the symmetry of the operator table.
 - 5. Complement:
 - (a) $x + x' = 1$: $0 + 0' = 0 + 1 = 1$; $1 + 1' = 1 + 0 = 1$
 - (b) $x \cdot x' = 0$: $0 \cdot 0' = 0 \cdot 1 = 0$; $1 \cdot 1' = 1 \cdot 0 = 0$
 - 6. The two-valued Boolean algebra has two distinct elements, 1 and 0.

10

Two-Valued Boolean Algebra (Cont'd)

- 4. The distributive law of “ \bullet ” over “ $+$ ”:

x	y	z	$y + z$	$x \cdot (y + z)$	$x \cdot y$	$x \cdot z$	$(x \cdot y) + (x \cdot z)$
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	1	0	1	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

- The distributive law of “ $+$ ” over “ \bullet ” ?

11

Basic Theorems and Properties of Boolean Algebra

- **Duality:** every algebraic expression deducible from the postulates of Boolean algebra remains valid if the operators and identity elements are interchanged.
- Example:
 - Postulate 2, Identity elements:
 - (a) $x + 0 = x$ (change 0 to 1 and “ $+$ ” to “ \bullet ”, we get (b))
 - (b) $x \bullet 1 = x$ (change 1 to 0 and “ \bullet ” to “ $+$ ”, we get (a))

12

Basic Theorems and Properties of Boolean Algebra (Cont'd)

- Six theorems and four postulates of Boolean algebra:

Pos. 2	(a) $x + 0 = x$	(b) $x \cdot 1 = x$
Pos. 5	(a) $x + x' = 1$	(b) $x \cdot x' = 0$
Thm. 1	(a) $x + x = x$	(b) $x \cdot x = x$
Thm. 2	(a) $x + 1 = 1$	(b) $x \cdot 0 = 0$
Thm. 3, involution	(a) $(x')' = x$	(b)
Pos. 3, commutative	(a) $x + y = y + x$	(b) $xy = yx$
Thm. 4, associative	(a) $x + (y + z) = (x + y) + z$	(b) $x(yz) = (xy)z$
Pos. 4, distributive	(a) $x(y + z) = xy + xz$	(b) $x + yz = (x + y)(x + z)$
Thm. 5, DeMorgan	(a) $(x + y)' = x' \cdot y'$	(b) $(xy)' = x' + y'$
Thm. 6, absorption	(a) $x + xy = x$	(b) $x(x + y) = x$

13

Basic Theorems

- The basic theorems can be derived from basic postulates.

- Thm. 1.(a): $x + x = x$

$$\begin{aligned}
 x + x &= (x + x) \cdot 1 && \text{Pos. 2(b)} \\
 &= (x + x) \cdot (x + x') && \text{Pos. 5(a)} \\
 &= x + x \cdot x' && \text{Pos. 4(b)} \\
 &= x + 0 && \text{Pos. 5(b)} \\
 &= x && \text{Pos. 2(a)}
 \end{aligned}$$

- Thm. 1(b): $x \cdot x = x$

$$\begin{aligned}
 x \cdot x &= x \cdot x + 0 && \text{Pos. 2(a)} \\
 &= x \cdot x + x \cdot x' && \text{Pos. 5(b)} \\
 &= x \cdot (x + x') && \text{Pos. 4(a)} \\
 &= x \cdot 1 && \text{Pos. 5(a)} \\
 &= x && \text{Pos. 2(b)}
 \end{aligned}$$

14

Basic Theorems

■ Thm. 2: $x + 1 = 1$

$$\begin{aligned}
 x+1 &= 1 \cdot (x+1) && \text{Pos. 2(b)} \\
 &= (x+x') \cdot (x+1) && \text{Pos. 5(a)} \\
 &= x + x' \cdot 1 && \text{Pos. 4(b)} \\
 &= x + x' && \text{Pos. 2(b)} \\
 &= 1 && \text{Pos. 5(a)}
 \end{aligned}$$

– $x \cdot 0 = 0$ is valid by duality.

■ Thm. 3: $(x')' = x$

- From Pos. 5: $x + x' = 1$ and $x \cdot x' = 0$, defines the complement of x' . $\Rightarrow x$ is the complement of x' .
- The complement of x' is x and is also $(x')'$. Since the complement is unique, $(x')' = x$.

15

Basic Theorems

■ Thm. 6: $x + xy = x$

$$\begin{aligned}
 x + xy &= x \cdot 1 + x \cdot y && \text{Pos. 2(b)} \\
 &= x \cdot (1 + y) && \text{Pos. 4(a)} \\
 &= x \cdot (y + 1) && \text{Pos. 3(a)} \\
 &= x \cdot 1 && \text{Pos. 2(a)} \\
 &= x && \text{Pos. 2(b)}
 \end{aligned}$$

– $x \cdot (x + y) = x$ by duality.

■ By means of truth table.

x	y	xy	$x + xy$
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

16

Basic Theorems

■ DeMorgan's Theorem:

– $(x + y)' = x' \cdot y'$

– $(x \cdot y)' = x' + y'$

Verified by truth table:

x	y	$x + y$	$(x + y)'$	x'	y'	$x'y'$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

17

Operator Precedence

■ The operator precedence for evaluating Boolean expressions:

- 1. parentheses
- 2. NOT
- 3. AND
- 4. OR

■ Examples:

– $xy' + z$

– $(xy + z)'$

18

Boolean Functions


- Boolean algebra deals with binary variables and logic operations.
- A Boolean function consists of
 - binary variables (1 or 0)
 - logic operators OR and AND
 - unary operator NOT
 - parentheses
- Examples: (by Truth Table)
 - $F_1 = x + y'z$
 - $F_2 = x'y'z + x'yz + xy'$

x	y	z	F_1	F_2
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	0
1	1	1	1	0

19


Implementations of Boolean Functions with Logic Gates

- Example: $F_1 = x + y'z$

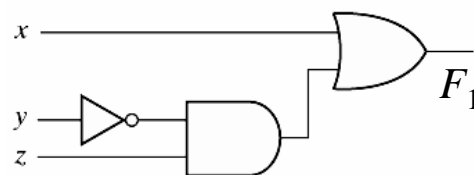

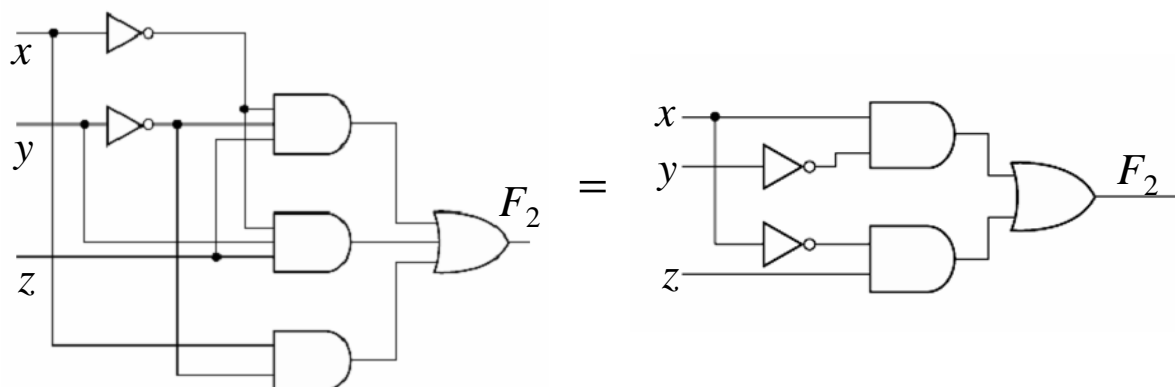- Example:

$$F_2 = x'y'z + x'yz + xy' = x'z(y' + y) + xy' = x'z + xy'$$



20

Algebraic Manipulation

- To minimize Boolean expressions
 - literal: a primed or unprimed variable (an input to a gate)
 - term: an implementation with a gate (F_2 : 3 terms, 8 literals)
 - The minimization of the number of literals and the number of terms \Rightarrow a circuit with less equipments
 - It is a hard problem (no specific rules to follow)
- Examples:
 - $x(x' + y) = xx' + xy = 0 + xy = xy$
 - $x + x'y = (x + x')(x + y) = 1(x + y) = x + y$ (by Pos.4(b))
 - $(x + y)(x + y') = x + xy + xy' + yy' = x(1 + y + y') = x$
 - $xy + x'z + yz = xy + x'z + yz(x + x')$
 $= xy + x'z + yzx + yzx'$
 $= xy(1 + z) + x'z(1 + y) = xy + x'z$

21

Complement of a Function

- The complement of a function F is F' and is an interchange of 0's for 1's and 1's for 0's in the value of F
 - by DeMorgan's theorem
 - DeMorgan's theorem can be extended to n variables:
 - $(A + B + C)' = (A + x)'$ let $B + C = x$
 $= A'x'$ by DeMorgan's
 $= A'(B + C)'$ substitute $B + C = x$
 $= A'(B'C')$ by DeMorgan's
 $= A'B'C'$ associative
- generalizations
 - $(A + B + C + \dots + F)' = A'B'C' \dots F'$
 - $(ABC \dots F)' = A' + B' + C' + \dots + F'$

22

Examples

- $(x'yz' + x'y'z)' = (x'yz')' (x'y'z)'$
 $= (x + y' + z) (x + y + z')$
- $[x(y'z' + yz)]' = x' + (y'z' + yz)'$
 $= x' + (y'z')' (yz)'$
 $= x' + (y + z) (y' + z')$
- A simpler procedure
 - take the dual of the function and complement each literal
 - $x'yz' + x'y'z \Rightarrow (x' + y + z') (x' + y' + z)$ (the dual)
 - $(x'yz' + x'y'z)' \Rightarrow (x + y' + z)(x + y + z')$

23

Canonical and Standard Forms

- Minterms and Maxterms
 - A minterm: an AND term consists of all literals in their normal form or in their complement form
 - For example, two binary variables x and y ,
 - $xy, xy', x'y, x'y'$
 - It is also called a standard product
 - n variables can be combined to form 2^n minterms
 - A maxterm: an OR term
 - It is also called a standard sum
 - n variables can be combined to form 2^n maxterms

24

Minterms and Maxterms

- Minterms (standard products) and Maxterms (standard sums) for three binary variables

			Minterms		Maxterms	
x	y	z	Term	Designation	Term	Designation
0	0	0	$x'y'z'$	m_0	$x + y + z$	M_0
0	0	1	$x'y'z$	m_1	$x + y + z'$	M_1
0	1	0	$x'yz'$	m_2	$x + y' + z$	M_2
0	1	1	$x'yz$	m_3	$x + y' + z'$	M_3
1	0	0	$xy'z'$	m_4	$x' + y + z$	M_4
1	0	1	$xy'z$	m_5	$x' + y + z'$	M_5
1	1	0	xyz'	m_6	$x' + y' + z$	M_6
1	1	1	xyz	m_7	$x' + y' + z'$	M_7

25

Minterms and Maxterms

- A Boolean function can be expressed by
 - A truth table
 - Sum of minterms
 - $f_1 = x'y'z + xy'z' + xyz = m_1 + m_4 + m_7$
 - $f_2 = x'yz + xy'z + xyz' + xyz$
 $= m_3 + m_5 + m_6 + m_7$

x	y	z	f_1	f_2
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

26

Minterms and Maxterms

- The complement of a Boolean function
 - the minterms that produce a 0
 - $f_1' = m_0 + m_2 + m_3 + m_5 + m_6$

$$= x'y'z' + x'yz' + x'yz + xy'z + xyz'$$
 - $f_1 = (f_1')'$

$$= (x + y + z)(x + y' + z)(x + y' + z')(x' + y + z')(x' + y' + z)$$

$$= M_0 M_2 M_3 M_5 M_6$$
 - Any Boolean function can be expressed as
 - a sum of minterms
 - a product of maxterms

} canonical form

27

Sum of Minterms

- Express the general logic function as a sum of minterms

Truth table for $F = A + B'C$

- $F = A + B'C$

$$= A(B + B') + B'C$$

$$= AB + AB' + B'C$$

$$= AB(C + C') + AB'(C + C') + (A + A')B'C$$

$$= ABC + ABC' + AB'C + AB'C' + A'B'C$$
- $F = A'B'C + AB'C' + AB'C + ABC' + ABC$

$$= m_1 + m_4 + m_5 + m_6 + m_7$$
- $F(A, B, C) = \Sigma(1, 4, 5, 6, 7) = \Pi(0, 2, 3)$
- or, built the truth table first

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

28

Product of Maxterms

■ Product of maxterms

- $x + yz = (x + y)(x + z)$
 $= (x + y + zz')(x + z + yy')$
 $= (x + y + z)(x + y + z')(x + y' + z) = M_0 M_1 M_2$
- $F = xy + x'z$
 $= (xy + x')(xy + z)$
 $= (x + x')(y + x')(x + z)(y + z)$
 $= (x' + y)(x + z)(y + z)$
- $x' + y = x' + y + zz'$
 $= (x' + y + z)(x' + y + z')$
- $F = (x + y + z)(x + y' + z)(x' + y + z)(x' + y + z')$
 $= M_0 M_2 M_4 M_5$
- $F(x, y, z) = \Pi(0, 2, 4, 5)$

29

Conversion between Canonical Forms

■ Conversion between Canonical Forms

- $F(A, B, C) = \Sigma(1, 4, 5, 6, 7)$
- $F'(A, B, C) = \Sigma(0, 2, 3)$
- By DeMorgan's theorem
 $F(A, B, C) = \Pi(0, 2, 3)$
- $m_j' = M_j$
- Sum of minterms = product of maxterms
- Interchange the symbols Σ and Π and list those numbers missing from the original form
- Σ of 1's = Π of 0's

30

Example

- $F = xy + x'z$
- $F(x, y, z) = \Sigma(1, 3, 6, 7)$
- $F(x, y, z) = \Pi(0, 2, 4, 5)$

Truth table for $F = xy + x'z$

<i>A</i>	<i>B</i>	<i>C</i>	<i>F</i>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

31

Standard Forms

■ Standard Forms

- Canonical forms are seldom used
- sum of products

$$F_1 = y' + xy + x'yz' \quad (\text{figure (a)})$$

$$F_3 = AB + C(D + E) \quad \text{nonstandard form (figure (c))}$$

$$F_3 = AB + CD + CE \quad \text{standard form (figure (d))}$$

- product of sums


$$F_2 = x(y' + z)(x' + y + z) \quad (\text{figure (b)})$$

- Standard form is preferred because the gate delay is minimized (figure (c) vs. figure (d))


32

Standard Form Logic

■ Two-level implementation

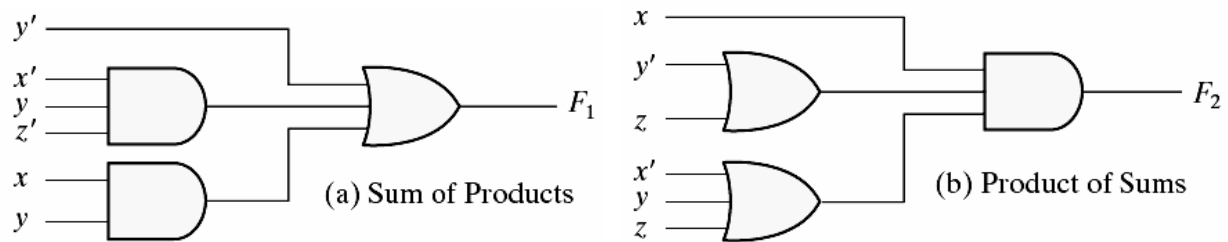

■ Multi-level implementation

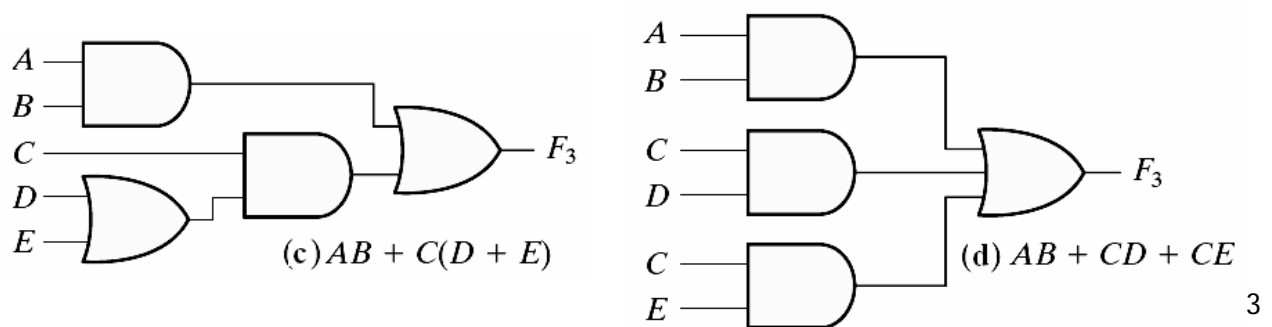

3

Other Logic Operations

- 2^n rows in the truth table of n binary variables
- 2^{2^n} functions for n binary variables
- 16 functions of two binary variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
Operator Symbol		.	/		/			\oplus	+	\downarrow	\odot	'	\subset	'	\supset	\uparrow	

- All the new symbols except for the exclusive-OR symbol are not in common use by digital designers

Table 2.8*Boolean Expressions for the 16 Functions of Two Variables*

Boolean Functions	Operator Symbol	Name	Comments
$F_0 = 0$		Null	Binary constant 0
$F_1 = xy$	$x \cdot y$	AND	x and y
$F_2 = xy'$	x/y	Inhibition	x , but not y
$F_3 = x$		Transfer	x
$F_4 = x'y$	y/x	Inhibition	y , but not x
$F_5 = y$		Transfer	y
$F_6 = xy' + x'y$	$x \oplus y$	Exclusive-OR	x or y , but not both
$F_7 = x + y$	$x + y$	OR	x or y
$F_8 = (x + y)'$	$x \downarrow y$	NOR	Not-OR
$F_9 = xy + x'y'$	$(x \oplus y)'$	Equivalence	x equals y
$F_{10} = y'$	y'	Complement	Not y
$F_{11} = x + y'$	$x \subset y$	Implication	If y , then x
$F_{12} = x'$	x'	Complement	Not x
$F_{13} = x' + y$	$x \supset y$	Implication	If x , then y
$F_{14} = (xy)'$	$x \uparrow y$	NAND	Not-AND
$F_{15} = 1$		Identity	Binary constant 1





35

Digital Logic Gates

- Boolean expression: AND, OR and NOT operations
- Considerations of constructing other logic gates:
 - the feasibility and economy
 - the possibility of extending gate's inputs
 - the basic properties of the binary operations
 - the ability of the gate to implement Boolean functions alone
- Consider the 16 functions
 - two are equal to a constant
 - four are repeated twice
 - inhibition and implication are not commutative or associative
 - the other eight: complement, transfer, AND, OR, NAND, NOR, XOR, and equivalence are used as standard gates
 - complement: inverter
 - transfer: buffer (increasing drive strength)
 - equivalence: XNOR

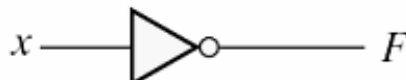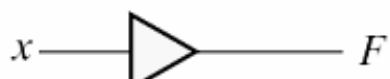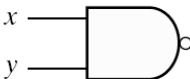

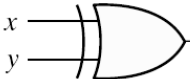

36

Basic Digital Circuit Gates

Name	Graphic symbol	Algebraic function	Truth table															
AND		$F = xy$	<table><tr><td>x</td><td>y</td><td>F</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$F = x + y$	<table><tr><td>x</td><td>y</td><td>F</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	1
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
Inverter		$F = x'$	<table><tr><td>x</td><td>F</td></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	x	F	0	1	1	0									
x	F																	
0	1																	
1	0																	
Buffer		$F = x$	<table><tr><td>x</td><td>F</td></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	x	F	0	0	1	1									
x	F																	
0	0																	
1	1																	

7

Basic Digital Circuit Gates (Cont'd)


NAND		$F = (xy)'$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	1	0	1	1	1	0	1	1	1	0
x	y	F																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$F = (x + y)'$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	0
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
Exclusive-OR (XOR)		$F = xy' + x'y$ $= x \oplus y$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	0
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
Exclusive-NOR or equivalence		$F = xy + x'y'$ $= (x \oplus y)'$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	1																

Digital Circuit Gates – AND/OR, NAND/NOR

■ Extension to multiple inputs


- A gate can be extended to multiple inputs
 - if its binary operation is commutative and associative
- AND and OR are commutative and associative
 - $(x + y) + z = x + (y + z) = x + y + z$
 - $(x \cdot y) \cdot z = x \cdot (y \cdot z) = x \cdot y \cdot z$

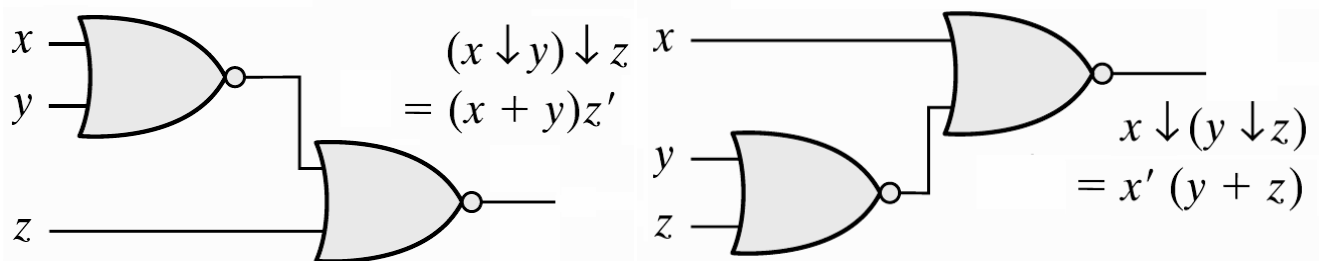■ NAND and NOR are commutative but not associative \Rightarrow They are not extendable.




Digital Circuit Gates – NAND/NOR

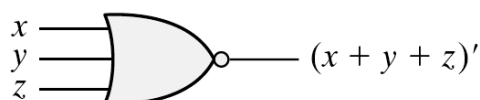
- Multiple NOR = a complement of OR gate } Definition
- Multiple NAND = a complement of AND } Modified
- The cascaded NAND operations = sum of products
- The cascaded NOR operations = product of sums



(a) 3-input NOR gate

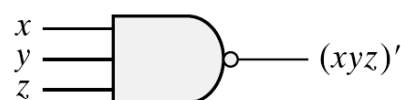



(b) 3-input NAND gate

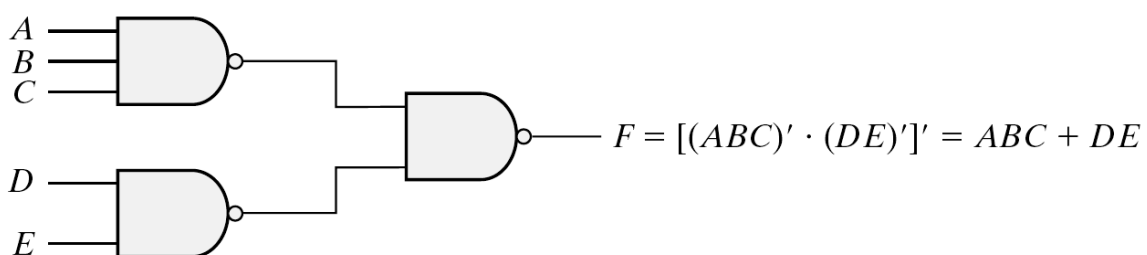

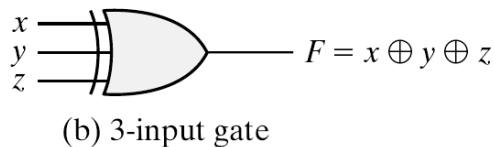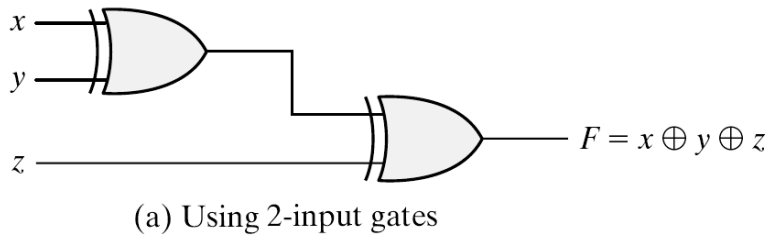(c) Cascaded NAND gates

Digital Circuit Gates - XOR

- The XOR and XNOR gates are commutative and associative
- Multiple-input XOR gates are uncommon.
- XOR is an odd function: it is equal to 1 if the inputs variables have an odd number of 1's




x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(c) Truth table


41

Digital Circuit Gates

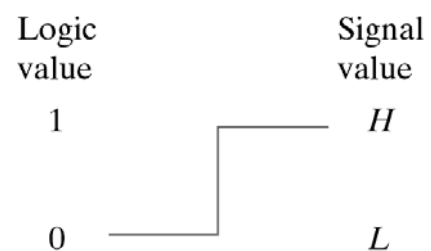- Positive and Negative Logic
 - two signal values \Leftrightarrow two logic values
 - positive logic: $H=1$; $L=0$
 - negative logic: $H=0$; $L=1$
- Consider a TTL gate
 - a positive logic NAND gate
 - a negative logic OR gate
 - the positive logic is used in this book



(a) Positive logic

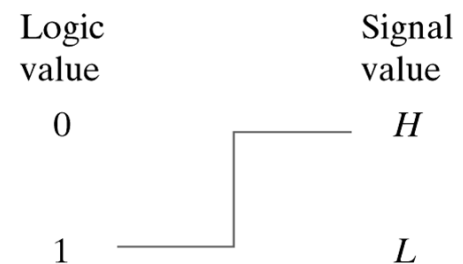

(b) Negative logic

42

x	y	z
L	L	L
L	H	L
H	L	L
H	H	H


(a) Truth table with H and L

x	y	z
0	0	0
0	1	0
1	0	0
1	1	1


(c) Truth table for positive logic

x	y	z
1	1	1
1	0	1
0	1	1
0	0	0


(e) Truth table for negative logic

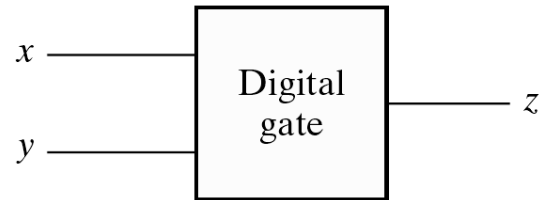

(b) Gate block diagram

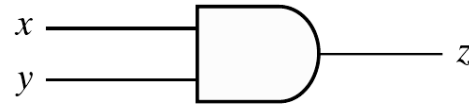

(d) Positive logic AND gate

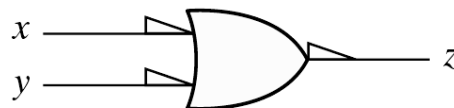

(f) Negative logic OR gate

43

Integrated Circuits

- An integrated circuit (IC) is a silicon semiconductor crystal, called a chip, containing electronic digital gates.
- Examples:
 - SSI: < 10 gates
 - MSI: 10 ~ 100 gates
 - LSI: 100 ~ xk gates
 - VLSI: > xk gates
 - small size (compact size)
 - low cost
 - low power consumption
 - high reliability
 - high speed



44

Integrated Circuits

- Digital logic families: circuit technology
 - TTL: transistor-transistor logic (dying?)
 - ECL: emitter-coupled logic (high speed, high power consumption)
 - MOS: metal-oxide semiconductor (NMOS, high density)
 - CMOS: complementary MOS (low power)
 - BiCMOS: high speed, high density
- The characteristics of digital logic families
 - Fan-out: the number of standard loads that the output of a typical gate can drive
 - Power dissipation
 - Propagation delay: the average transition delay time for the signal to propagate from input to output
 - Noise margin: the minimum of external noise voltage that caused an undesirable change in the circuit output

45

Integrated Circuits

- CAD – Computer-Aided Design
 - Millions of transistors
 - Computer-based representation and aid
 - Automatic the design process
 - Design entry
 - Schematic capture
 - HDL – Hardware Description Language
 - Verilog, VHDL
 - Simulation
 - Physical realization
 - ASIC, FPGA, PLD