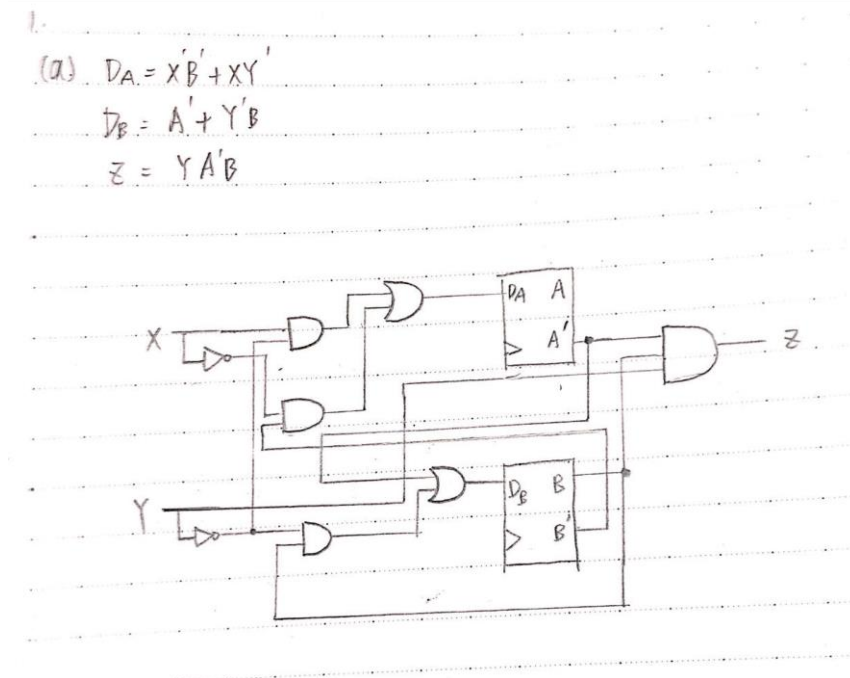


HW5

1. (15%) A sequential circuit with two D flip-flops A and B, two inputs X and Y, and one output Z is specified by the following input equations:

$$D_A = X'B' + XY', D_B = A' + Y'B, Z = YA'B$$


- (a) Draw the logic diagram of the circuit.





- (b) Derive the state table.

Present state		Input		Next state		Output
A(t)	B(t)	X	Y	A(t+1)	B(t+1)	Z
0	0	0	0	1	1	1
0	0	0	1	1	1	0
0	0	1	0	1	1	1
0	0	1	1	0	1	0
0	1	0	0	0	1	0
0	1	0	1	0	1	0
0	1	1	0	1	1	0
0	1	1	1	0	1	0
1	0	0	0	1	0	1
1	0	0	1	1	0	0
1	0	1	0	1	0	1
1	0	1	1	0	0	0
1	1	0	0	0	1	0
1	1	0	1	0	0	0
1	1	1	0	1	1	0
1	1	1	1	0	0	0


(c) Derive the state diagram.

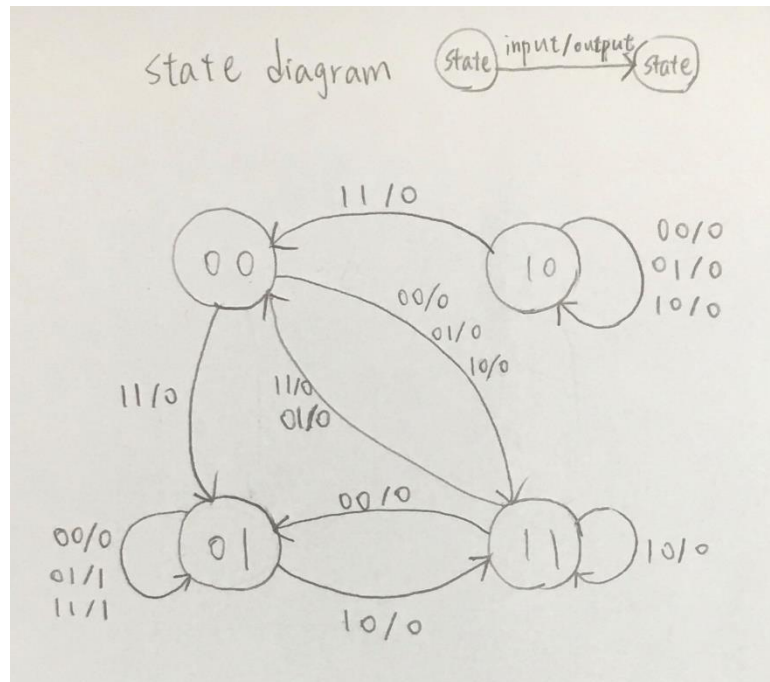

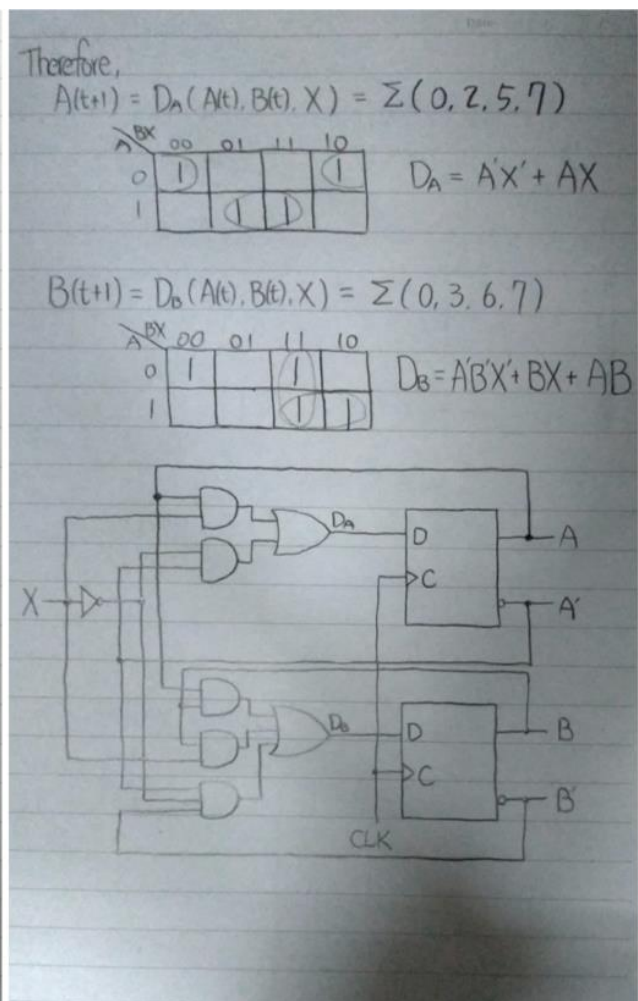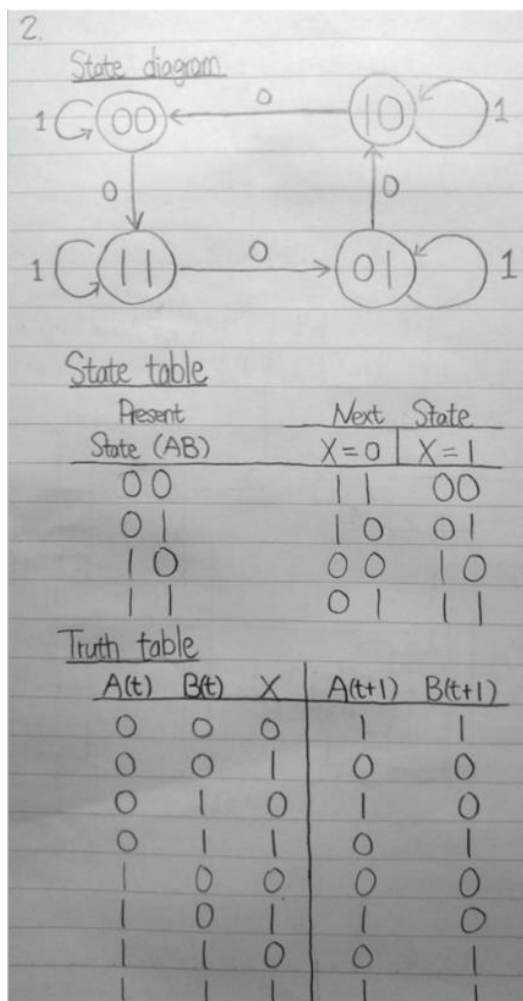
2. (10%) Design a sequential circuit with two D flip-flops A and B and one input X. When $X = 1$, the state of the circuit remains the same. When $X = 0$, the circuit goes through the state transitions from 00 to 11 to 01 to 10, back to 00, and then repeats.



 
3. (20%) For the D-type positive edge-triggered flip-flop and D-type positive level-sensitive (level-triggered) latch with the same clock (clk), asynchronous reset signal (rst, active low), and input (Data) below. Assume the initial state of both the flip-flop and latch are '0', and both devices are with 0 D-to-Q delay. Point out the incorrect parts for Q1 and Q2 in the timing diagram and redraw the correct timing diagram.




Incorrect parts:

 

Correct timing diagram:

 


 4. (10%) A sequential circuit has two flip-flops A and B, one input X, and one output Y. The state diagram is shown in figure below. Design the circuit with D flip-flops.




Ans:

Present state			Input	Next state			Output
A	B	C		A+1	B+1	C+1	
0	0	0	0	0	1	1	0
0	0	0	1	1	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	1	0	0	1
0	1	0	0	0	1	0	0
0	1	0	1	0	0	0	1
0	1	1	0	0	0	1	0
0	1	1	1	0	1	0	1
1	0	0	0	0	1	0	0
1	0	0	1	0	1	1	0

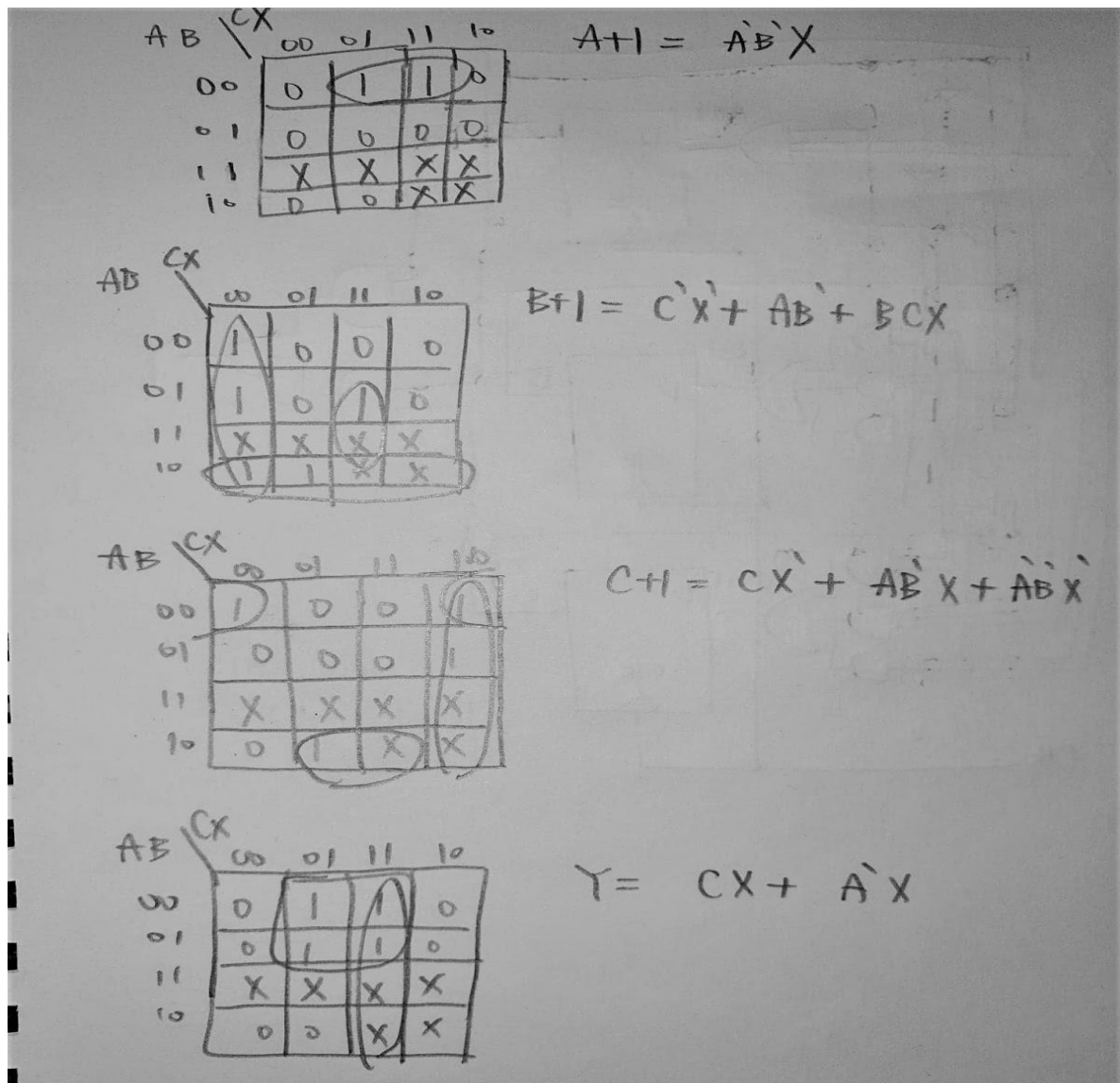


Logic Diagram (Optional):

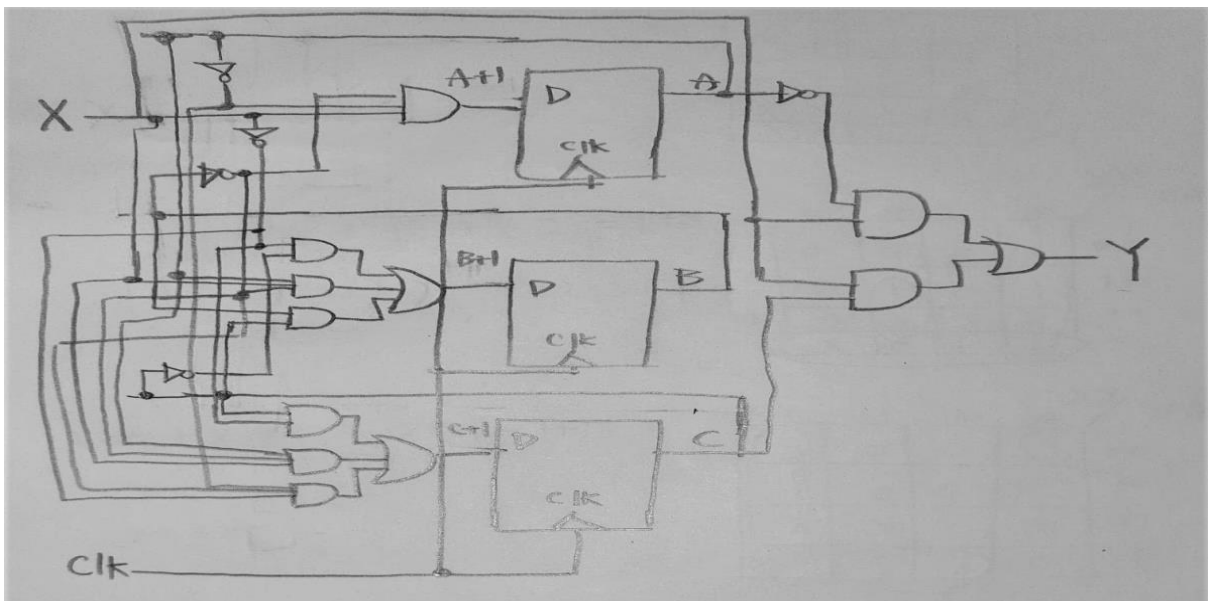

5. (10%) Draw the state diagram of the sequential circuit specified by the following state table.

Present State		Inputs		Next State		Output
A	B	X	Y	A	B	Z
0	0	0	0	0	0	0
0	0	0	1	0	1	0
0	0	1	0	1	0	1
0	0	1	1	1	1	1
0	1	0	0	0	1	1
0	1	0	1	1	0	1
0	1	1	0	1	0	0
0	1	1	1	0	0	0
1	0	0	0	1	1	1
1	0	0	1	1	1	0
1	0	1	0	1	1	1
1	0	1	1	1	0	0
1	1	0	0	0	0	0
1	1	0	1	0	0	1
1	1	1	0	0	0	0
1	1	1	1	0	1	1


Ans:

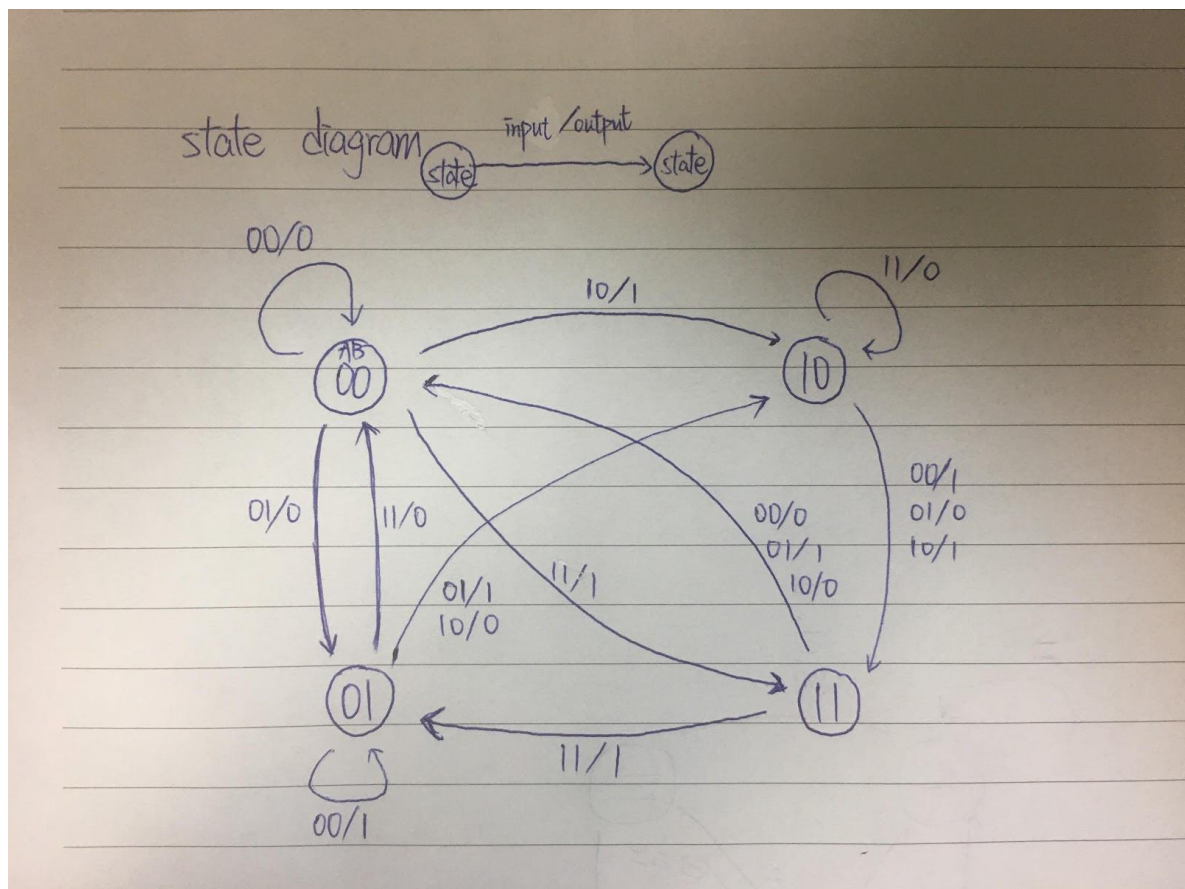

6. (15%) Design a recognizer that recognizes an input sequence that has at least three 1's. The recognizer has a single input X, and a single output Y, and one asynchronous Reset input signal. The recognizer sets the output Y to 1 if the input signal X was equal to 1 in at least 3 clock cycles after reset. (a) Derive the state diagram. (b) Encode the states to minimize the combinational logic. (c) Draw the logic diagram using D flip-flops.

*本題使用 Moore Machine 或 Mealy Machine 皆可，解答以 Mealy Machine 為例


(a)

 

(b)

present state	next state		output y	
	x=0	x=1	x=0	x=1
S0	00	01	0	0
S1	00	10	0	0
S2	00	11	0	1

(c)

 

7. (20%) Reduce the number of states in the following state table and tabulate the reduced state table.

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
a	f	b	0	0
b	d	e	1	0
c	f	e	0	0
d	g	a	1	0
e	d	e	1	0
f	f	b	1	1
g	g	a	1	0
h	g	c	0	0

Show that the same output sequences are obtained for both the state table of the previous problem and the reduced state table from the previous problem. The state-circuit starts from state a, and the input sequence is 101101001.

Ans:

1st turn							2nd turn						
	Present state	Next state		Output			Present state	Next state		Output			
		x=0	x=1	x=0	x=1			x=0	x=1	x=0	x=1		
	a	f	b	0	0		a	f	b	0	0		
	b	d	e b	1	0		b	d	b	1	0		
	c	f	e b	0	0		c	f	b	0	0		
	d	g	a	1	0		d	g d	a	1	0		
	e	d	e	1	0								
	f	f	b	1	1		f	f	b	1	1		
	g	g	a	1	0		g	g	a	1	0		
	h	g	c	0	0		h	g d	c	0	0		
Reduced table													
	Present state	Next state		Output									
		x=0	x=1	x=0	x=1								
	a	f	b	0	0								
	b	d	b	1	0								
	c	f	b	0	0								
	d	d	a	1	0								
	f	f	b	1	1								
	h	d	c	0	0								

Before Reduced												
Time	1	2	3	4	5	6	7	8	9	10	11	
Present state	a	b	d	a	b	d	a	f	b	d	g	
Input	1	0	1	1	0	1	0	1	0	0	1	
Next State	b	d	a	b	d	a	f	b	d	g	a	
Output	0	1	0	0	1	0	0	1	1	1	0	
After Reduced												
Time	1	2	3	4	5	6	7	8	9	10	11	
Present state	a	b	d	a	b	d	a	f	b	d	d	
Input	1	0	1	1	0	1	0	1	0	0	1	
Next State	b	d	a	b	d	a	f	b	d	d	a	
Output	0	1	0	0	1	0	0	1	1	1	0	