

Chapter 7

Memory and Programmable Logic

1

Outline

- Random-Access Memory
- Memory Decoding
- Error Detecting and Correction
- Read-Only Memory
- Programmable Logic Array
- Programmable Array Logic
- Sequential Programmable Devices


Introduction

- A memory unit
 - is a storage to provide and to receive binary information.
 - is a collection of cells stores binary information
- RAM – Random-Access Memory
 - To accept new information for storage to be available later for use
 - Memory *read* operation
 - Memory *write* operation
- ROM – Read-Only Memory
 - The information inside can not be altered by writing.
 - A *programmable logic device* specified by some hardware procedure.


3

Introduction

- Programmable Logic Device (PLD)
 - ROM– data is written in when memory is fabricated.
 - PLA– programmable logic array: data is written in through burning machine.
 - PAL– programmable array logic: data is written in through burning machine.
 - FPGA– field-programmable gate array: data is written in through download port from external system.
 - programmable logic blocks
 - programmable interconnects

 

(a) Conventional symbol

 


(b) Array logic symbol

4

Random-Access Memory

■ Characteristics

 - The time it takes to transfer data to or from any desired location is always the same.
- The communication between a memory and its environment is achieved through
 - Data input lines,
 - Data output lines,
 - Address selection lines, and
 - Control lines (read and write).



■ A memory unit (width)

- stores binary information in groups of bits (words)
- 8 bits (a byte), 2 bytes, 4 bytes

5

Memory Content Array

- A memory with k -bit address has 2^k data. (depth)

- (depth) x (width) memory

- Ex. An 1k*16 Memory

Memory address		Memory content
Binary	Decimal	
0000000000	0	1011010101011101
0000000001	1	1010101110001001
0000000010	2	0000110101000110
	⋮	⋮
1111111101	1021	1001110100010100
1111111110	1022	0000110100011110
1111111111	1023	1101111000100101

6

Write and Read Operations

- Write operation
 - Apply the binary address to the address lines
 - Apply the data bits to the data input lines
 - Activate the *write* input
- Read operation
 - Apply the binary address to the address lines
 - Activate the *read* input

Control Inputs to Memory Chip

Memory Enable	Read/Write	Memory Operation
0	X	None
1	0	Write to selected word
1	1	Read from selected word

7

Memory Description in HDL

- Declaration: **reg** [width-:0] memword [0:depth-1]

```
// Read and write operations of memory
// Memory size is 64 words of 4 bits each
module memory(Enable, ReadWrite, Address, DataIn, DataOut);
  input Enable, ReadWrite;
  input [3:0] DataIn;
  input [5:0] Address;
  output [3:0] DataOut;
  reg [3:0] DataOut;
  reg [3:0] Mem [0:63];
  always @ (Enable or ReadWrite)
    if (Enable)
      if (ReadWrite) DataOut = Mem[Address]; // Read
      else Mem[Address] = DataIn; // Write
      else DataOut = 4'bz; // High impedance state
endmodule
```

8


Timing Waveforms

- The operation of the memory unit is controlled by an external device such as CPU
- The *access time* is the time required to select a word and read it
- The *cycle time* is the time required to complete a write operation
- Read and write operations must be controlled by CPU and be synchronized with an external clock.

9

Memory Cycle Timing Waveforms

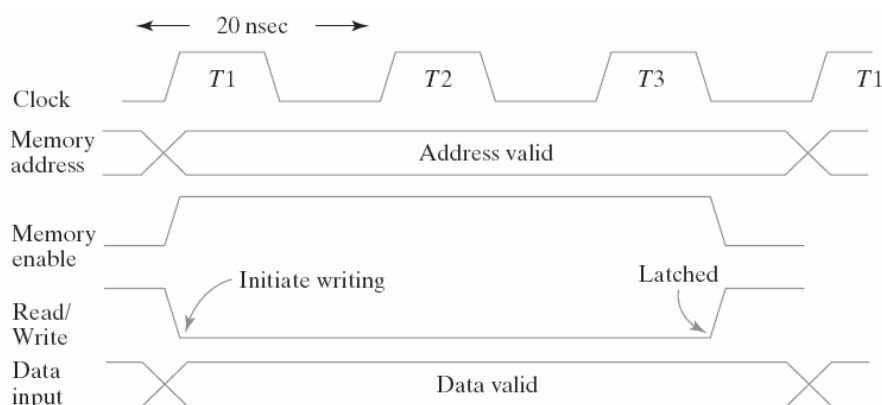
- CPU clock – 50 MHz (20ns period)
- A write cycle
 - T1: Providing the address and input data to the memory, and the read/write control signal
 - Address bus and read/write control must stay active for 50ns
 - The address and data signal must remain stable for a short time after control signal is deactivated.



10

Memory Cycle Timing Waveforms

■ A Read Cycle

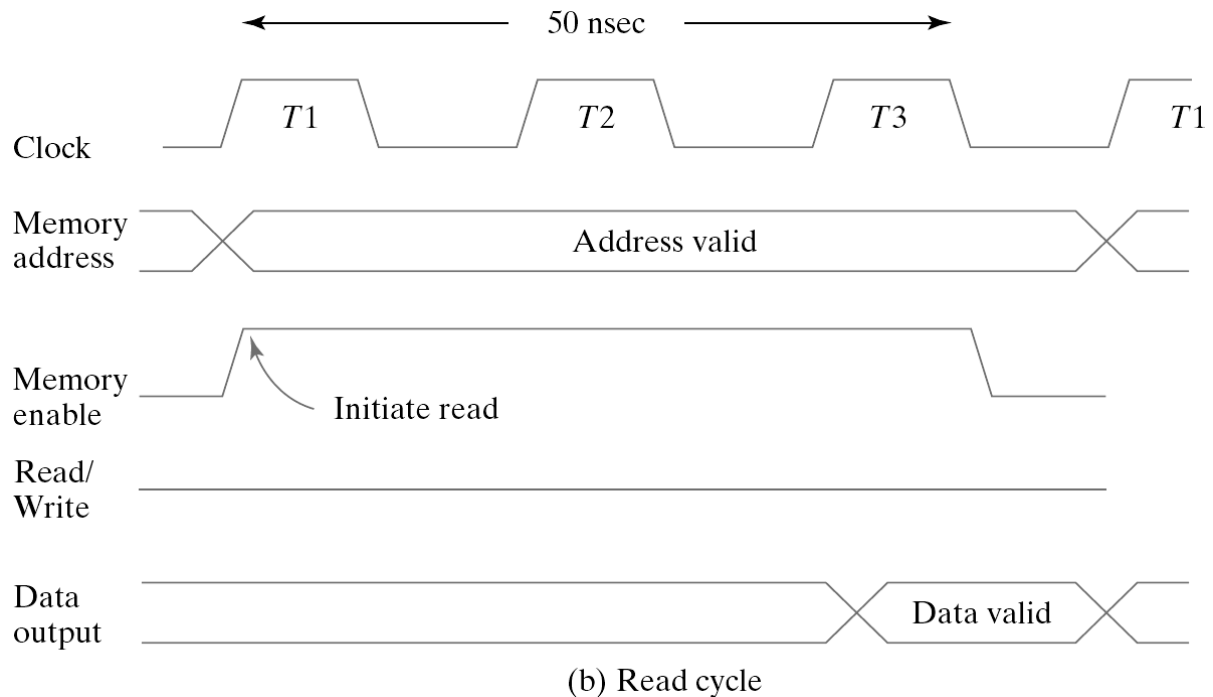

11

Types of Memories

■ Sequential access memory

- The information stored in the medium is available only at certain interval of time.
- The access time depends on the location of the accessed word. The access time is variable.
- A magnetic disk or tape is this type.

■ Random access memory

- The access time is always the same regardless of the particular location of the word.
- Integrated circuit memory is this type

12

Static and Dynamic Memory

- Static memory
 - Information are stored in latches.
 - Data remains valid as long as power is applied.
 - Read/write cycle is shorter.
 - Control is easier
- Dynamic memory
 - Information are stored in the form of charges on capacitors.
 - Refreshing: The stored charge tends to discharge with time and need be refreshed (read and write back) due to leakage current.
 - Power consumption is reduced.
 - Memory capacity is larger.

13



Volatile and Non-Volatile Memory

- *Volatile* Memory
 - Stored information is lost when power is turned off.
 - SRAM, DRAM
- *Non-volatile* Memory
 - Stored information is retained after the removal of power.
 - Magnetic disk or tape
 - ROM
 - EPROM, EEPROM
 - Flash memory
 - Ex. The startup of the computer must use the program in the *non-volatile* memory (ROM).

14

Memory Decoding

 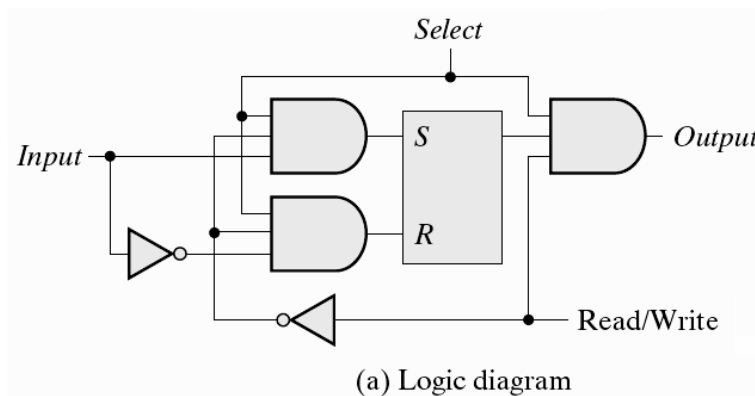- A memory unit has two parts
 - the storage components
 - the decoding circuits to select the memory word
- A basic memory cell model (Virtual, not practical)
 - Actually, the cell is an electronic circuit with four to six transistors.




15

Internal Construction

- A RAM of m (*depth*) words and n (*width*) bits per word
 - $m \times n$ binary storage cells
 - Decoding circuits to select individual words
 - k-to-2k decoder : address input to word line
 - Read/Write control
 - Input data/Output data

16


A 4 × 4 RAM

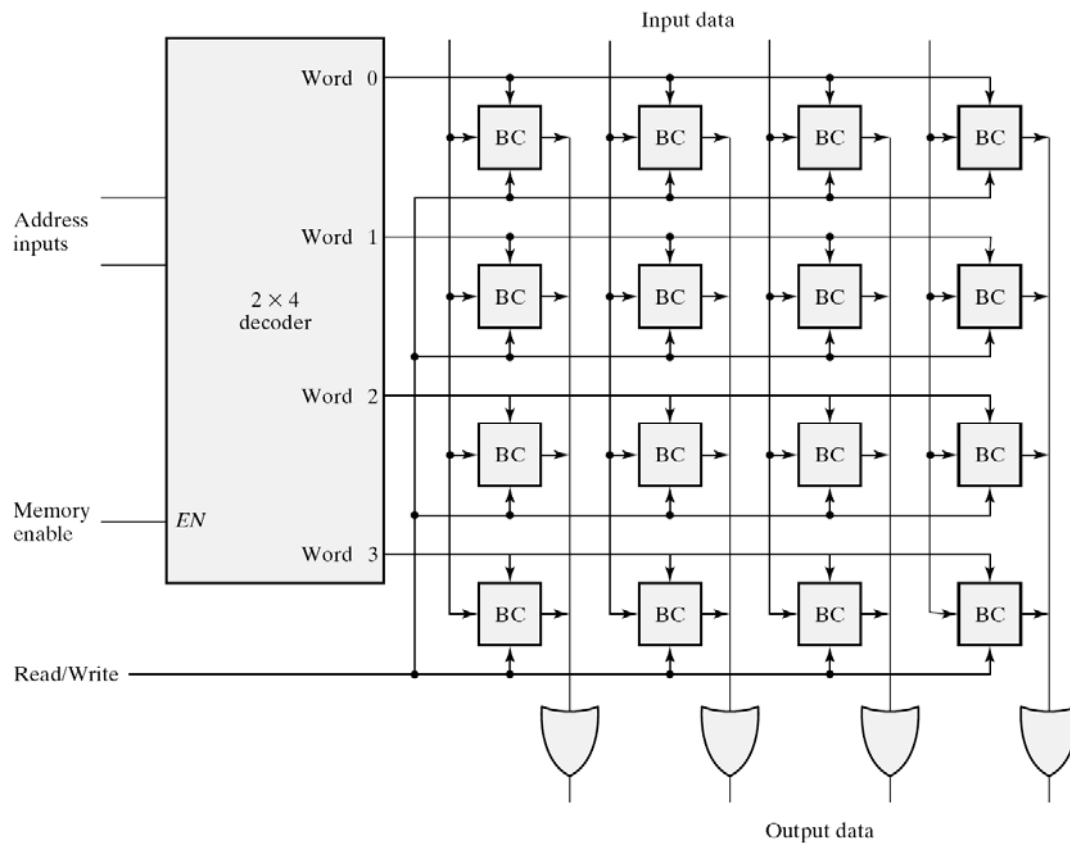

17

Coincident Decoding

 - A two-dimensional selection scheme
 - To reduce the complexity of the decoding circuits
 - To arrange the memory cells in an array that is close as possible to square



18

Example

- A 10-to-1024 decoder
 - 1024 AND gates with 10 inputs per gates
- Two 5-to-32 decoders
 - $2 * (32 \text{ AND gates with 5 inputs per gates})$
- Each word in the memory is selected by the coincidence between 1 of 32 rows and 1 of 32 columns for a total 1,024 words.
- Two dimensional decoding structure reduces the circuit complexity and the cycle time of the memory.

19


Address Multiplexing

- Address multiplexing reduces the number of pins in the IC package (especially DRAM)
 - DRAM is about four times the density of SRAM, thus has larger capacity than SRAM and more address bits.
 - Ex. a 64M*1 DRAM
 - 26-bit address lines
 - In order to reduce the pins in IC package, multiplexing the address lines (especially in DRAM) is utilized in one set of address input pins.

20

Address Multiplexing

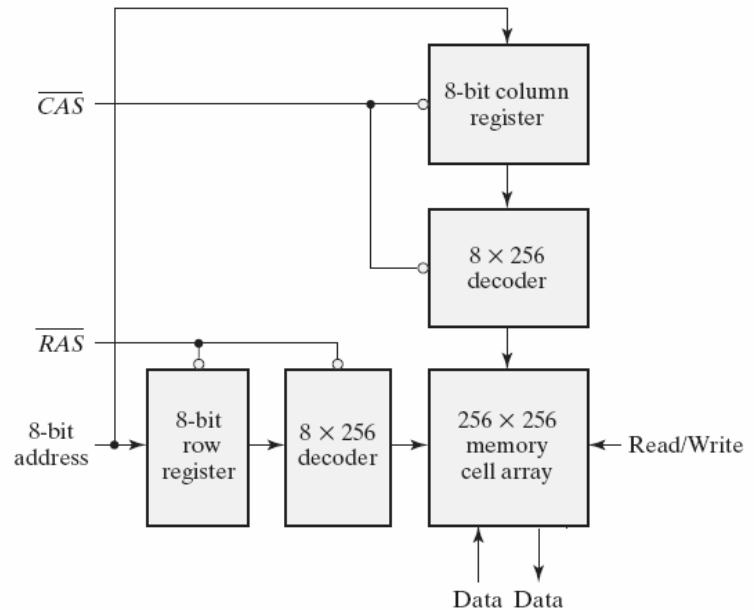- An examples
 - RAS – row address strobe
 - CAS – column address strobe
- 8-bit MSB and 8-bit LSB addresses are multiplexed into column register through 8 input pins




21

RAS, CAS Addressing - Read

- Even to read 1 bit, an entire 64-bit row is read!
- Separate addressing into two cycles: Row Address, Column Address
- Saves on package pins, speeds RAM access for sequential bits!


Read Cycle

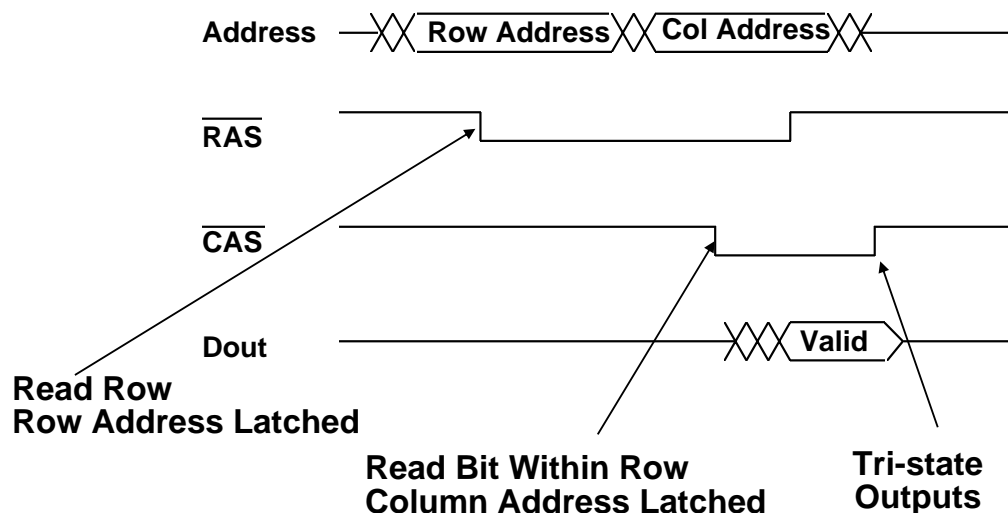

22

RAS, CAS Addressing - Write

Write Cycle Timing

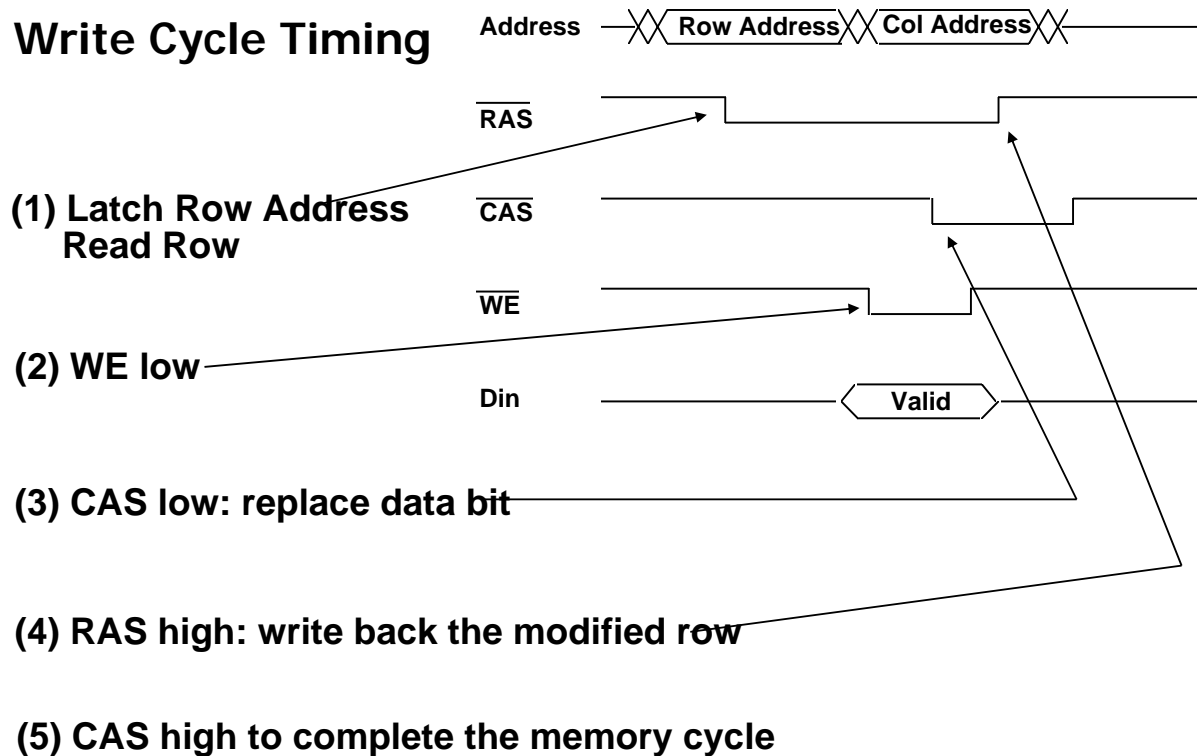

23

Error Detection And Correction

- Error detection and correction improve the reliability of a memory unit.
- A simple error detection scheme
 - A parity bit (Sec. 3-8) is stored with the data and checked after reading out from the memory.
 - A single bit error can be detected, but cannot be corrected.
- An error-correction code
 - To generates multiple parity check bits and be stored with the memory
 - To read out and check a unique pattern, called a syndrome.
 - The specific bit in error can be identified and corrected by implementing erroneous bits.

24

Hamming Code

- k parity bits are added to an n -bit data word
 - $(2^k - 1) \geq n + k$
 - The bit positions are numbered in sequence from 1 to $n + k$
 - Those positions numbered as a power of 2 are reserved for the parity bits
 - The remaining bits are the data bits

25

Hamming Code – Encoding

- Example: 8-bit data word 11000100
 - Include 4 parity bits and the 8-bit word \Rightarrow 12 bits
 $2^k - 1 \geq n + k, n = 8 \Rightarrow k = 4$
Bit position: 1 2 3 4 5 6 7 8 9 10 11 12
 P_1 P_2 1 P_4 1 0 0 P_8 0 1 0 0
 - Calculate the parity bits: even parity – assumption
 $P_1 = \text{XOR of bits (3, 5, 7, 9, 11)} = 1 \oplus 1 \oplus 0 \oplus 0 \oplus 0 = 0$
 $P_2 = \text{XOR of bits (3, 6, 7, 10, 11)} = 1 \oplus 0 \oplus 0 \oplus 1 \oplus 0 = 0$
 $P_4 = \text{XOR of bits (5, 6, 7, 12)} = 1 \oplus 0 \oplus 0 \oplus 0 = 1$
 $P_8 = \text{XOR of bits (9, 10, 11, 12)} = 0 \oplus 1 \oplus 0 \oplus 0 = 1$
 - Store the 12-bit composite word in memory.
Bit position: 1 2 3 4 5 6 7 8 9 10 11 12
 0 0 1 1 1 0 0 1 0 1 0 0

26

Hamming Code – Decoding

- When the 12 bits are read from the memory
 - Check bits are calculated using XOR operation for oddparity

$$C_1 = \text{XOR of bits (1, 3, 5, 7, 9, 11)}$$

$$C_2 = \text{XOR of bits (2, 3, 6, 7, 10, 11)}$$

$$C_4 = \text{XOR of bits (4, 5, 6, 7, 12)}$$

$$C_8 = \text{XOR of bits (8, 9, 10, 11, 12)}$$

- If no error has occurred

Bit position: 1 2 3 4 5 6 7 8 9 10 11 12

0 0 1 1 1 0 0 1 0 1 0 0

$$\Rightarrow \mathbf{C} = C_8 C_4 C_2 C_1 = 0000$$

27

Hamming Code – Decoding

- One-bit error

- error in bit 1

- $C_1 = \text{XOR of bits (1, 3, 5, 7, 9, 11)} = 1$

- $C_2 = \text{XOR of bits (2, 3, 6, 7, 10, 11)} = 0$

- $C_4 = \text{XOR of bits (4, 5, 6, 7, 12)} = 0$

- $C_8 = \text{XOR of bits (8, 9, 10, 11, 12)} = 0$

- $C_8 C_4 C_2 C_1 = 0001$

- error in bit 5

- $C_8 C_4 C_2 C_1 = 0101$

- Two-bit error can not be identified.

- errors in bits 1 and 5

- errors in bit 4

- $C_8 C_4 C_2 C_1 = 0100$

28

Hamming Code

- The Hamming code can be used for data of any length
 - k check bits
 - $2^k - 1 \geq n + k$

Table 7.2

Range of Data Bits for k Check Bits

Number of Check Bits, k	Range of Data Bits, n
3	2–4
4	5–11
5	12–26
6	27–57
7	58–120

29

Single-Error Correction, Double-Error Detection

- Hamming code
 - It can detect and correct only a single error
 - Multiple errors may not be detected.
- Hamming code + a parity bit
 - It can detect double errors and correct a single error.
 - The additional parity bit is the XOR of all the other bits.
 - E.g.: the previous 12-bit coded word
 $001110010100 P_{13} \Rightarrow 0011100101001$ (even parity).


Single-Error Correction, Double-Error Detection

- When the word is read from memory
 - If $P = 0$, the parity is correct; $P = 1$, incorrect
 - Four cases
 - 1. If $C = 0$, $P = 0$, no error
 - 2. If $C \neq 0$, $P = 1$, a single error that can be corrected
 - 3. If $C \neq 0$, $P = 0$, a double error that is detected but cannot be corrected
 - 4. If $C = 0$, $P = 1$, an error occurred in the P_{13} bit

31

Read-Only Memory

 - ROM stores permanent binary information
 - Once the pattern is established in the ROM, it stays within the unit when power is on or off.
- $2^k \times n$ ROM
 - k address input lines
 - enable input(s)
 - three-state outputs




32

 Example

■ 32 x 8 ROM

- 5 (k) – to – 32 (2^k) decoder
- 32 (2^k) outputs of the decoder are connected to each of the eight OR gates, which have 32(2^k) inputs
- 32 x 8 internal programmable connections



33

ROM Programming

■ Programmable interconnections

- close [1]: connected to high voltage
- open [0]: ground left
- A fuse that can be blown by applying a high voltage pulse

Example


ROM Truth Table (Partial)

Inputs					Outputs							
I_4	I_3	I_2	I_1	I_0	A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
		\vdots						\vdots				
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1

34

Programmable Interconnections

 - ROM programming according to ROM table using fusing.



35

Combinational Circuit Implementation

- The internal operation of ROM can be interpreted in two ways.
 - A memory contains a fixed pattern of stored words.
 - A unit that implements a combination circuit as sum of minterms in Section 4-8.
- ROM: a decoder + OR gates
 - a Boolean function = sum of minterms
 - Example: $A_7 = (I_4, I_3, I_2, I_1, I_0) = \Sigma(0, 2, 3, \dots, 29)$
 - For an n -input, m -output combinational circuit
 $\Rightarrow 2^n \times m$ ROM
- Design procedure:
 1. Determine the size of ROM
 2. Obtain the programming truth table of the ROM
 3. The truth table = the fuse pattern

36


Example

- A combination circuit has 3 inputs, 6 outputs
- $B_1 = 0, B_0 = A_0$
- 8 x 4 ROM is used.

Inputs			Outputs						Decimal
A_2	A_1	A_0	B_5	B_4	B_3	B_2	B_1	B_0	
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	1	9
1	0	0	0	1	0	0	0	0	16
1	0	1	0	1	1	0	0	1	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	0	0	0	1	49

37

ROM Implementation

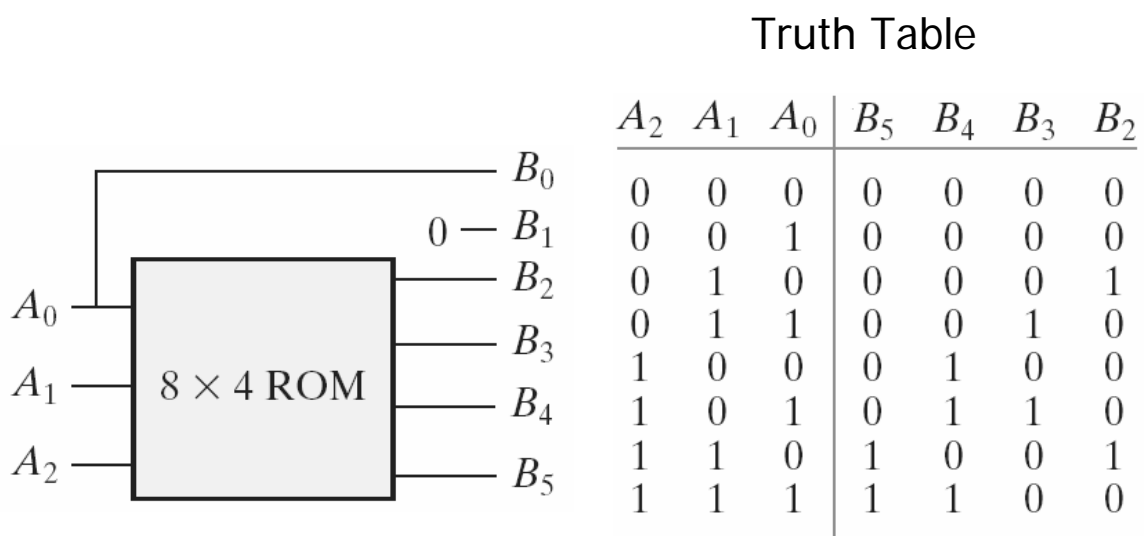

38

Types of ROM

- Mask programming ROM
 - Data is programmed by IC manufacturers
 - It is economical if a large quantity of the same ROM
- PROM: Programmable ROM
 - Fuses in the ROM are blown by high-voltage pulse
 - Universal programmer can program PROM one time.
- EPROM: erasable PROM
 - Floating gate
 - The data in the ROM can be erased by ultraviolet light.
- EEPROM: electrically erasable PROM
 - Longer time is needed to write
 - Flash ROM
 - Limited times of write operations


39

Combinational PLDs


- PLD : Programmable logic device
- Programmable two-level logic
 - Sum of products
 - an AND array and an OR array



(a) Programmable read-only memory (PROM)

 

(b) Programmable array logic (PAL)

 

(c) Programmable logic array (PLA)

40

Programmable Logic Array


- PLA has two main parts
 - An array of programmable AND gates
 - can generate any product terms of the inputs
 - An array of programmable OR gates
 - can generate the sums of the products
- PLA is more flexible than programmable ROM
 - PLA uses any combination of products while programmable ROM uses sum of minterms
- PLA uses less circuits than programmable ROM
 - Only the needed product terms are generated in PLA while all the minterms must be generated in programmable ROM.

41

Programmable Logic Array

- An example:

 - $F_1 = AB' + AC + A'BC'$
- $F_2 = (AC + BC)'$
- XOR gates can invert the outputs



42

PLA Programming Table

- PLA programming table
 - specify the fuse map
 - 1st column: List the product terms numerically
 - 2nd column: Specify the required paths between inputs and AND gates.
 - 3rd column: Specify the required paths between the AND gates and OR gates.
 - (T)(C) stands for true or complement for programming XOR gate.

			Inputs			Outputs (T) (C)	
Product Term			A	B	C	F₁	F₂
AB'	1		1	0	—	1	—
AC	2		1	—	1	1	1
BC	3		—	1	1	—	1
$A'BC'$	4		0	1	0	1	—

43

Characteristics of PLA

- The size of a PLA is determined by
 - The number of inputs
 - The number of product terms (AND gates)
 - The number of outputs (OR gates)
- When implementing with a PLA
 - One must reduce the number of distinct product terms before implementation.
 - The number of terms in a product is not important.
- Mask programmable and field programmable

44

Example

■ Example

- $F_1(A, B, C) = \Sigma(0, 1, 2, 4)$; $F_2(A, B, C) = \Sigma(0, 5, 6, 7)$
- both the true value and the complement of the function should be simplified to check

$A \backslash BC$		B			
		00	01	11	10
A	0	m_0 1	m_1 1	m_3 0	m_2 1
	1	m_4 1	m_5 0	m_7 0	m_6 0

$A \backslash BC$		B			
		00	01	11	10
A	0	m_0 1	m_1 0	m_3 0	m_2 0
	1	m_4 0	m_5 1	m_7 1	m_6 1

$$F_1 = A'B' + A'C' + B'C'$$

$$= (AB + AC + BC)'$$

$$F_2 = AB + AC + A'B'C'$$

$$= (A'B + A'C + AB'C')'$$

45

PLA Programming Table

- $F_1 = (AB + AC + BC)'$
- $F_2 = AB + AC + A'B'C'$


PLA programming table

		Inputs			Outputs	
					(C)	(T)
Product term		A	B	C	F_1	F_2
AB	1	1	1	–	1	1
AC	2	1	–	1	1	1
BC	3	–	1	1	1	–
$A'B'C'$	4	0	0	0	–	1

46

Programmable Array Logic

 
- A programmable AND array and a fixed OR array
 - The PAL is easier to program, but is not as flexible as the PLA



47

PAL Structure

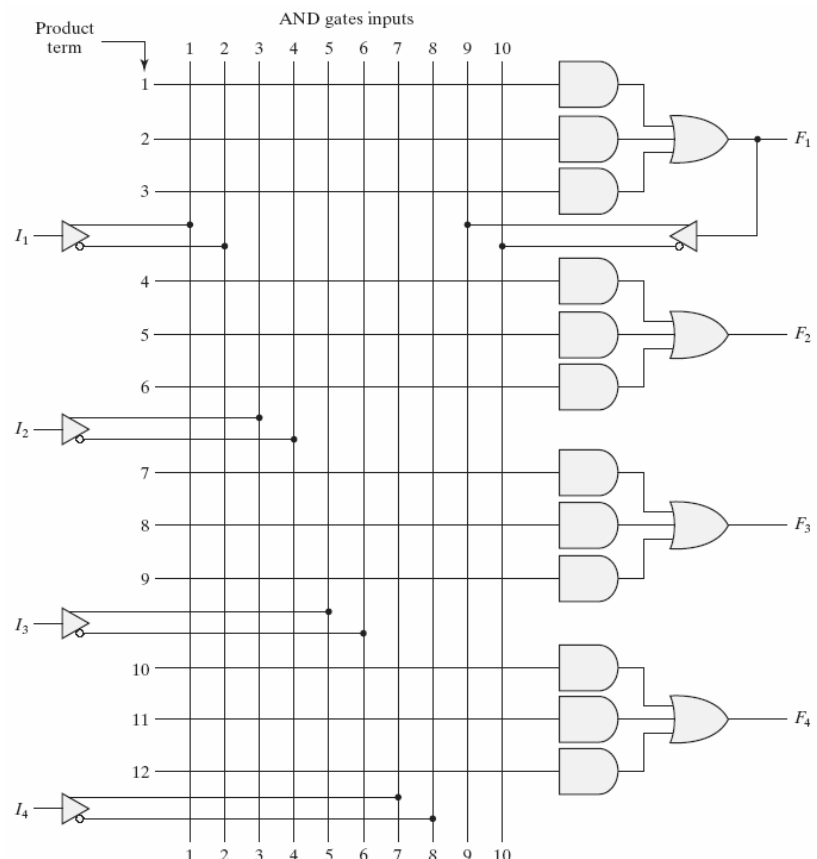- An example PAL
- product terms cannot be shared.



48

An Example Implementation

$$w(A,B,C,D) = \Sigma (2, 12, 13)$$

$$x(A,B,C,D) = \Sigma (7, 8, 9, 10, 11, 12, 13, 14)$$

$$y(A,B,C,D) = \Sigma (0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$$

$$z(A,B,C,D) = \Sigma (1, 2, 8, 12, 13)$$

■ Simplify the functions

$$w = ABC' + A'B'CD'$$

$$x = A + BCD$$

$$y = A'B + CD + B'D'$$

$$z = ABC' + A'B'CD' + AC'D' + A'B'C'D$$

$$= w + AC'D' + A'B'C'D$$

49


PAL Programming Table

Product Term	AND Inputs				w	Outputs
	A	B	C	D		
1	1	1	0	—	—	$w = ABC' + A'B'CD'$
2	0	0	1	0	—	
3	—	—	—	—	—	
4	1	—	—	—	—	$x = A + BCD$
5	—	1	1	1	—	
6	—	—	—	—	—	
7	0	1	—	—	—	$y = A'B + CD + B'D'$
8	—	—	1	1	—	
9	—	0	—	0	—	
10	—	—	—	—	1	$z = w + AC'D' + A'B'C'D$
11	1	—	0	0	—	
12	0	0	0	1	—	

50


Programmed PLA
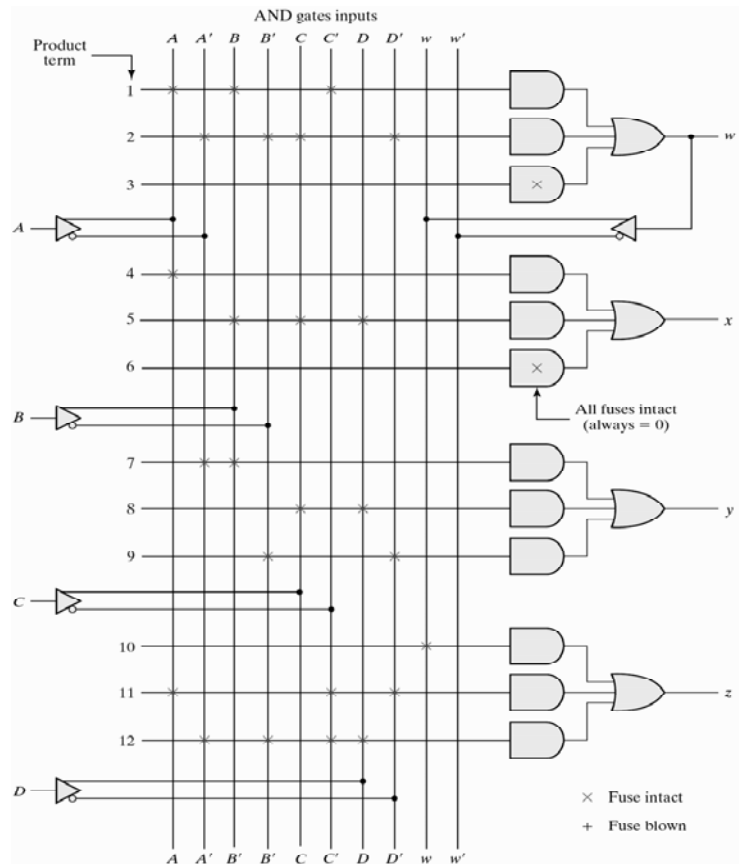
$$\begin{aligned}
 w &= ABC' + A'B'CD' \\
 x &= A + BCD \\
 y &= A'B + CD + B'D' \\
 z &= w + AC'D' + A'B'C'D
 \end{aligned}$$




Sequential Programmable Devices

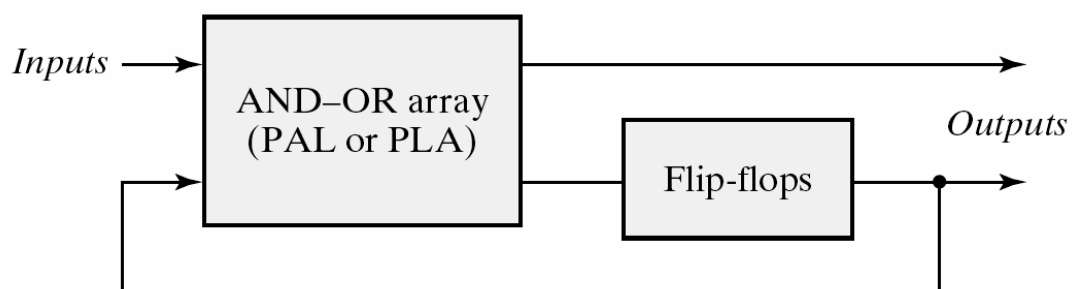- Sequential programmable devices include both programmable gates and flip-flop.
- Three major types of sequential programmable devices
 - SPLD : Sequential programmable logic device
 - CPLD : Complex programmable logic device
 - FPGA : Field programmable gate array



Sequential PLD

 - A PAL or PLA is modified by including a number of flip-flops
 - Sequential PLD macrocell
 - A typical SPLD contains 8-10 macrocells



53


Sequential PLD

- Programming features:
 - AND array
 - use or bypass the flip-flop
 - select clock edge polarity
 - preset or clear for the register
 - complement an output
 - programmable input/output pins

54

Example

■ Altera macrocell

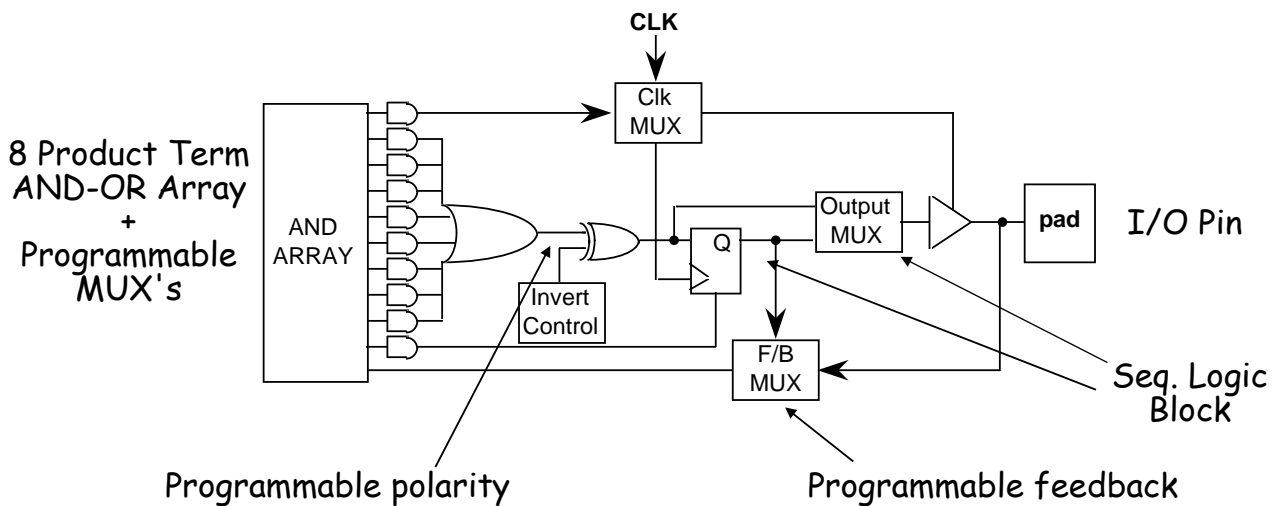


55

CPLD

■ Complex PLD

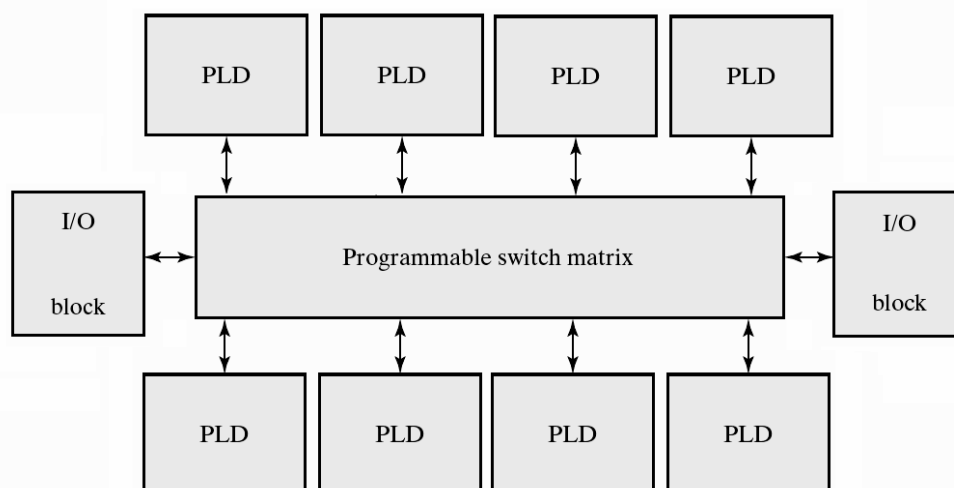- Puts a lot of PLDs on a chip
- Adds wires between them whose connections can be programmed
- Uses fuse/EEPROM technology



56


FPGA

- Field-Programmable Gate Array
 - Emulate gate array technology
 - Hence *Field Programmable Gate Array*
 - You need:
 - A way to implement logic gates
 - A way to connect them together
 - SRAM is often used to configure the combinational circuit function. (Volatile)
- PALs, PLAs = 10 - 100 Gate Equivalents
- Field Programmable Gate Arrays = FPGAs
 - 100 - 1000(s) of Gate Equivalents

57

Field-Programmable Gate Arrays

 - Logic blocks
 - To implement combinational and sequential logic
- Interconnect
 - Wires to connect inputs and outputs to logic blocks
- I/O blocks
 - Special logic blocks at periphery of device for external connections
- Key questions:
 - How to make logic blocks programmable?
 - How to connect the wires?



58

Basic Xilinx Architecture

