

Sequential Logic Examples

Hsi-Pin Ma

<http://lms.nthu.edu.tw/course/40757>

Department of Electrical Engineering
National Tsing Hua University

Binary Up Counter

```

`define CNT_BIT_WIDTH 4
module bincnt(
    q, // output
    clk, // global clock
    rst_n // active low reset
);


output [`CNT_BIT_WIDTH-1:0] q; // output
input clk; // global clock
input rst_n; // active low reset

reg [`CNT_BIT_WIDTH-1:0] q; // output (in always block)
reg [`CNT_BIT_WIDTH-1:0] q_tmp; // input to dff (in always block)

// Combinational logics
always @*
    q_tmp = q + 1'b1;

// Sequential logics: Flip flops
always @(posedge clk or negedge rst_n)
    if (~rst_n) q <= `CNT_BIT_WIDTH'd0;
    else q <= q_tmp;

endmodule
  
```

 

Frequency Divider

```

`define FREQ_DIV_BIT 27
module freqdiv(
  clk_out, // divided clock output
  clk, // global clock input
  rst_n // active low reset
);

output clk_out; // divided output
input clk; // global clock input
input rst_n; // active low reset


reg clk_out; // clk output (in always block)
reg [FREQ_DIV_BIT-2:0] cnt; // remainder of the counter
reg [FREQ_DIV_BIT-1:0] cnt_tmp; // input to dff (in always block)

// Combinational logics: increment, neglecting overflow
always @*
  cnt_tmp = {clk_out,cnt} + 1'b1;

// Sequential logics: Flip flops
always @(posedge clk or negedge rst_n)
  if (~rst_n) {clk_out, cnt} <= `FREQ_DIV_BIT'd0;
  else {clk_out,cnt} <= cnt_tmp;

endmodule

```

 


cnt_tmp[26:0]

cnt[26:0]

Modularized Shift Register

Shift Register

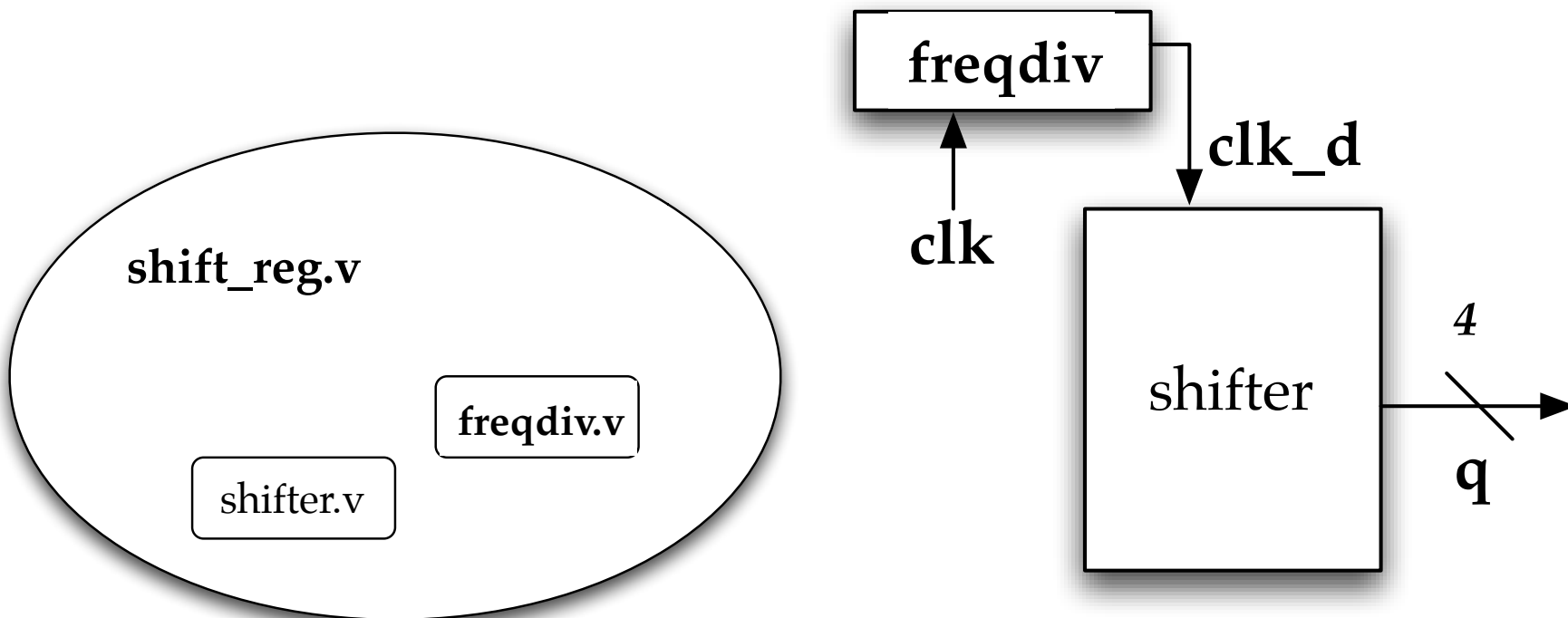

```


`define BIT_WIDTH 4
module shifter(
  q, // shifter output
  clk, // global clock
  rst_n // active low reset
);

output [^BIT_WIDTH-1:0] q; // output
input clk; // global clock
input rst_n; // active low reset

reg [^BIT_WIDTH-1:0] q; // output

// Sequential logics: Flip flops
always @(posedge clk or negedge rst_n)
  if (~rst_n)
    begin
      q<=`BIT_WIDTH'b0001;
    end
    else
    begin
      q[0]<=q[3];
      q[1]<=q[0];
      q[2]<=q[1];
      q[3]<=q[2];
    end
endmodule
  
```

shifter.v

 

Top Module (shift_reg.v)

```
`define BIT_WIDTH 4
module shift_reg(
    q, // LED output
    clk, // global clock
    rst_n // active low reset
);

output [`BIT_WIDTH-1:0] q; // LED output
input clk; // global clock
input rst_n; // active low reset

wire clk_d; // divided clock
wire [`BIT_WIDTH-1:0] q; // LED output
```

1

```
// Insert frequency divider (freq_div.v)
freqdiv U_FD(
    .clk_out(clk_d), // divided clock output
    .clk(clk), // clock from the crystal
    .rst_n(rst_n) // active low reset
);

// Insert shifter (shifter.v)
shifter U_D(
    .q(q), // shifter output
    .clk(clk_d), // clock from the frequency divider
    .rst_n(rst_n) // active low reset
);

endmodule
```

2

Modularized BCD Counter


Load Default Value for DFFs

- at reset of DFFs

```


always @(posedge clk or negedge rst_n)
  if (~rst_n)
    q <= 0;
  else
    q <= d;
  
```

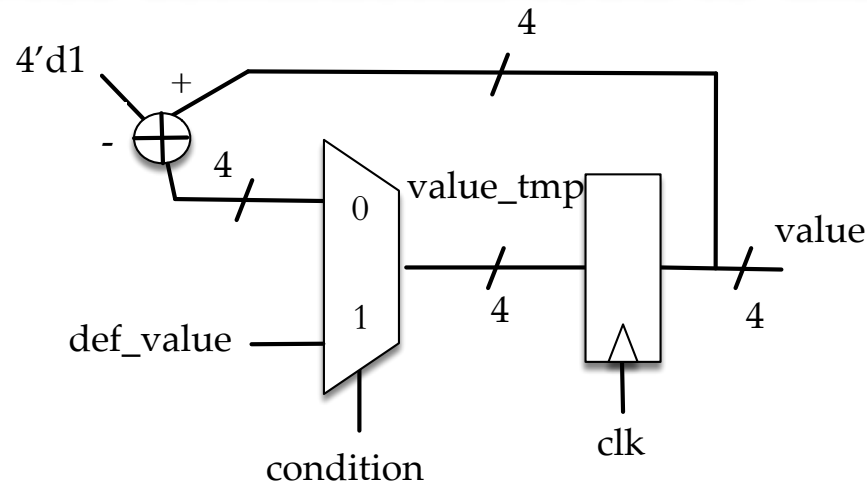- Use MUX for conditional load to the DFFs



- Do not use *initial*

BCD Down-Counter

 



```
// Combinational logics
always @*
  if (value == `BCD_ZERO)
    value_tmp = `BCD_NINE;
  else
    value_tmp = value - `INCREMENT;

// register part for BCD counter
always @(posedge clk or negedge rst_n)
  if (~rst_n) value <= `BCD_ZERO;
  else value <= value_tmp;
```

clk1 and clk2 needed to be synchronized in frequency and phase!!

BCD Down-Counter

  How to use one single clock for different digit counting?



borrow signal in lower digit is the *decrease* control in the upper digit

BCD Down-Counter

```

module dncounter(
    value, // counter output
    borrow, // borrow indicator
    clk, // global clock
    rst_n, // active low reset
    decrease, // counter enable control
    limit // limit for the counter
);
... ..
// Combinational logics
always @*
    if (value==`BCD_ZERO && decrease)
        begin
            value_tmp = limit;
            borrow = `ENABLED;
        end
    else if (value!=`BCD_ZERO && decrease)
        begin
            value_tmp = value - `INCREMENT;
            borrow = `DISABLED;
        end
    else
        begin
            value_tmp = value;
            borrow = `DISABLED;
        end
end

```


```

// register part for BCD counter
always @(posedge clk or negedge rst_n)
    if (~rst_n) value <= `BCD_ZERO;
    else value <= value_tmp;

endmodule

```

2-digit BCD Down-Counter

 

// 30 sec down counter

downcounter Udc0(

.value(digit0), // counter value

.borrow(br0), // borrow indicator

.clk(clk), // global clock signal

.rst_n(rst_n), // low active reset

.decrease(decrease_enable), // counter enable control

.limit(BCD_NINE) // limit for the counter

);

downcounter Udc1(

.value(digit1), // counter value

.borrow(br1), // borrow indicator

.clk(clk), // global clock signal

.rst_n(rst_n), // low active reset

.decrease(br0), // counter enable control

.limit(BCD_FIVE) // limit for the counter

);

counting from 59 to 0