

HW7

1. The memory units that follow are specified by the number of words times the number of bits per word. (1) How many address lines and input-output lines are needed in each case? (2) Give the number of bits stored in the memories in each case. (a) $2M \times 16$ (b) $2G \times 8$.



(a)


- (1) 21 address lines,
16 data input lines,
16 data output lines.
(2) $2^{21} \times 2^4 = 2^{25}$ bits

(b)

- (1) 31 address lines,
8 data input lines,
8 data output lines.
(2) $2^{31} \times 2^3 = 2^{34}$ bits

2. Design a 8×5 RAM.

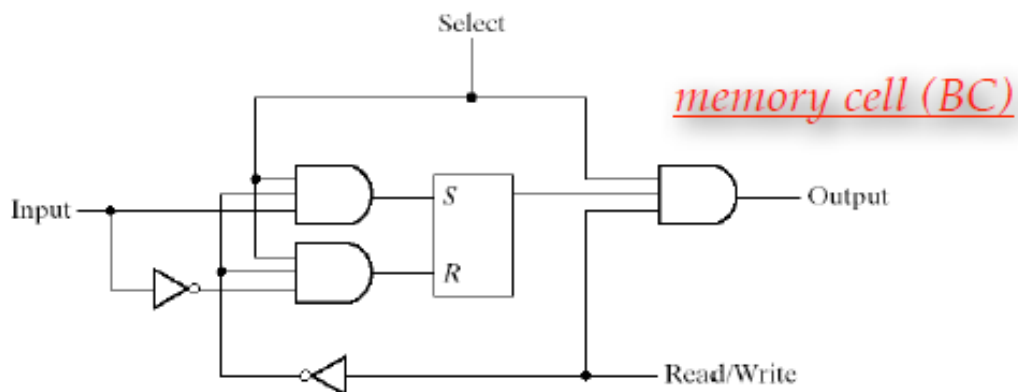 

 

3. A 12-bit Hamming code word containing 8 bits of data and 4 parity bits is read from the memory. What is the original 8-bit data word that was written into memory if the 12-bit word read out is as:
 (a) 011001000110 (b) 101110110100

3. a) 011001000110

$$C_1 = \text{XOR of bits } (1, 3, 5, 7, 9, 11) = 0$$

$$C_2 = \text{XOR of bits } (2, 3, 6, 7, 10, 11) = 1$$

$$C_4 = \text{XOR of bits } (4, 5, 6, 7, 12) = 1$$

$$C_8 = \text{XOR of bits } (8, 9, 10, 11, 12) = 0$$

$$C_8 C_4 C_2 C_1 = (0110)_2 = (6)_{10} \Rightarrow \text{No. 6 bit is wrong}$$

$$\Rightarrow 01100\cancel{0}000110$$

$$\Rightarrow 011000000110 \Rightarrow 10000110$$

$\begin{array}{cccc} 1 & 2 & 4 & 8 \\ \times & \times & \times & \times \end{array}$
 去除 parity bits

(b) 101110110100

$$C_1 = \text{XOR } (1, 3, 5, 7, 9, 11) = 0$$

$$C_2 = \text{XOR } (2, 3, 6, 7, 10, 11) = 1$$

$$C_4 = \text{XOR } (4, 5, 6, 7, 12) = 1$$

$$C_8 = \text{XOR } (8, 9, 10, 11, 12) = 0$$

$$C_8 C_4 C_2 C_1 = (0110)_2 = (6)_{10} \Rightarrow \text{No. 6 bit is wrong}$$

$$\Rightarrow 10111\cancel{0}110100$$

$$\Rightarrow 101111110100 \Rightarrow 11110100$$

$\begin{array}{cccc} 1 & 2 & 4 & 8 \\ \times & \times & \times & \times \end{array}$
 去除 parity bits

4. Tabulate the truth table for an 8x4 ROM that implements the Boolean functions.

(a) $A(X, Y, Z) = \Sigma m(1, 2, 4)$

(b) $B(X, Y, Z) = \Sigma m(3, 5, 7)$


(c) $C(X, Y, Z) = \Sigma m(1, 2, 6, 7)$

(d) $D(X, Y, Z) = \Sigma m(2, 3, 5, 6, 7)$

Truth Table:

Inputs			Outputs			
X	Y	Z	A	B	C	D
0	0	0	0	0	0	0
0	0	1	1	0	1	0
0	1	0	1	0	1	1
0	1	1	0	1	0	1
1	0	0	1	0	0	0
1	0	1	0	1	0	1
1	1	0	0	0	1	1
1	1	1	0	1	1	1


ROM Configuration:

 

(3x8 decoder 可參考第 2 題的設計)

5. FPGA: The logic cell has four inputs (A, B, C, D) and one output (Z).
- (a) Draw the logic diagram of a simple logic cell with 4-bit inputs and 1-bit outputs.
- (b) Explain how the logic cell can finish the sum function in a full adder. ($Z=A+B+C$)

(a)

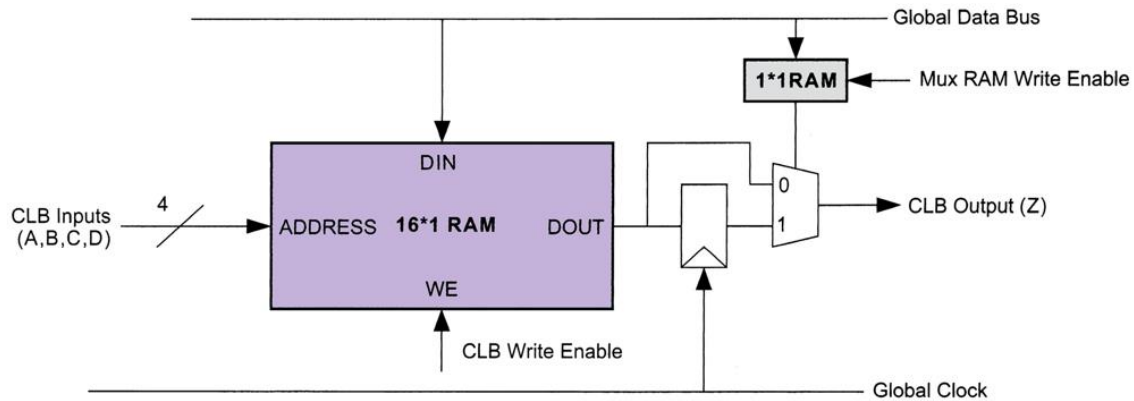

若FPGA需要做Sequential Circuit，1*1 RAM內的data=1；反之若為Combinational Circuit，1*1 RAM內的data=0。

(b)

address	A	B	C	D	Dout
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	1
9	1	0	0	1	1
10	1	0	1	0	0
11	1	0	1	1	0
12	1	1	0	0	0
13	1	1	0	1	0
14	1	1	1	0	1
15	1	1	1	1	1

(sum function : $Dout=A \text{ xor } B \text{ xor } C$)

首先，CLB Write Enable=1，將以上的 LUT 資料存進 16*1 RAM 對應的；存完之後 CLB Write Enable=0，將資料藉由 CLB inputs 獲得 address，再將對應 address 的 data 讀出；而 1*1 RAM 的 data=0，因為 sum function 只需使用 Combination circuit 來實現。