

Chapter 8

Design at the Register Transfer Level

1

Outline

- Register Transfer Level (RTL) Notation
- Algorithmic State Machines (ASMs)
- Design Example
- Sequential Binary Multiplier
- Control Logic
- Design with Multiplexers
- HDL Description of Design Examples

Introduction

- A digital system is a sequential logic system constructed with flip-flops and gates.
 - To specify a large digital system with a state table is very difficult .
 - Modular subsystems
 - Registers, decoders, multiplexers, arithmetic elements and control logic.
 - They are interconnected with datapaths and control signals.

3

Register Transfer Level

- A digital system is represented in register transfer level when it is specified by the three components.
 - 1. The set of registers in the system
 - 2. The operations that are performed on the data in the registers
 - 3. The control that supervises the sequence of operations.
- Register : a group of flip-flops that stores binary information and performs elementary operations.
- Operation: execution on the information stored in register in parallel during one clock cycle. The results may replace the original register or transfer to another register
- Control: initiation of a sequence of operations consisting of timing signals that sequence the operations in a prescribed manner.

4

Operations

- Information Transfer
 - $(R2 \leftarrow R1)$
 - From output of R1 to input of R2
 - Parallel load capability
- Conditioned Transfer
 - (If $(T1 = 1)$ then $(R2 \leftarrow R1)$)
 - Clock transfer occurs during clock edges.
- Two or more Transfer
 - (If $(T3 = 1)$ then $(R2 \leftarrow R1, R1 \leftarrow R2)$)
 - Exchange of the content of R1 and R2 during clock edge, provided that $T3 = 1$.

5


Operation Types

- Four categories of operational types in digital systems.
 - Transfer operations that transfer data from one register to another
 - Arithmetic operations that perform arithmetic on data in register
 - Logic operations that perform bit manipulation of non-numeric data in register
 - Shift operations that shift data in register

6

Algorithmic State Machine (ASM)

- Control logic and data processing in a digital system
- Control signal
 - Initiates a sequence of commands to the data path.
 - Uses the status conditions from datapath as decision variable for determining the sequence of control signals.
- A hardware algorithm is used to describe the objective of the digital design.
- An algorithmic state machine (ASM) is a flow-chart method which can be used to defined the digital hardware algorithm.

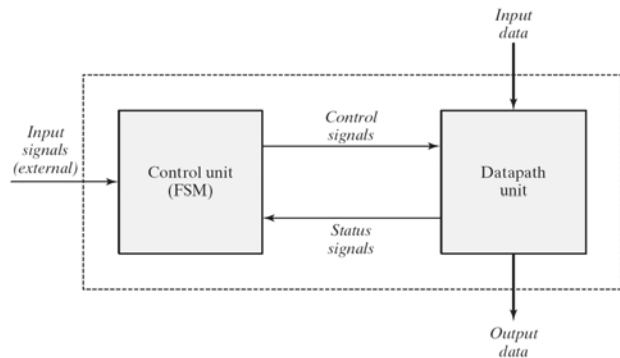

7


ASM Chart

- The ASM chart is a special type of flow-chart for describing the sequential operations of a digital system.
- Three basic element
 - The state box
 - The decision box
 - The condition box
- They are connected by directed edges indicating the sequential precedence and evolution of the states as the machine operates.

8

State Box

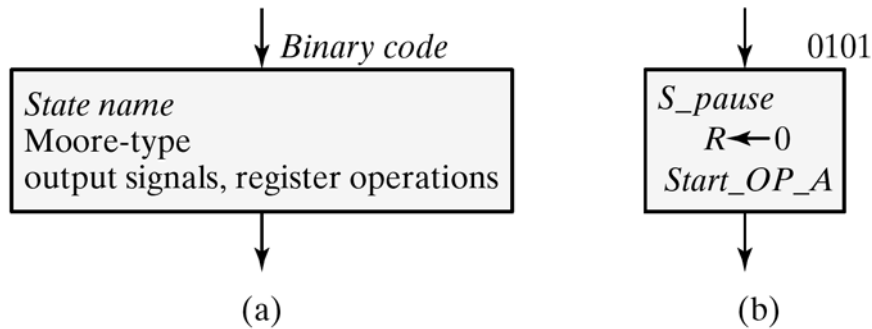
- State box is rectangular
 - Register Operation or Output
 - State Specification



9

Decision Box


 
- The decision box is diamond-shaped box
 - The effect of an input on the control system
 - Indication of decision condition



10


Condition Box

  - The condition box is oval-shaped.
 - Unique to ASM chart
 - The input path must come from one of the exit paths of decision box
 - The operation or output is generated if input condition is satisfied.



11


ASM Block Example

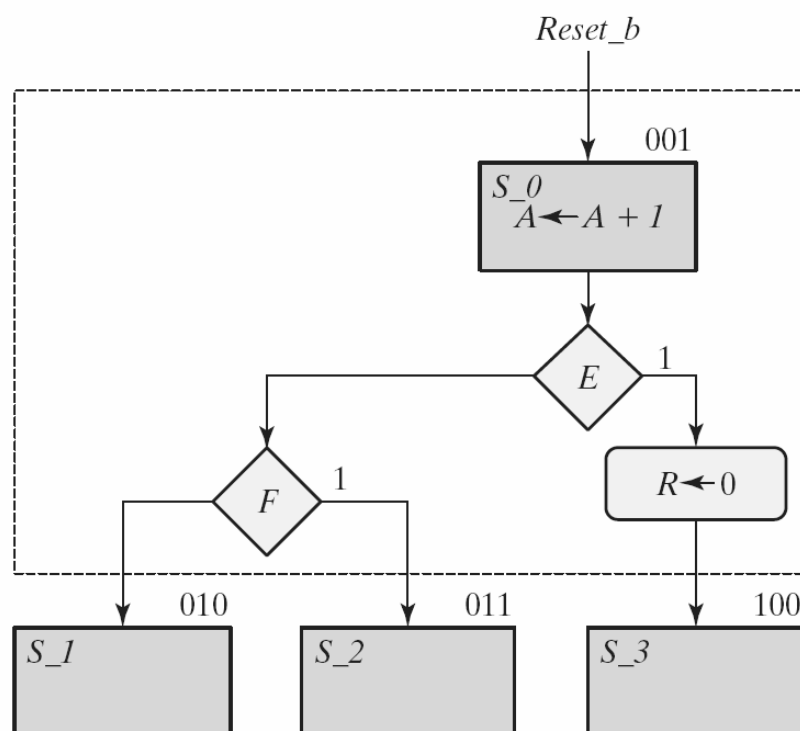

12

Equivalent State Diagram

 
- Each block in ASM chart describes the state of the system during one clock-pulse interval.
- Each state block is equivalent to a state in a sequential circuit, thus, is easy to convert to a state diagram.



13

Timing Consideration

 - The timing for all registers and flip-flops in a digital system is controlled by a master-clock.
- In ASM chart, all operations specified in a block must occur during the edge transition of the clock pulse.
 - Example of state transition



14

ASMD Chart

- Contrasted between Algorithmic State Machine and Datapath (ASMD) charts & ASM charts.
 - An ASMD chart does not list register operations within a state box.
 - The edges of an ASMD chart are annotated with register operations that are concurrent with the state transition indicated by the edge.
 - An ASMD chart includes conditional boxes identifying the signals which control the register operations that annotate the edges of the chart.
 - An ASMD chart associates register operations with state transitions rather than with state.

15

ASMD Chart

- Designing an ASMD chart has three steps:
 - Form an ASM chart displaying only how the inputs to the controller determine its state transitions.
 - Convert the ASM chart to an ASMD chart by annotating the edges of the ASM chart to indicate the concurrent register operations of the datapath unit.
 - Modify the ASMD chart to identify the control signals that are generated by the controller and the cases where the indicated register operations in the datapath unit.

16

Design Example I - Counter

■ Specification


- Two flip-flops, E and F.
- One 4-bit binary counter A ($A_3A_2A_1A_0$)
- Start signal S
- Counter bits $A_4 A_3$ determine the sequence of operations
 - If $A_2 = 0$, E is 0, and count continues.
 - If $A_2 = 1$, E is 1, then if $A_3 = 0$, the count continues, but if $A_3 = 1$, F is 1 on next cycle, system stops counting.
 - If $Start = 0$, the system remains in initial state, but if $Start = 1$, the operation cycle repeats.

17

Design Example

Block Diagram

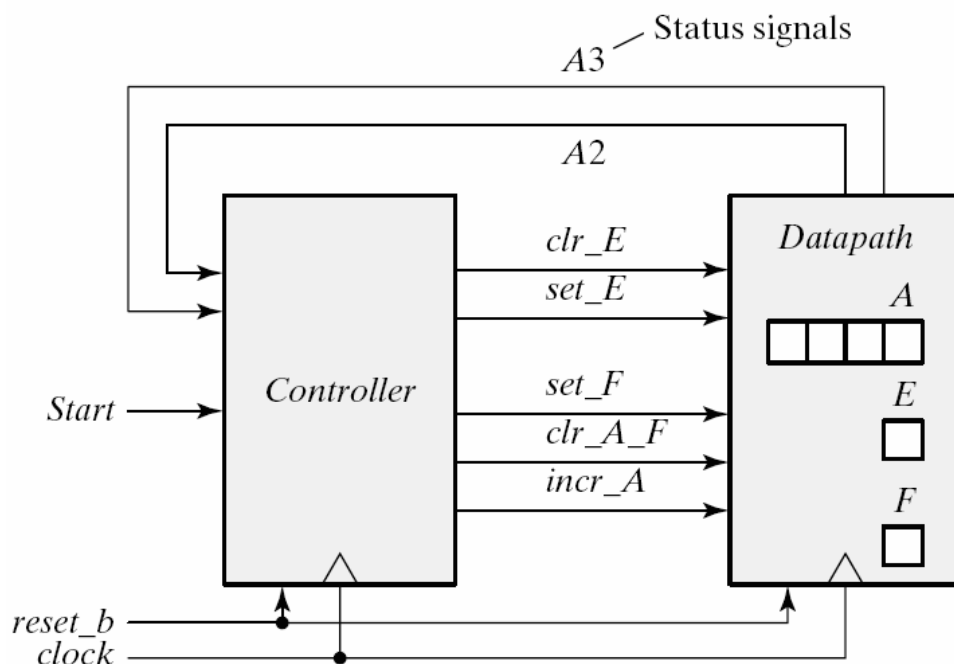Note: A3 denotes A[3],
A2 denotes A[2],
<= denotes nonblocking assignment
reset_b denotes active-low reset condition





18

ASMD Charts


Asynchronous Reset

Synchronous Reset

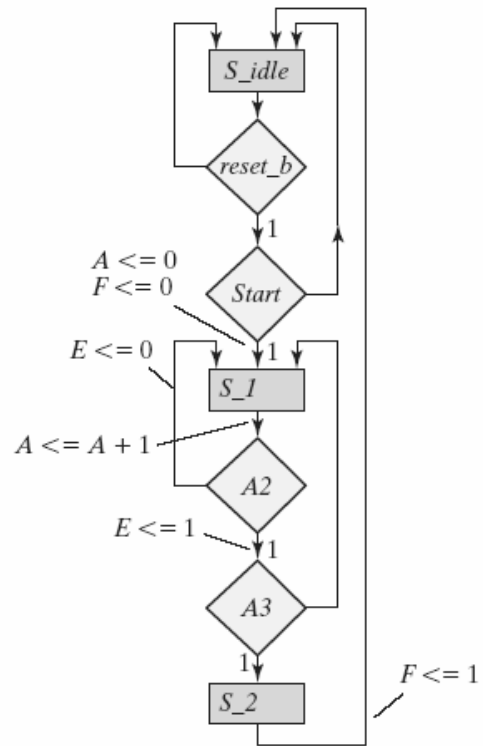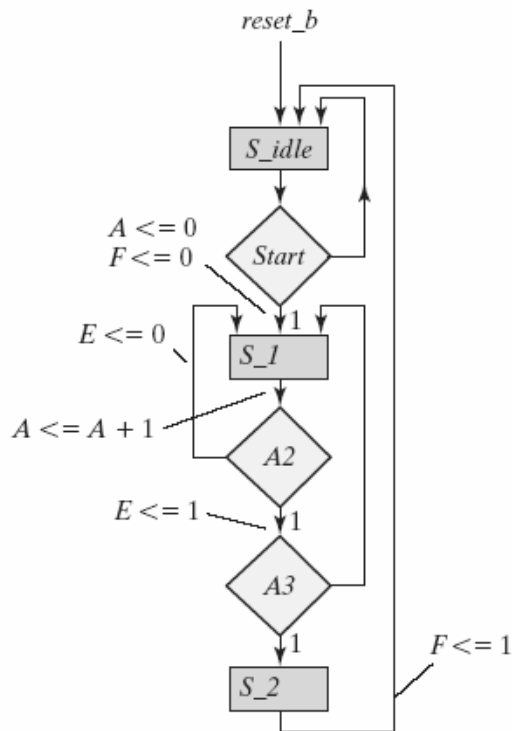

19

ASMD Charts

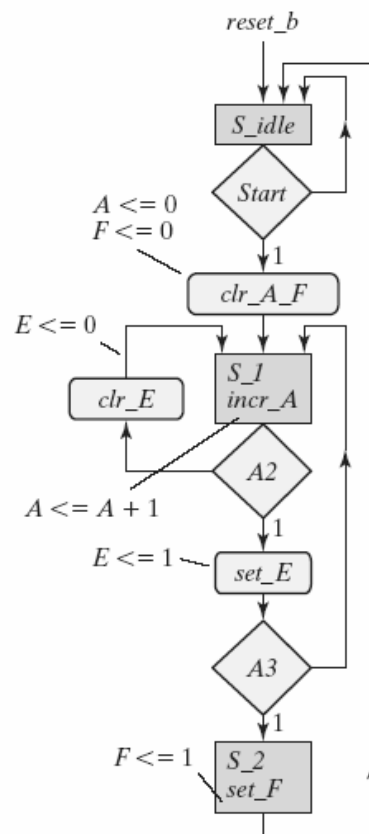

20

Timing Sequence


Sequence of Operations for Design Example

Counter				Flip-Flops		Conditions	State
A_3	A_2	A_1	A_0	E	F		
0	0	0	0	1	0	$A_2 = 0, A_3 = 0$	S_I
0	0	0	1	0	0		
0	0	1	0	0	0		
0	0	1	1	0	0		
0	1	0	0	0	0	$A_2 = 1, A_3 = 0$	
0	1	0	1	1	0		
0	1	1	0	1	0		
0	1	1	1	1	0		
1	0	0	0	1	0	$A_2 = 0, A_3 = 1$	
1	0	0	1	0	0		
1	0	1	0	0	0		
1	0	1	1	0	0		
1	1	0	0	0	0	$A_2 = 1, A_3 = 1$	
1	1	0	1	1	0		
1	1	0	1	1	1		S_idle

21

Controller and Datapath Design


Design_Example

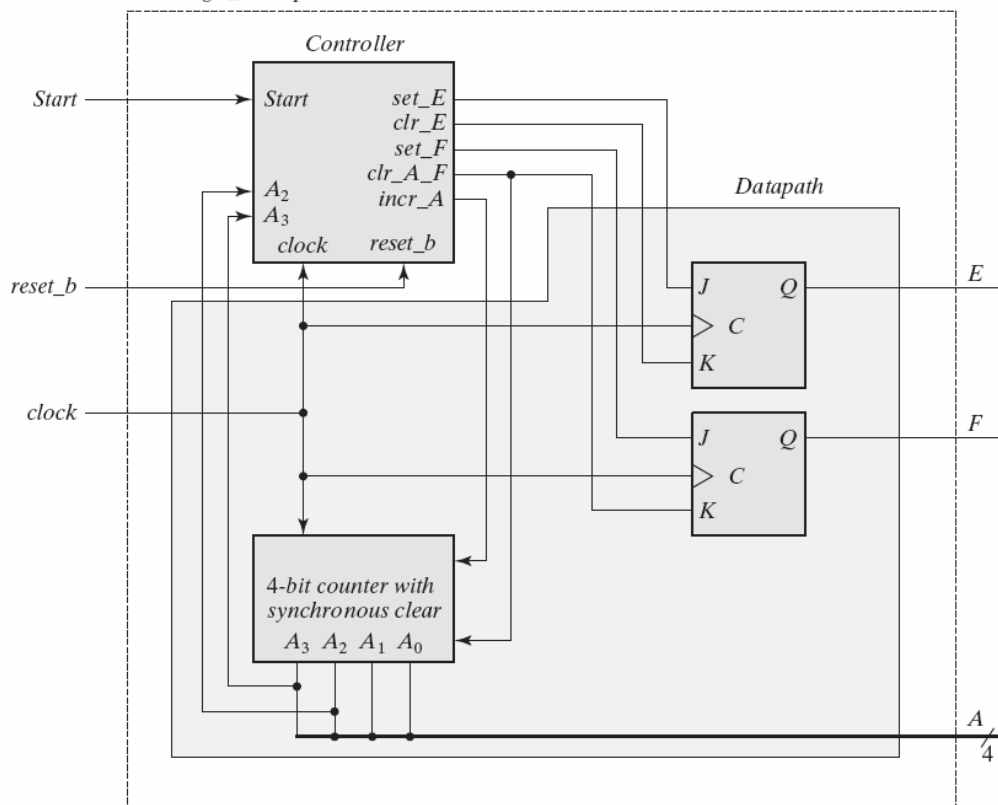

22

Register Transfer Level

■ Register transfer level description

 

$S_idle \longrightarrow S_1, clr_A_F:$ $A \longleftarrow 0, F \longleftarrow 0$
 $S_1 \longrightarrow S_1, incr_A:$ $A \longleftarrow A + 1$
 if ($A_2 = 1$) then $set_E:$ $E \longleftarrow 1$
 if ($A_2 = 0$) then $clr_E:$ $E \longleftarrow 0$
 $S_2 \longrightarrow S_idle, set_F:$ $F \longleftarrow 1$

23

State Table

State Table for the Controller of Fig. 8.10

Present-State Symbol	Present State		Inputs			Next State		Outputs				
	G_1	G_0	$Start$	A_2	A_3	G_1	G_0	set_E	clr_E	set_F	clr_A_F	$incr_A$
S_idle	0	0	0	X	X	0	0	0	0	0	0	0
S_idle	0	0	1	X	X	0	1	0	0	0	1	0
S_1	0	1	X	0	X	0	1	0	1	0	0	1
S_1	0	1	X	1	0	0	1	1	0	0	0	1
S_1	0	1	X	1	1	1	1	1	0	0	0	1
S_2	1	1	X	X	X	0	0	0	0	1	0	0

24

Control

■ Method 1

- Five-variable map using $G_1 G_0 S A_3 A_2$

■ Method 2

- Simply the circuit by inspection and set each flip-flop to 1 for next-state.

- $D_{G1} = S_1 A_3 A_2$

- $D_{G0} = Start\ S_idle + S_1$

– Output

- $set_E = S_1 A_2$

- $clr_E = S_1 A_2'$


- $set_F = S_2$

- $clr_A_F = Start\ S_idle$

- $incr_A = S_1$

25

Logic Diagram

 

26

Sequential Binary Multiplier

- Specification: Binary Multiplication
- Method: Shift left and accumulate (direct way)
- Example: multiplying two binary numbers 10111 (23)₁₀ and 10011 (19)₁₀:

```

      23      10111 multiplicand
      19      10011 multiplier
            
      10111
    10111
  00000
00000
10111
437 110110101 product


```

The product obtained from the multiplication of two n -bit binary numbers can be up to $2n$ bits.

27

Sequential Binary Multiplier

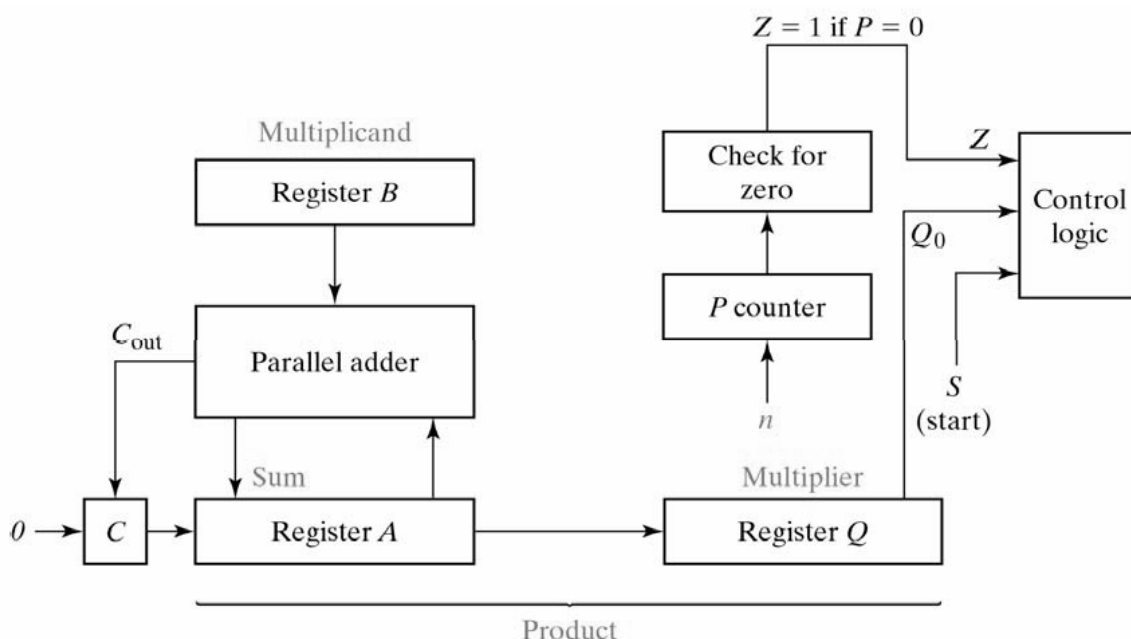- An alternative method: Shift Right and accumulate
- Block Diagram of Binary Multiplier




28

ASM Chart

- Register A: A shift register with parallel load to accept the sum of the adder, and clear to reset to 0.
- Register B and Q: A shift registers with parallel load to received multiplicand and multiplier.
- Counter P: Binary counter with a parallel load to accept a binary constant.
 - Z status register: $Z = 0$ when $P = 0$; $Z = 1$ when $P \neq 0$
- C flip-flop: flip-flop to accept input carry and a synchronous reset.
- Shift right CAQ in the chart
 - $A \leftarrow \text{shr } A, A_{n-1} \leftarrow C$
 - $Q \leftarrow \text{shr } Q, Q_{n-1} \leftarrow A_0$
 - $C \leftarrow 0$



29

Register Configuration

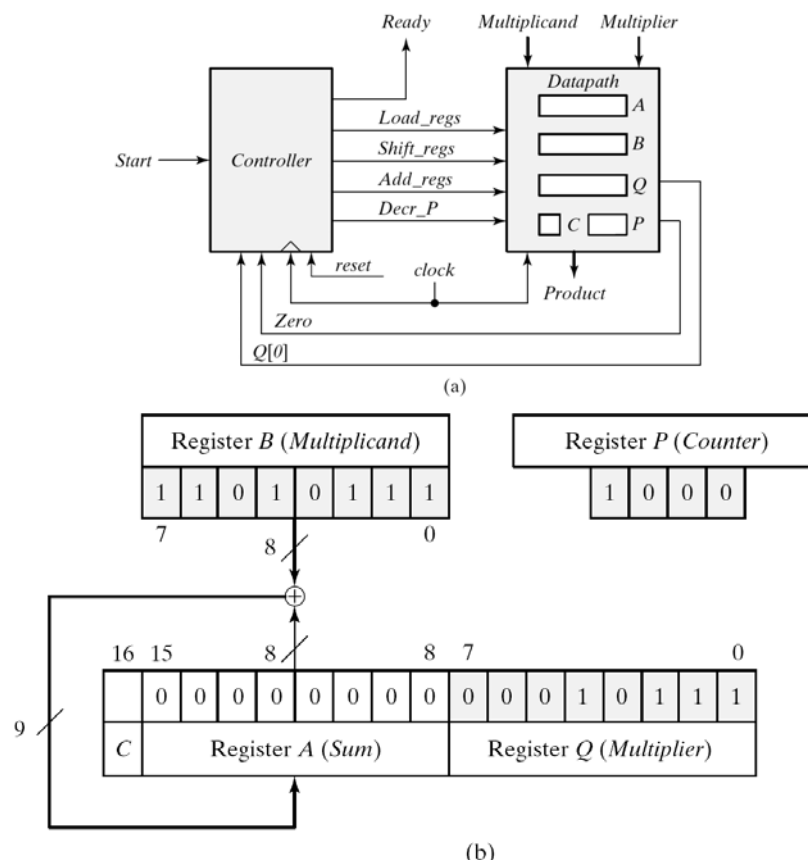

30

ASMD for Binary Multiplier

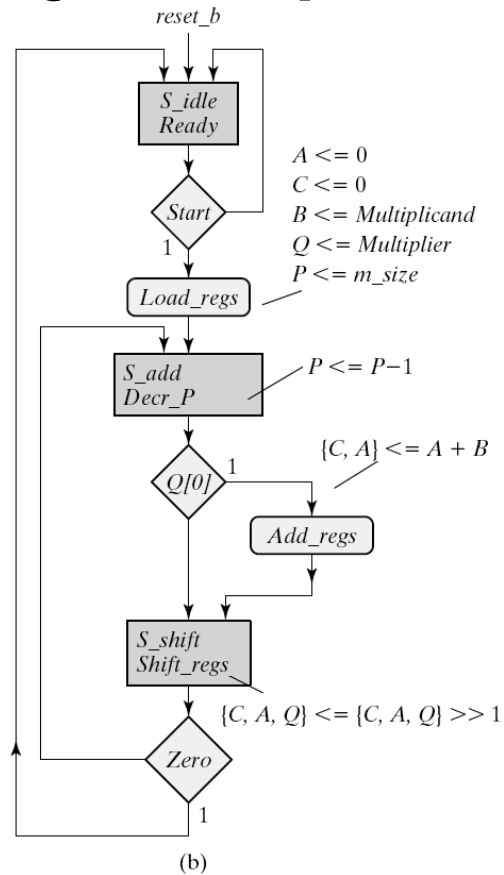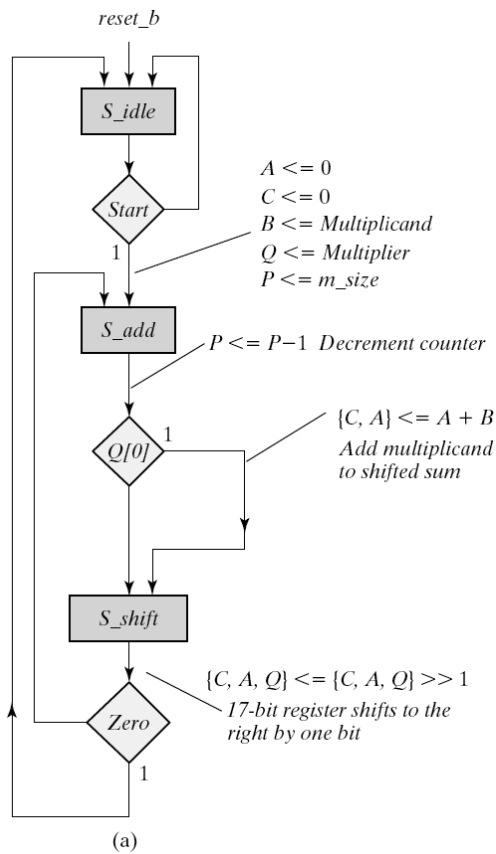

31

Numerical Example

Numerical Example For Binary Multiplier

Multiplicand $B = 10111_2 = 17_H = 23_{10}$

Multiplier $Q = 10011_2 = 13_H = 19_{10}$

Multiplier in Q

$Q_0 = 1$; add B

First partial product

Shift right CAQ

$Q_0 = 1$; add B

Second partial product

Shift right CAQ

$Q_0 = 0$; shift right CAQ

$Q_0 = 0$; shift right CAQ

$Q_0 = 1$; add B

Fifth partial product

Shift right CAQ


Final product in $AQ = 0110110101_2 = 1b5_H$

	C	A	Q	P
0	00000	10011	101	
		<u>10111</u>		
0	10111			100
0	01011	11001		
		<u>10111</u>		
1	00010			011
0	10001	01100		
0	01000	10110	010	
0	00100	01011	001	
		<u>10111</u>		
0	11011			
0	01101	10101	000	

32

Control Logic

 - The design of a digital system has two parts
 - The design of register transfers in the datapath
 - The design of control logic
- The control logic design is a sequential circuit design problem.
- Converting from ASM Chart to state diagram.



State Transition		Register Operations
From	To	
<i>S_idle</i>		Initial state
<i>S_idle</i>	<i>S_add</i>	$A \leq 0, C \leq 0, P \leq dp_width$
<i>S_add</i>	<i>S_shift</i>	$P \leq P - 1$ if ($Q[0]$) then ($A \leq A + B, C \leq C_{out}$)
<i>S_shift</i>		shift right {CAQ}, $C \leq 0$

State Assignment for Control

State	Binary	Gray Code	One-Hot
<i>S_idle</i>	00	00	001
<i>S_add</i>	01	01	010
<i>S_shift</i>	10	11	100

Control Logic and State Assignment

- There are two distinct aspects
 - Establish the required sequence of states. (State Diagram)
 - Provide signals to control the register operations. (register transfer)
- State assignment
 - Binary number
 - Gray code
 - One-hot assignment
- One method
 - Sequential circuit may use binary number for control logic design
 - Use sequence register and decoder
- The other method
 - Use one flip-flop per state (one-hot assignment)

Sequence Register and Decoder


- Control logic using Sequence Register and Decoder
 - User binary-valued register for control states
 - Decoder provides corresponding output to each states

State Table for Control Circuit

Present-State Symbol	Present State		Inputs			Next State		Ready	Load_regs	Decr_P	Add_regs	Shift_regs
	G ₁	G ₀	Start	Q[0]	Zero	G ₁	G ₀					
S_idle	0	0	0	X	X	0	0	1	0	0	0	0
S_idle	0	0	1	X	X	0	1	1	1	0	0	0
S_add	0	1	X	0	X	1	0	0	0	1	0	0
S_add	0	1	X	1	X	1	0	0	0	1	1	0
S_shift	1	0	X	X	0	0	1	0	0	0	0	1
S_shift	1	0	X	X	1	0	0	0	0	0	0	1


35

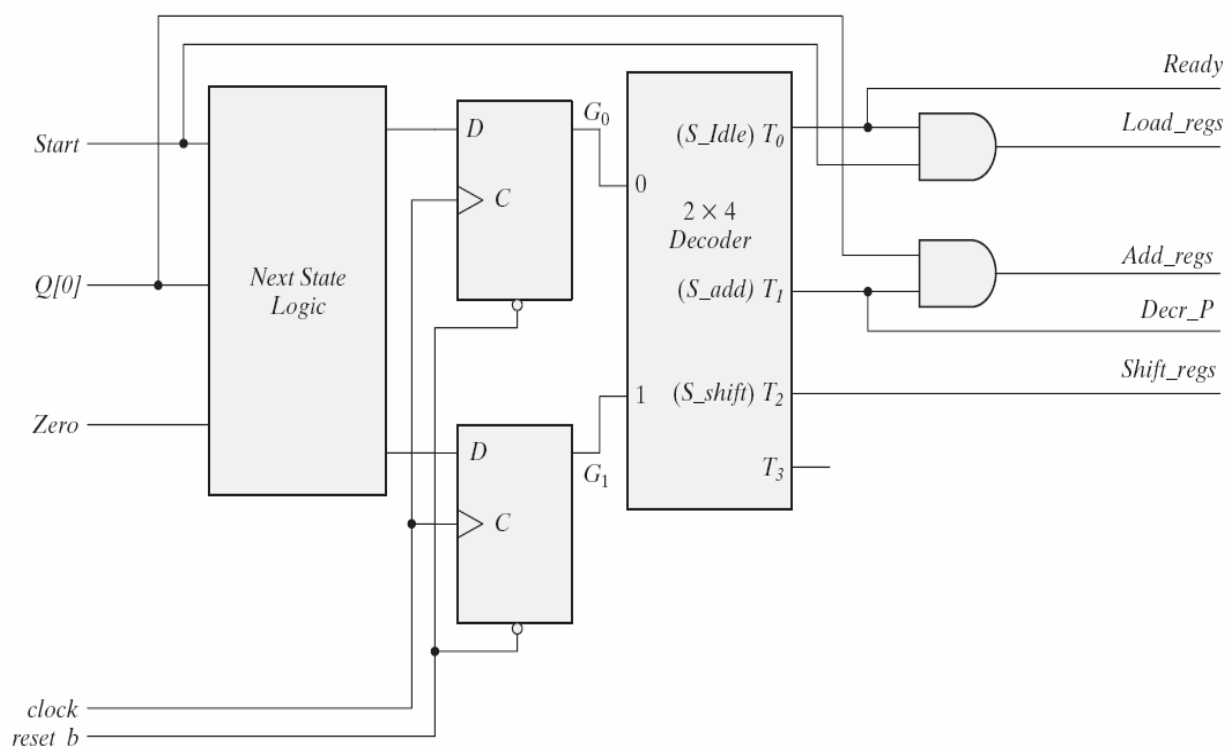Logic Diagram of Control for Binary Multiplier



36

 Logic Diagram of Control for Binary Multiplier



37

Example


- From the next-state conditions in the state table, we find the next state G_1 is equal to 1 when the present state is S_add and is equal to 0 when the present state is S_idle or S_shift . These conditions can be specified by the equation

$$D_{G1} = T_1$$

where D_{G1} is D input of flip-flop G_1 . Similarly, the D input of G_0 is

$$D_{G0} = T_0 Start' + T_2 Zero'$$

 Logic Diagram for One-Hot State Controller



39

Example

- D_{G0} the input to flip-flop G_0 , is set to 1 if the machine is in state G_0 and $Start$ is not asserted, or if the machine is in state G_2 and $Zero$ is asserted. The conditions are specified by the input equation:

$$D_{G0} = G_0 Start' + G_2 Zero$$

Using this procedure for the other three flip-flops, we obtain the remaining input equations:

$$D_{G1} = G_0 Start + G_2 Zero'$$

$$D_{G2} = G_1$$


40

Design with Multiplexers

- Replacing the gates with multiplexers results in a regular pattern of three levels of components.
 - The first level consist of multiplexers that determine the next state of the register.
 - The second level contains a register that holds the present binary state.
 - The three level has a decoder that asserts a unique output line for each control state.


41

 Example of ASM Chart with Four Control Inputs



42

Control Implementation with Multiplexers

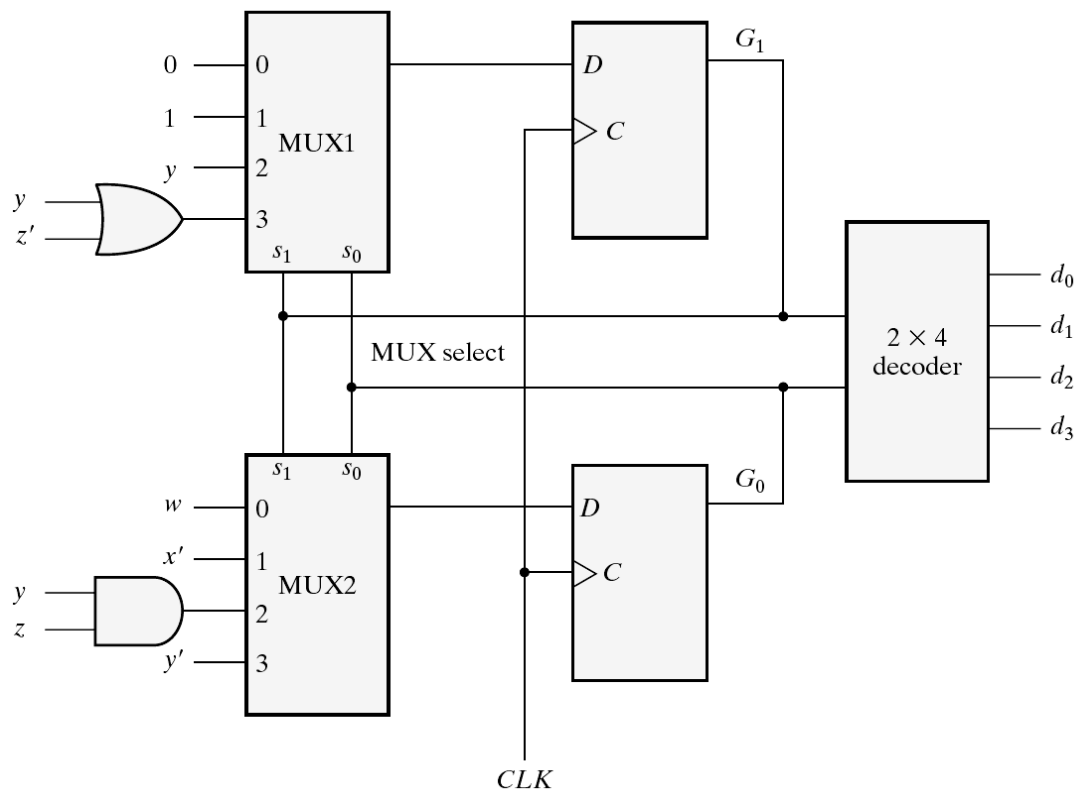

43

State Table


Multiplexer Input Conditions

Present State		Next State		Input Condition	Inputs	
G_1	G_0	G_1	G_0		MUX1	MUX2
0	0	0	0	w'		
0	0	0	1	w	0	w
0	1	1	0	x		
0	1	1	1	x'	1	x'
1	0	0	0	y'		
1	0	1	0	yz'		
1	0	1	1	yz	$yz' + yz = y$	yz
1	1	0	1	$y'z$		
1	1	1	0	y		
1	1	1	1	$y'z'$	$y + y'z' = y + z'$	$y'z + y'z' = y'$

44


Design Example: Count the Number of Ones in a Register

 - A system that is to count the number of 1's in a word of data



45

ASMD Chart

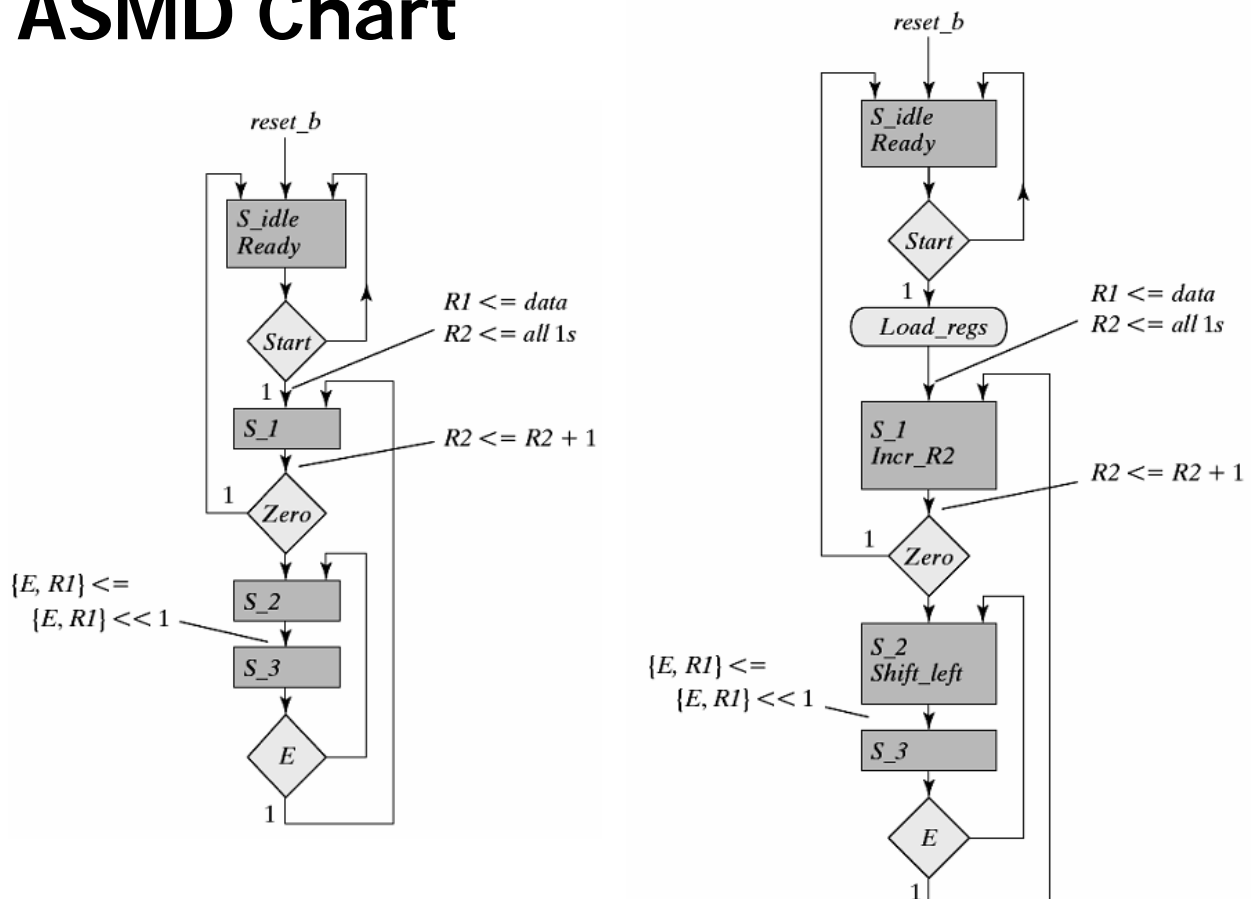

16


State Table

Multiplexer Input Conditions for Design Example

Present State		Next State		Input Conditions	Multiplexer Inputs	
G_1	G_0	G_1	G_0		MUX1	MUX2
0	0	0	0	$Start'$		
0	0	0	1	$Start$	0	$Start$
0	1	0	0	$Zero$		
0	1	1	0	$Zero'$	$Zero'$	0
1	0	1	1	None	1	1
1	1	1	0	E'		
1	1	0	1	E	E'	E

47

Control Implementation

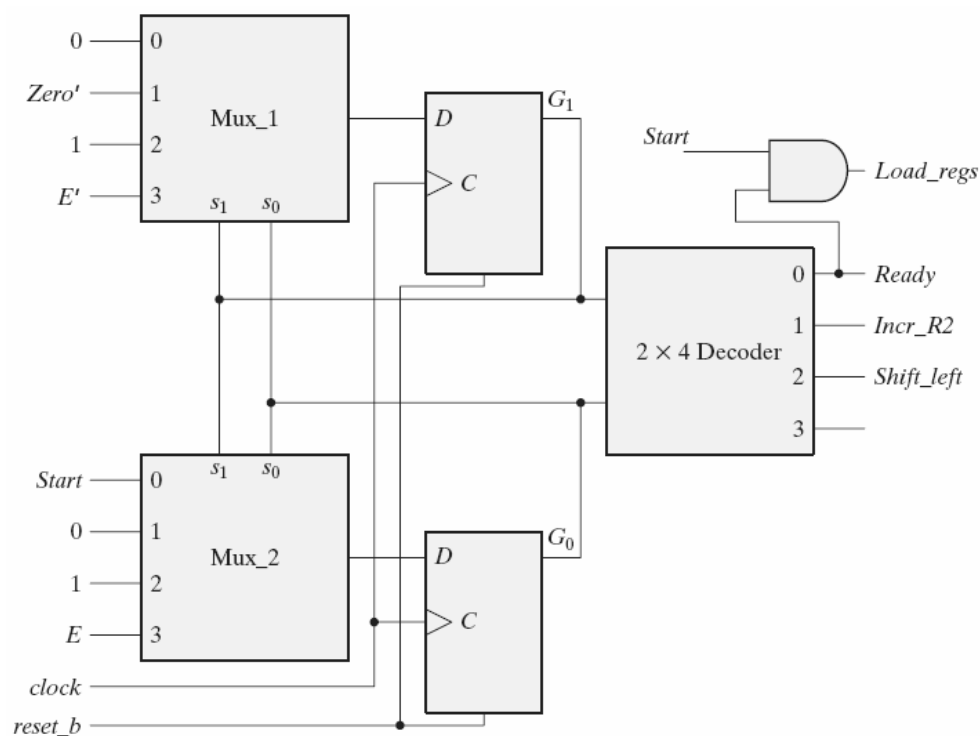

48